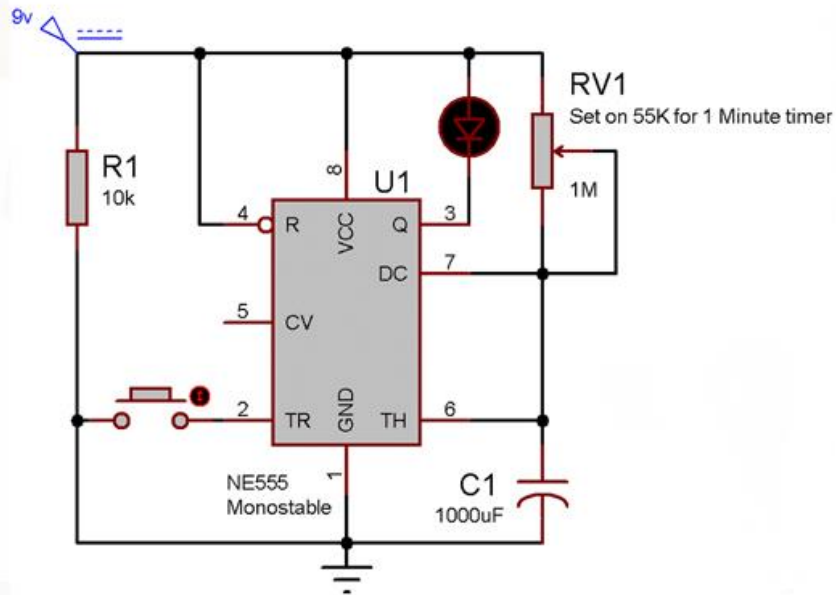


Multivibrators, Timer Circuit and Schmitt Trigger

EEE 203: Electronic Devices and Circuits & Pulse Techniques




Multivibrators


Using Op-Amps

Astable Multivibrator

1

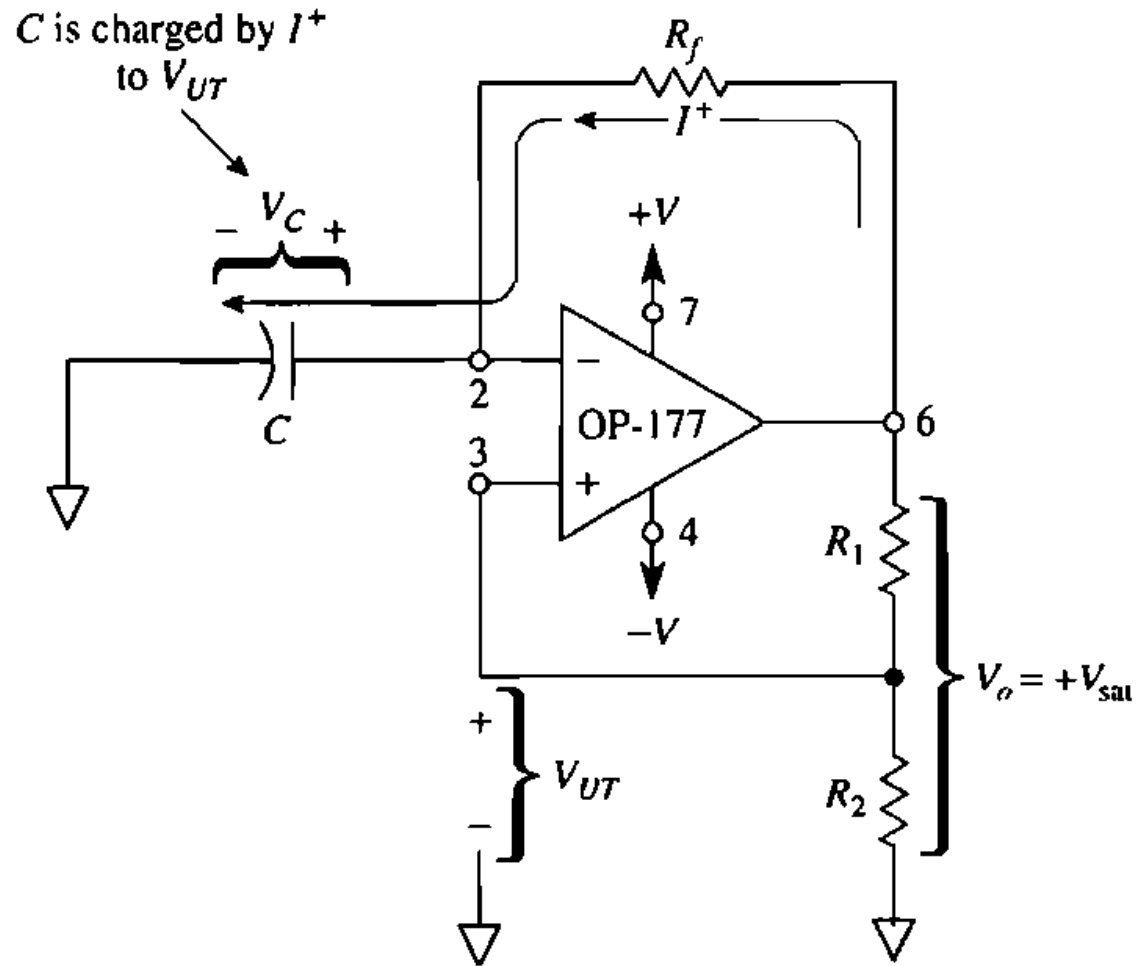

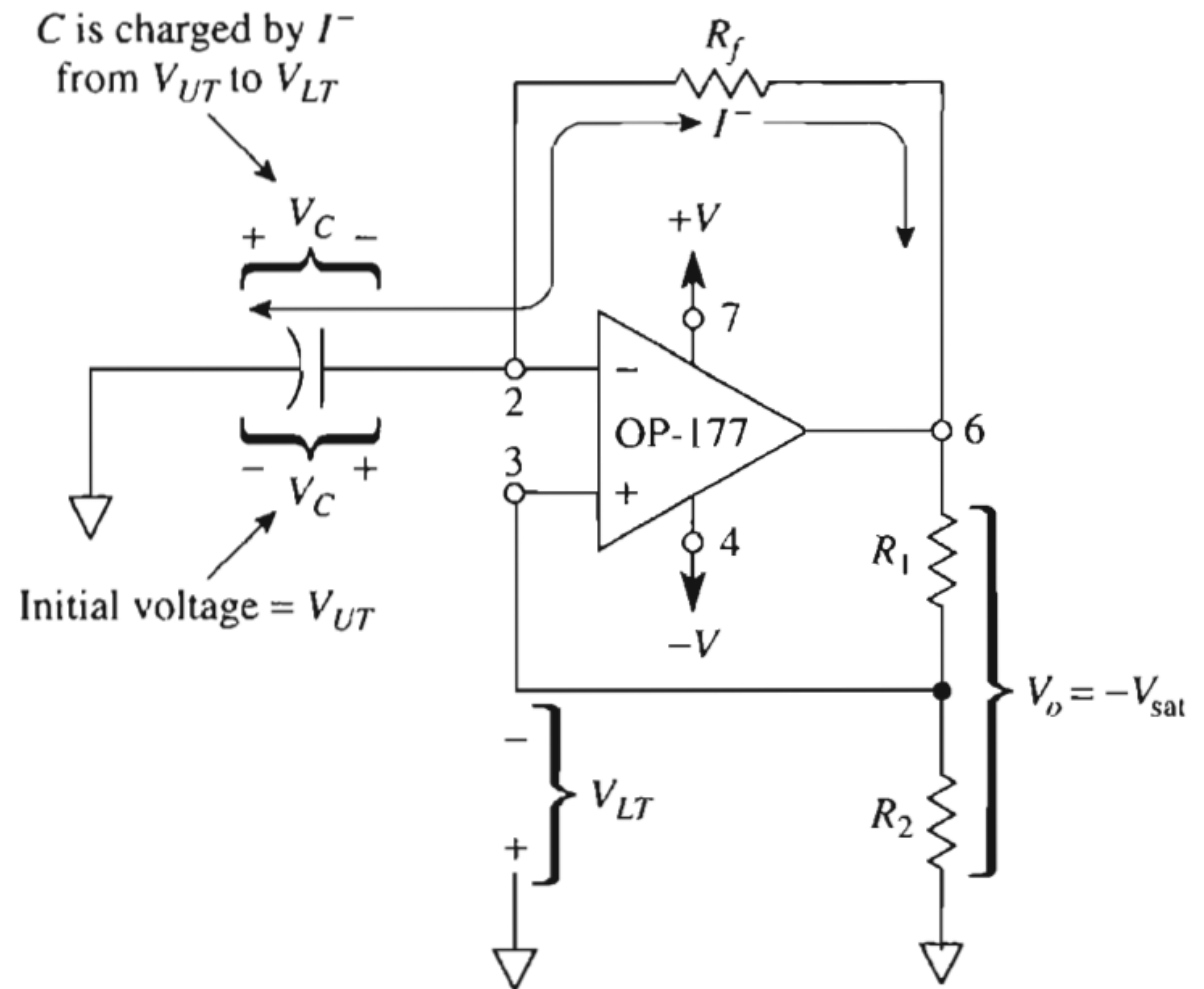
(a) When $V_o = +V_{sat}$, V_C charges toward V_{UT} .



(a) When $V_o = -V_{sat}$, V_C charges toward V_{LT} .

Astable Multivibrator

2

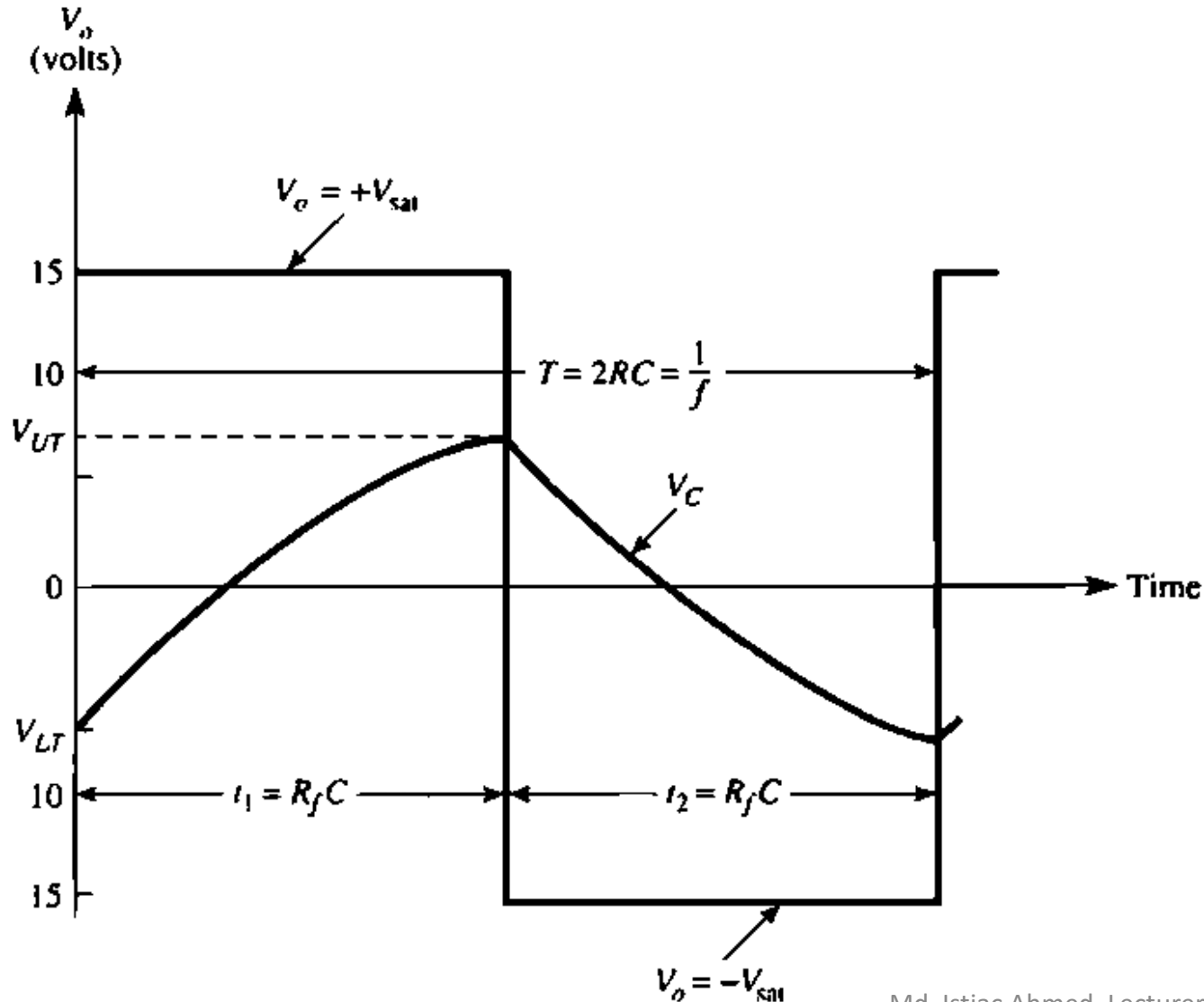

$$V_{UT} = \frac{R_2}{R_1 + R_2} (+V_{sat})$$

$$V_{LT} = \frac{R_2}{R_1 + R_2} (-V_{sat})$$

$$T = 2R_f C \ln \left(\frac{2R_1 + R_2}{R_2} \right)$$

**Self Study: One-shot (Monostable) Multivibrator from Ref 1.


555 Timer




Md. Istiaq Ahmed, Lecturer, EEE, GUB

Internal Diagram

3

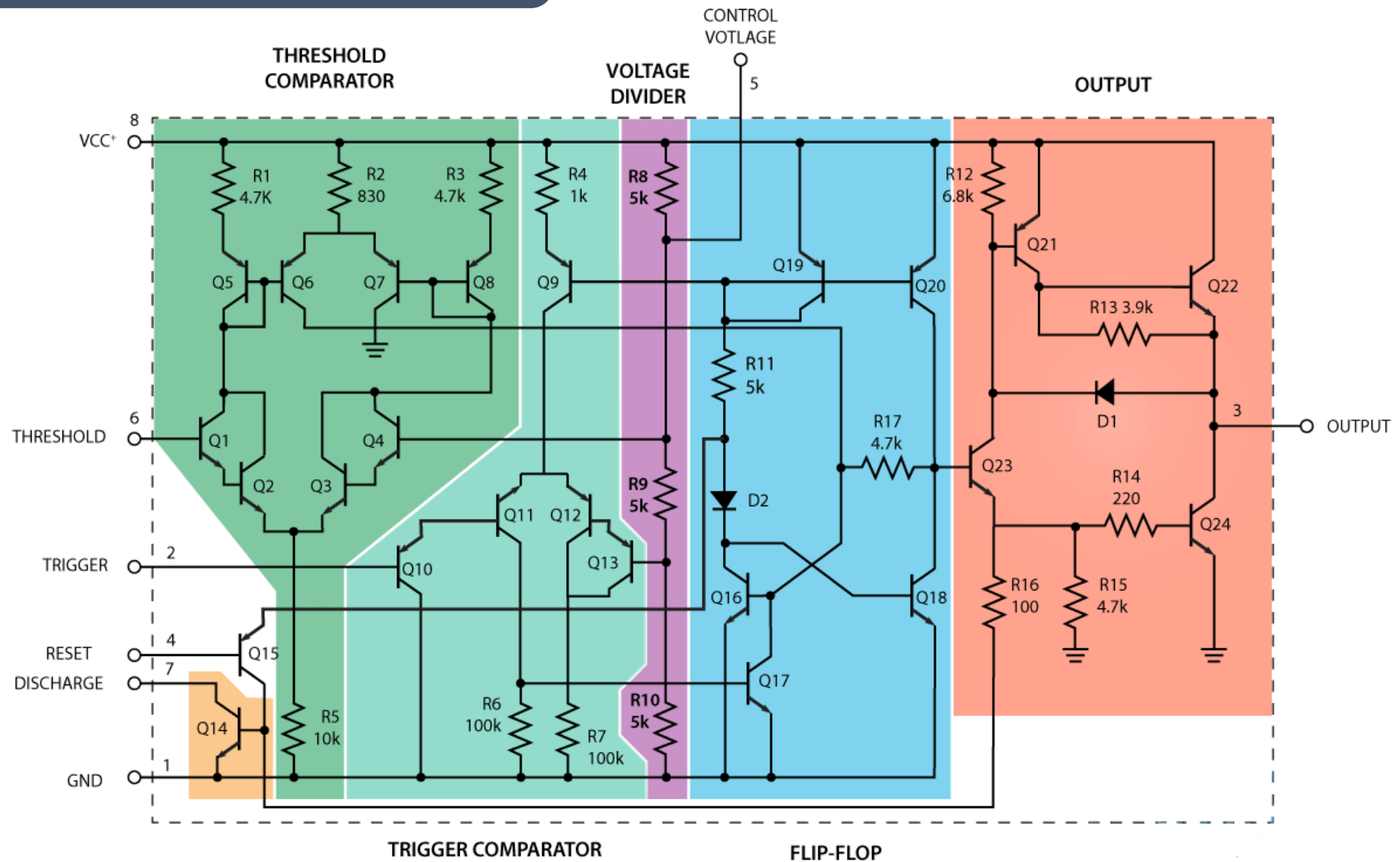

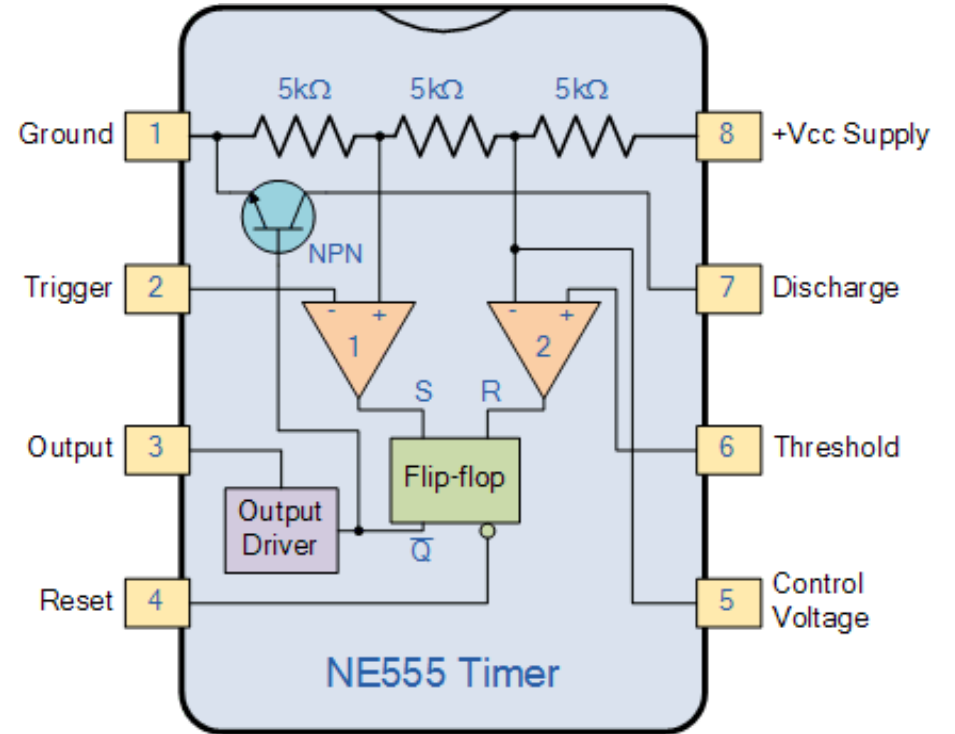
There is a **voltage divider** circuit consisting of **three $5\text{ k}\Omega$ resistors**. Again it has adjustable controls over the **timing** of the output signal. For these reasons, this IC is called **555 Timer**.



Block Diagram


5

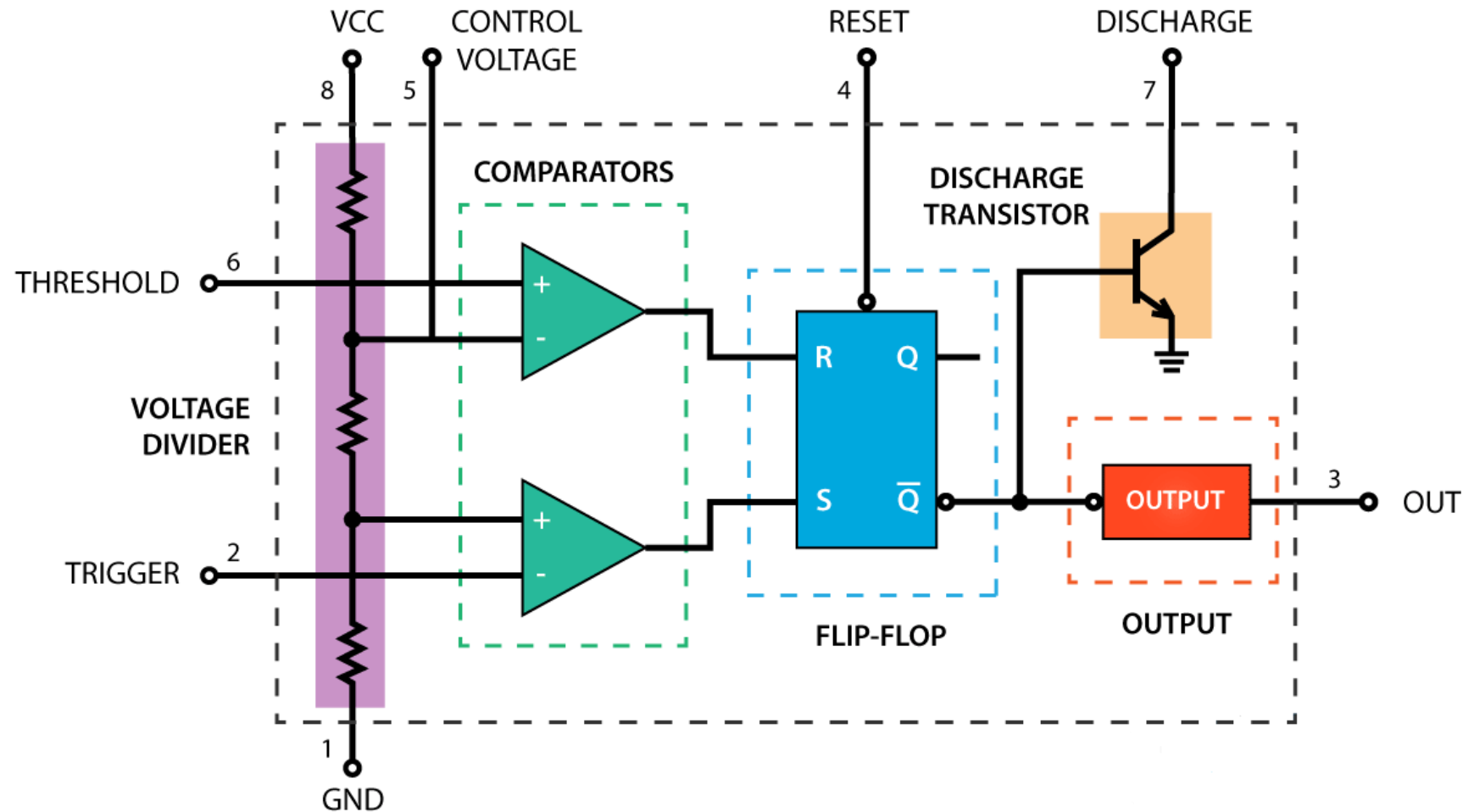1. Voltage Divider
2. Comparators
3. Flip-Flop
4. Discharge
5. Output



Comparator Unit

6

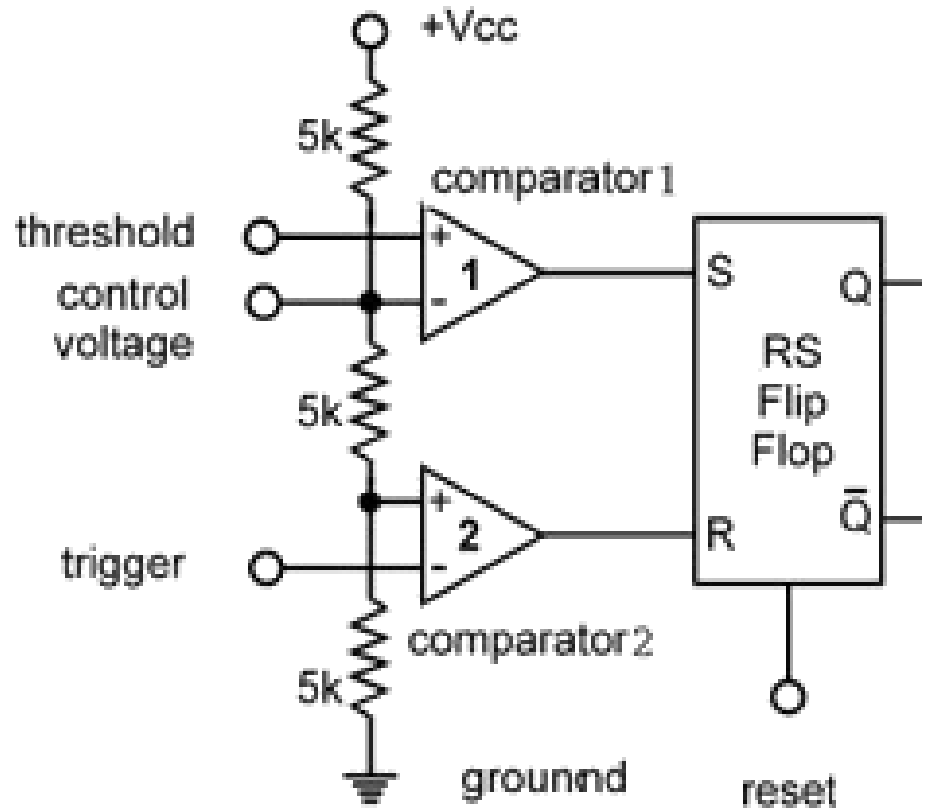


Condition		C1=S	C2=R	Q
$V_{THD} > \frac{2}{3}V_{CC}$	$V_{TRG} > \frac{1}{3}V_{CC}$	1	0	1 [SET]
	$V_{TRG} < \frac{1}{3}V_{CC}$	1	1	[INVALID]
$V_{THD} < \frac{2}{3}V_{CC}$	$V_{TRG} > \frac{1}{3}V_{CC}$	0	0	[NC]
	$V_{TRG} < \frac{1}{3}V_{CC}$	0	1	0 [RESET]

Output Unit


7

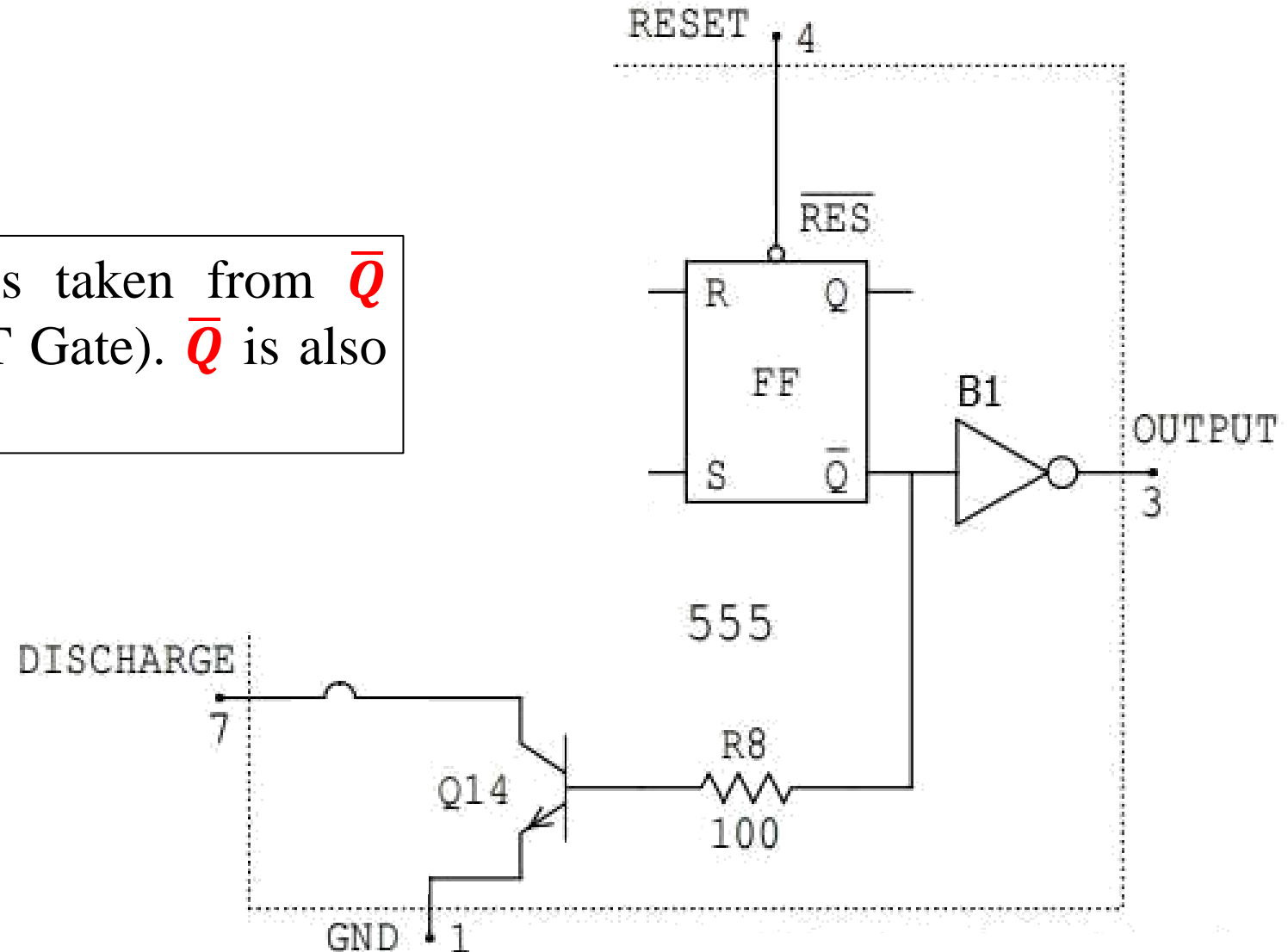The output of the 555 timer is taken from \bar{Q} through an inverting buffer (NOT Gate). \bar{Q} is also fed to the discharge unit.



Discharge Unit


8

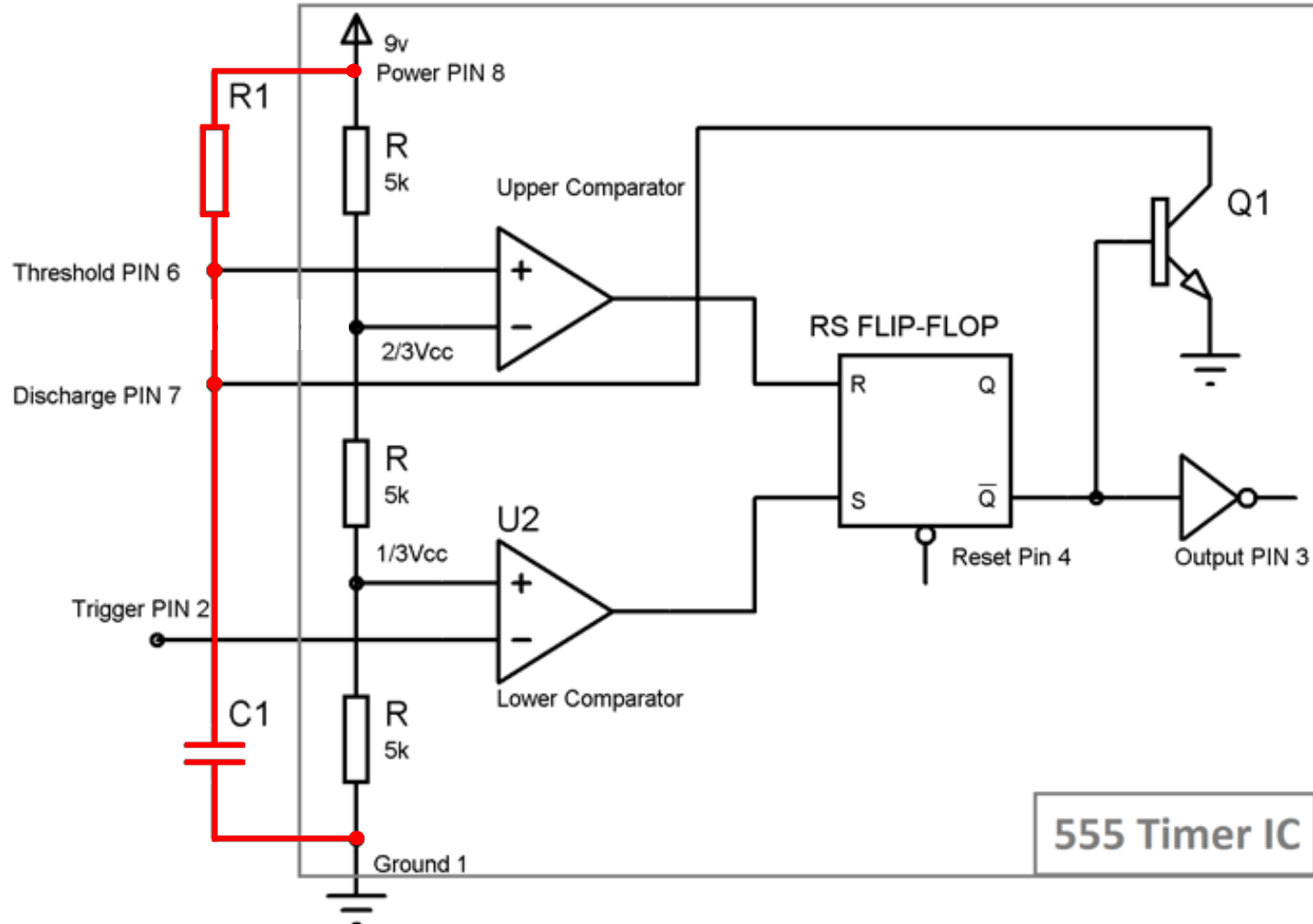

\bar{Q}	O/P	Q1	Capacitor Status
1	0	ON	Discharging
0	1	OFF	Charging

Monostable Multivibrator using 555 Timer IC

9


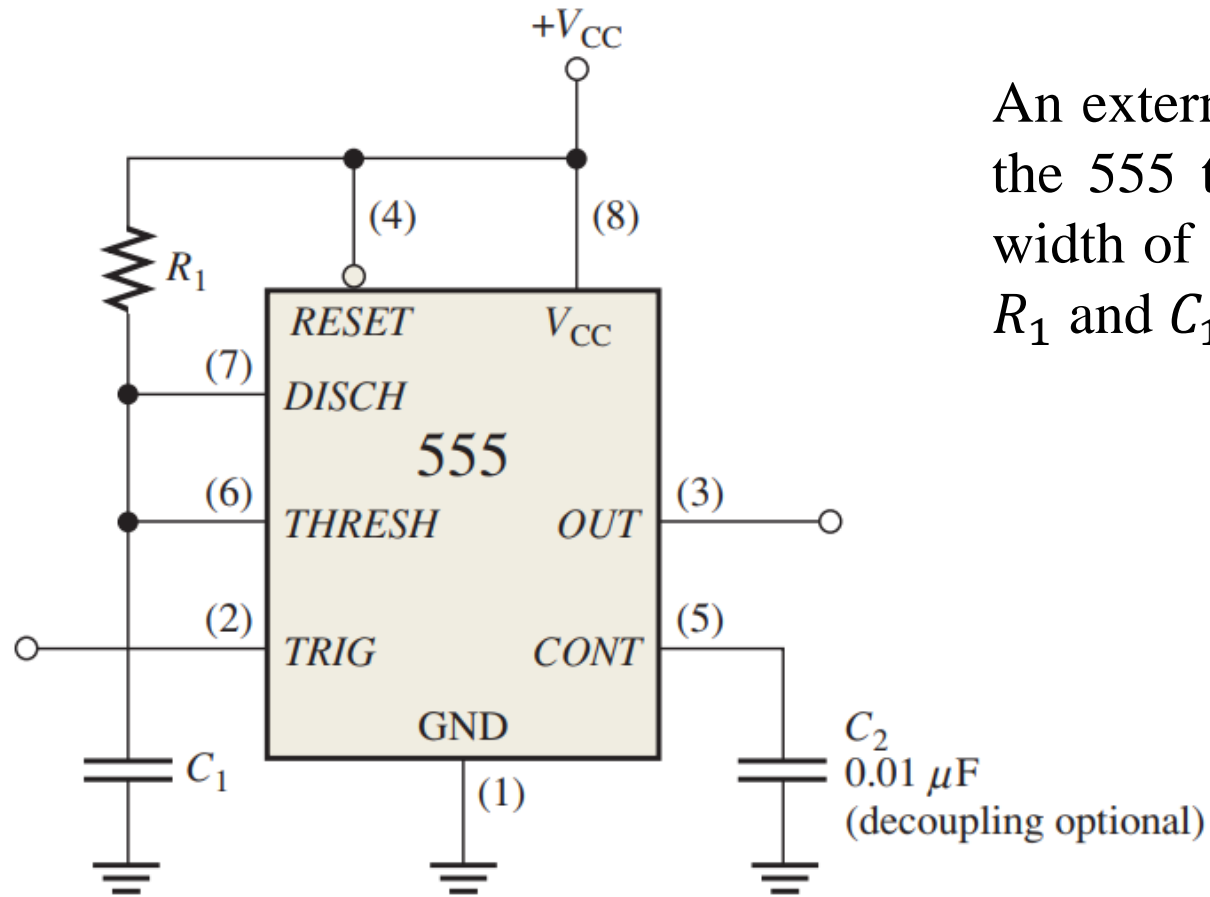


An external resistor R_1 and capacitor C_1 is used to set up the 555 timer as a monostable multivibrator. The pulse width of the output is determined by the time constant of R_1 and C_1 according to the following formula;

$$t_w = 1.1R_1C_1$$

Monostable Multivibrator


10

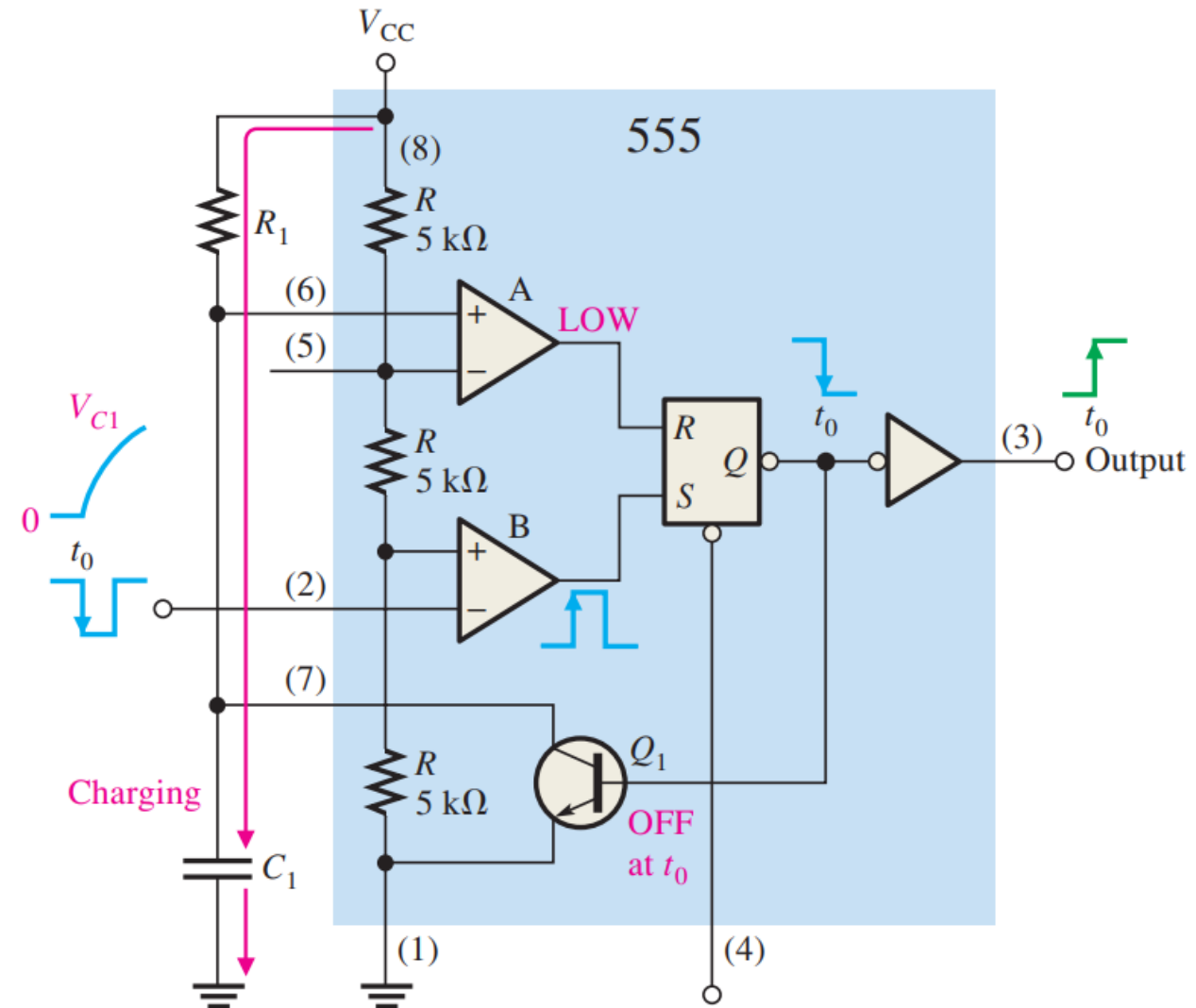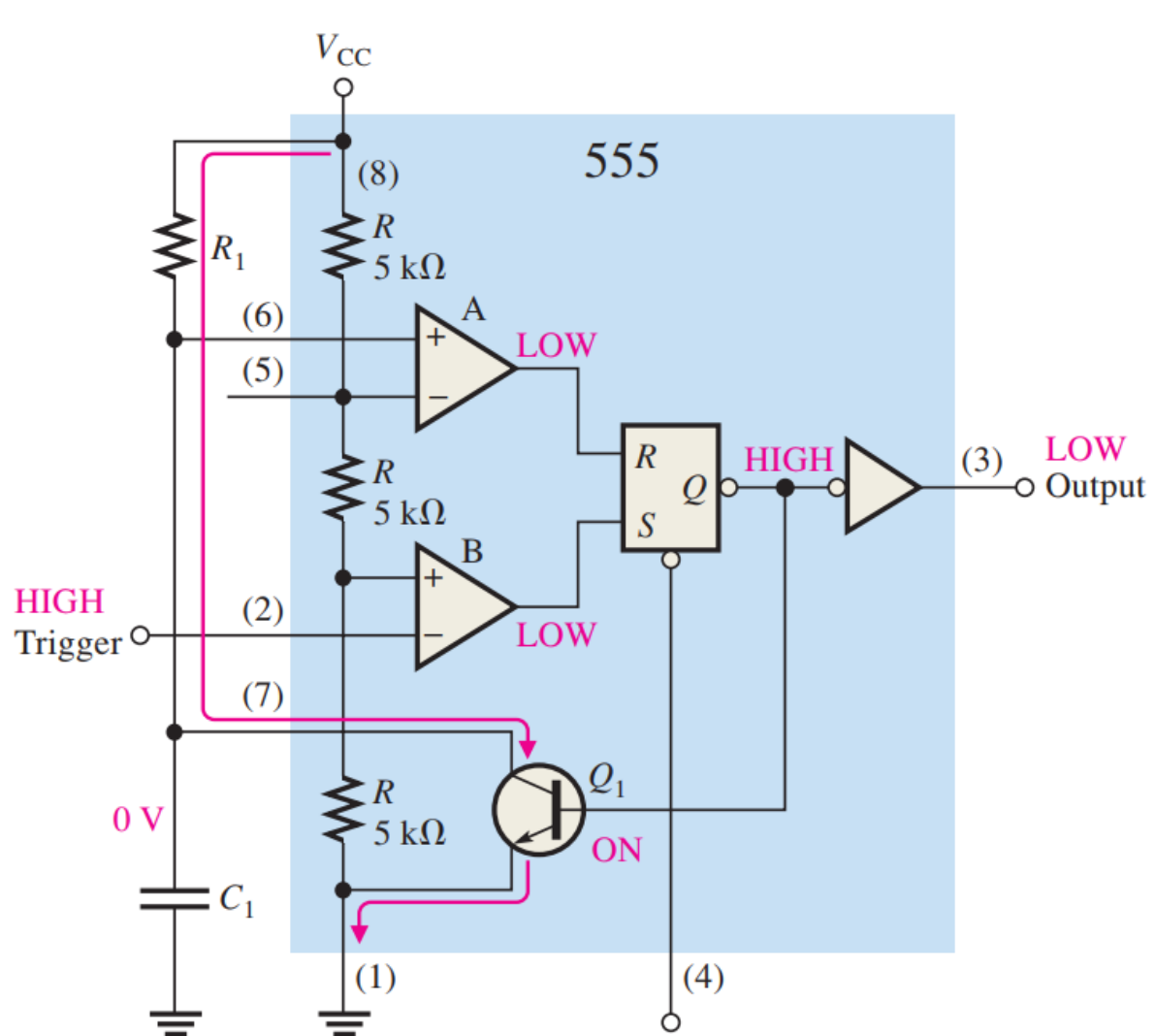

(a) Prior to triggering. (The current path is indicated by the red arrow.) (b) When triggered

Monostable Multivibrator

11


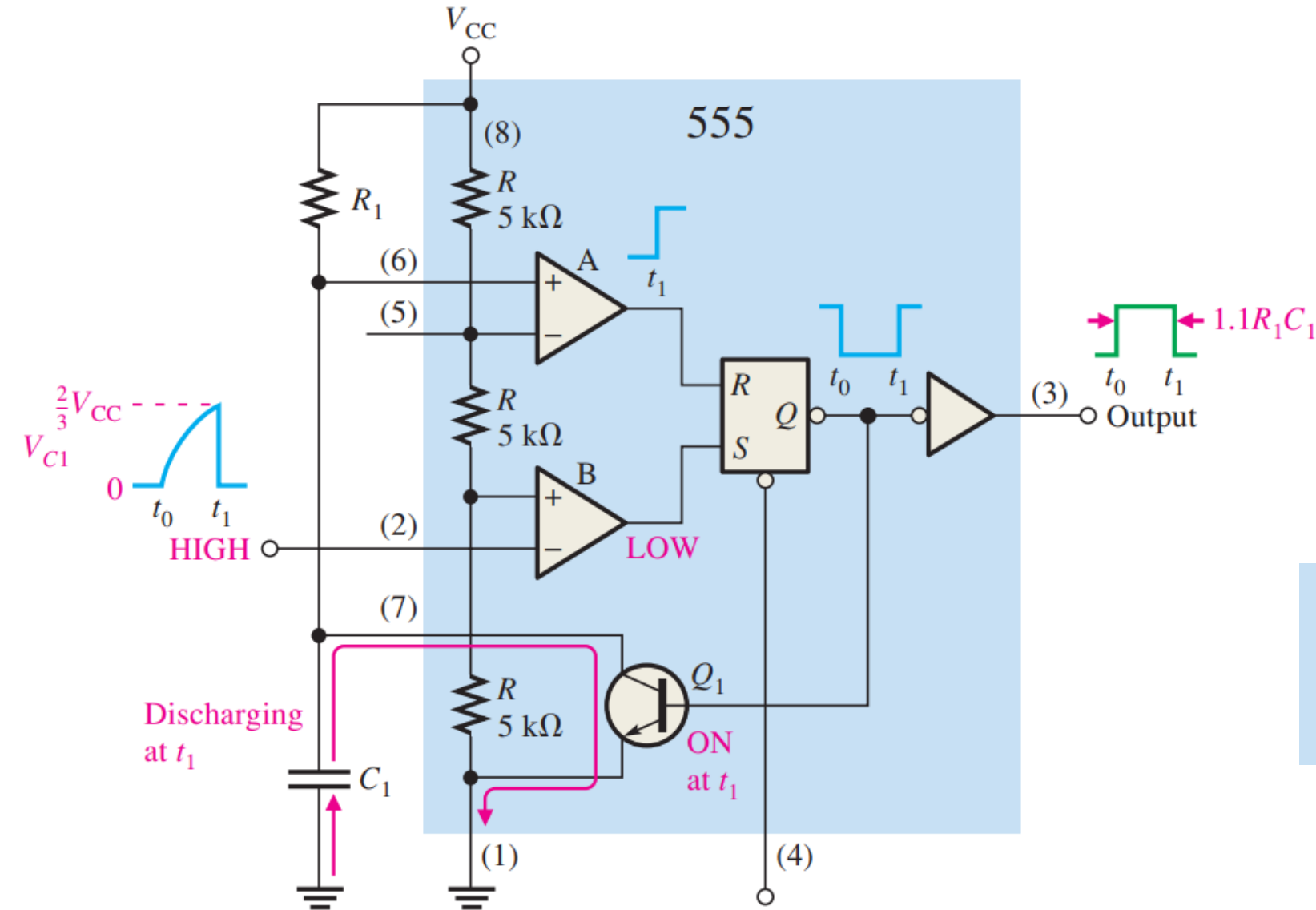


Determine the pulse width of a 555 timer one-shot when $C = 1\mu F$ and $R = 10k\Omega$

(c) At end of charging interval

Astable Multivibrator using 555 Timer IC

12

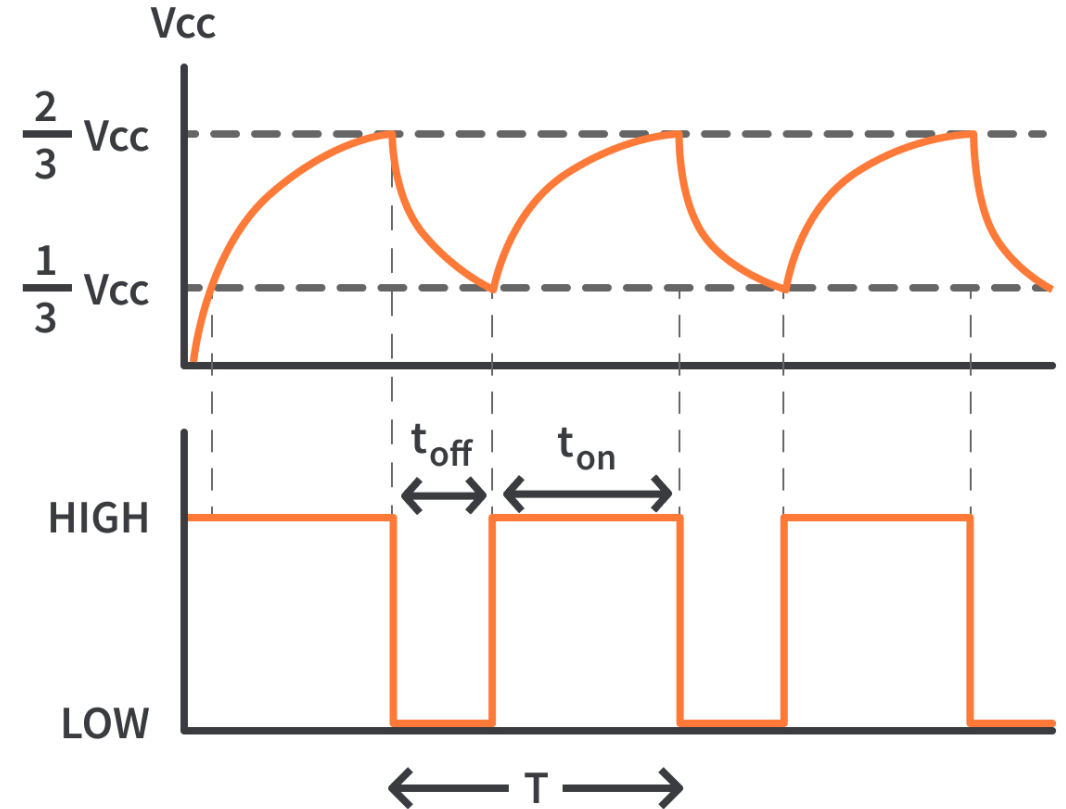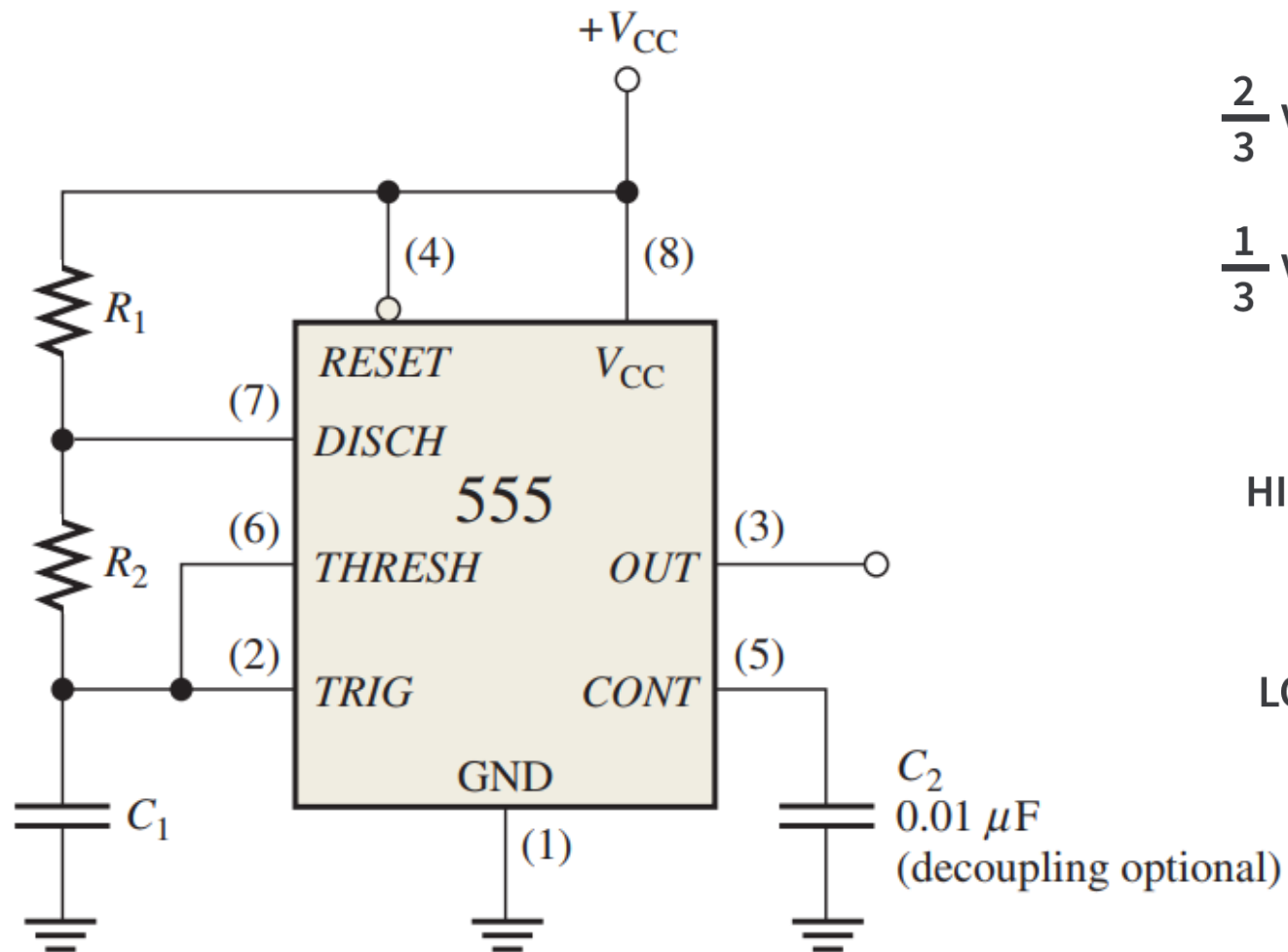

Astable Multivibrator

13

$$\text{Frequency, } f = \frac{1.44}{(R_1 + 2R_2)C_1}$$

$$\text{Duty Cycle} = \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) \times 100\%$$

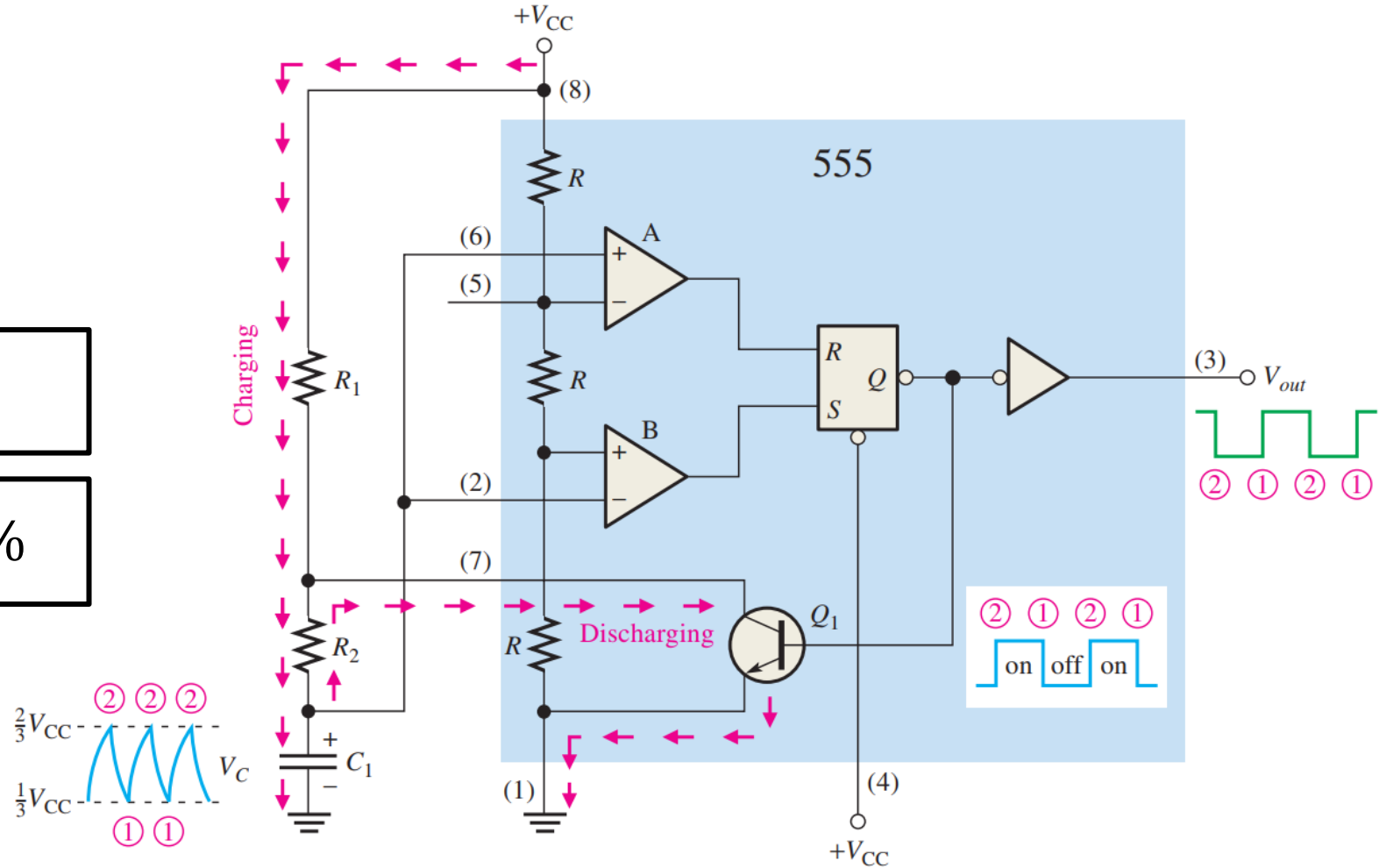


FIGURE 7-57 Operation of the 555 timer in the astable mode.


A 555 timer configured to run in the astable mode is shown. Determine the frequency of the output and the duty cycle.

$$f = \frac{1.44}{(R_1 + 2R_2)C_1} = \frac{1.44}{(2.2k\Omega + 9.4k\Omega)0.022\mu F}$$


$$f = 5.64 \text{ kHz}$$

$$D.C. = \left(\frac{R_1 + R_2}{R_1 + 2R_2} \right) 100\% = \left(\frac{2.2k\Omega + 4.7k\Omega}{2.2k\Omega + 9.4k\Omega} \right) 100\%$$


$$\text{Duty Cycle} = 59.5\%$$

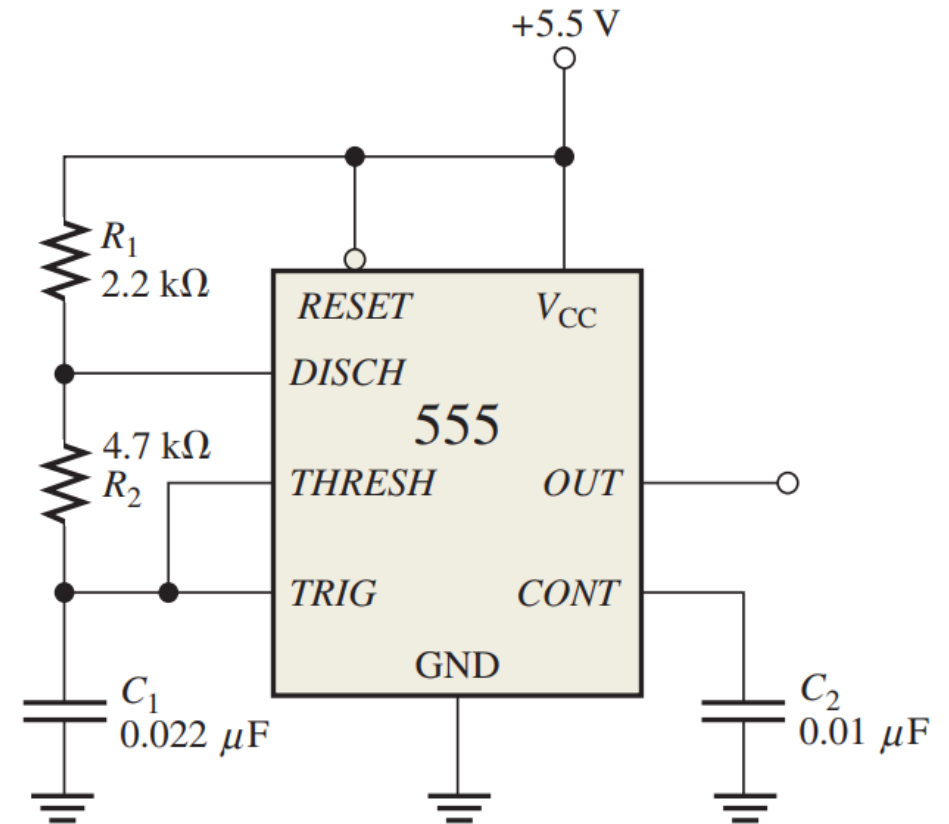

Schmitt Trigger

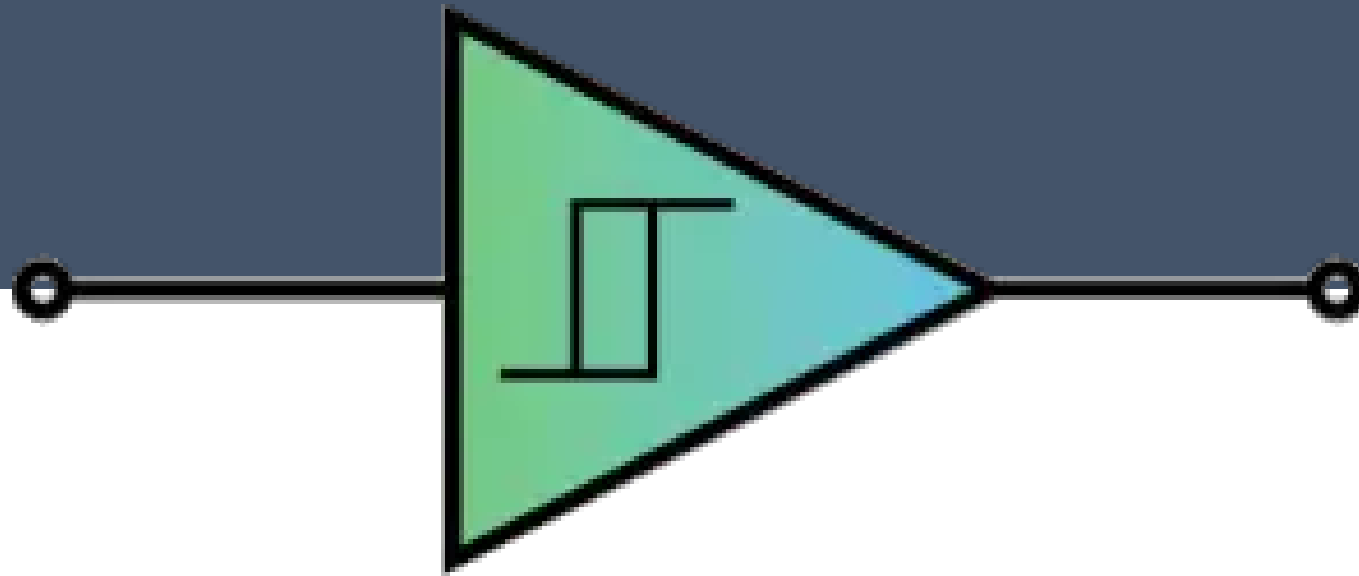


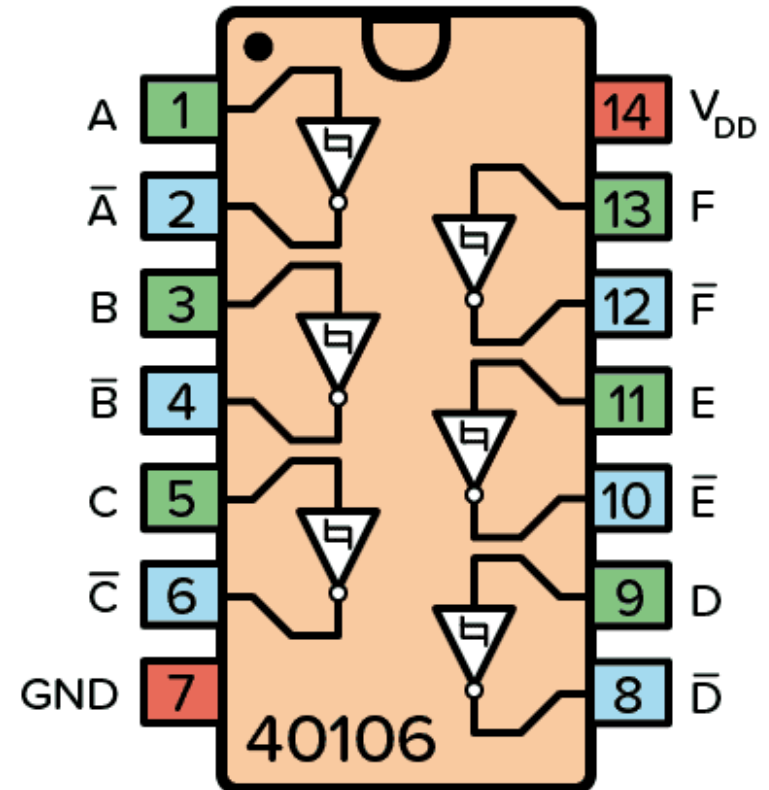
Schmitt trigger is basically a voltage comparator consisting of operational amplifier circuits. Both inverting and non-inverting comparator can be designed. Schmitt trigger eliminates the noise effect.



Voltage Comparator



16

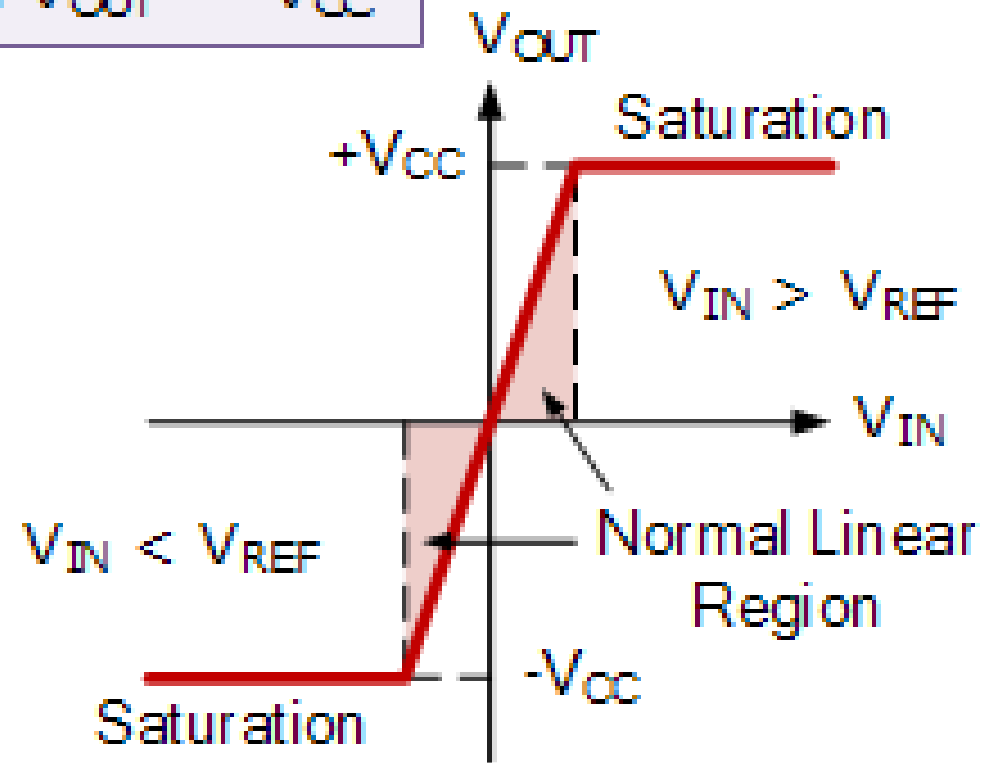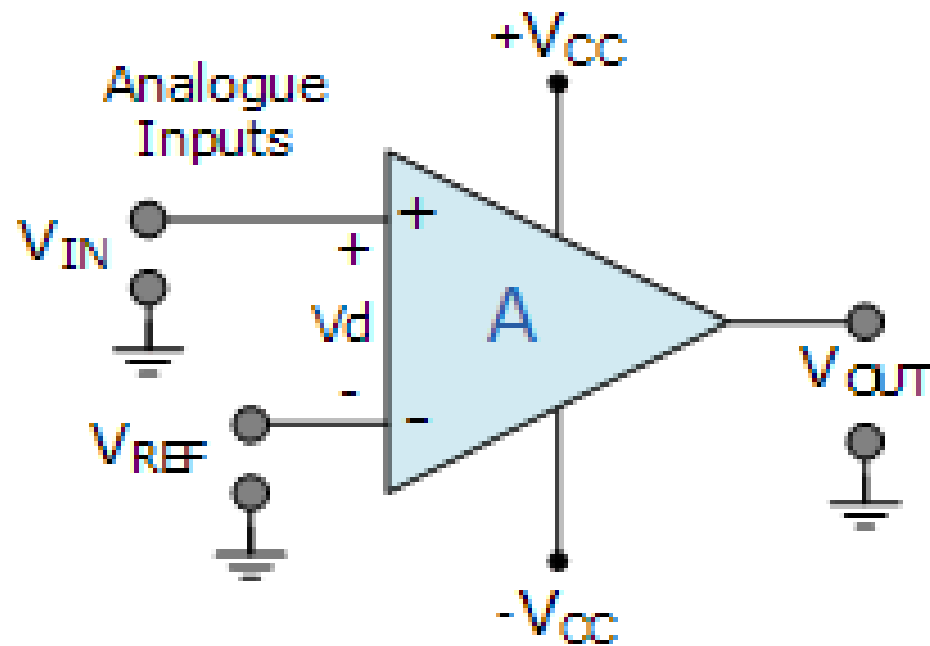If $V_{IN} > V_{REF}$ then $V_{OUT} = +V_{CC}$
If $V_{IN} < V_{REF}$ then $V_{OUT} = -V_{CC}$




Noise Effect on Comparator

17

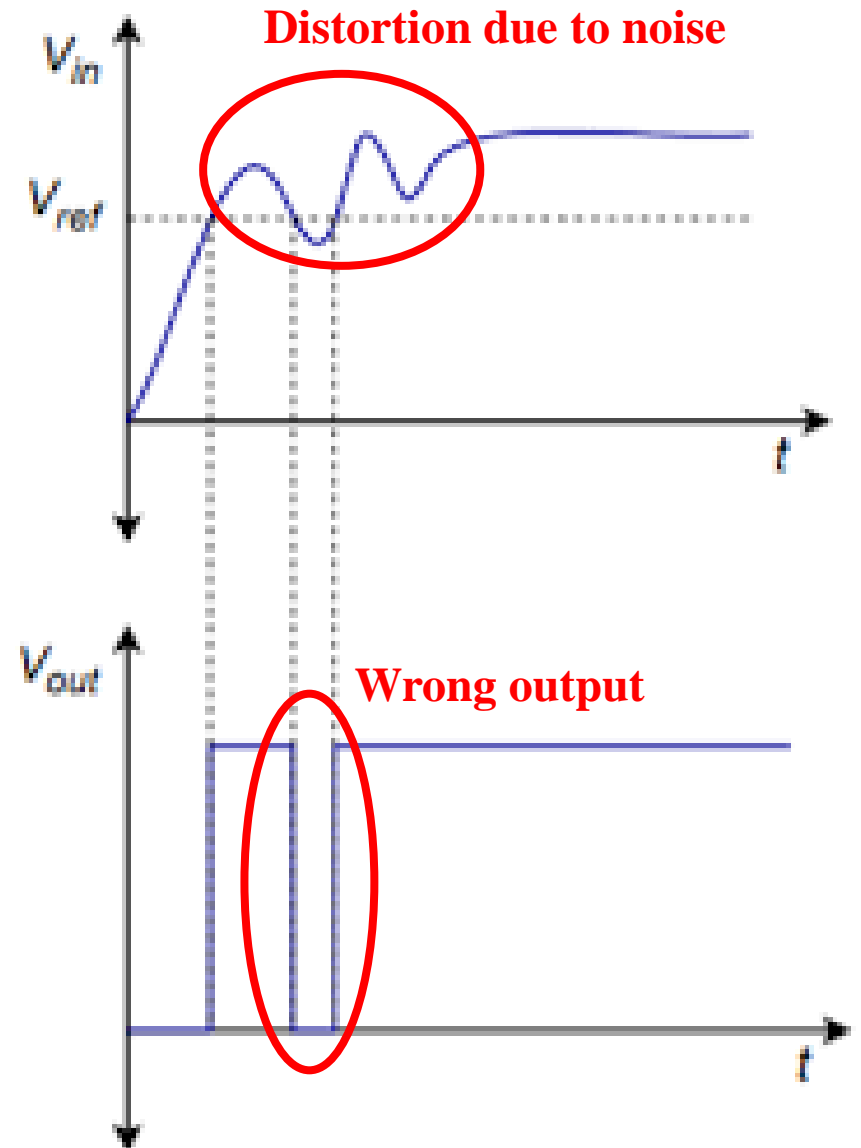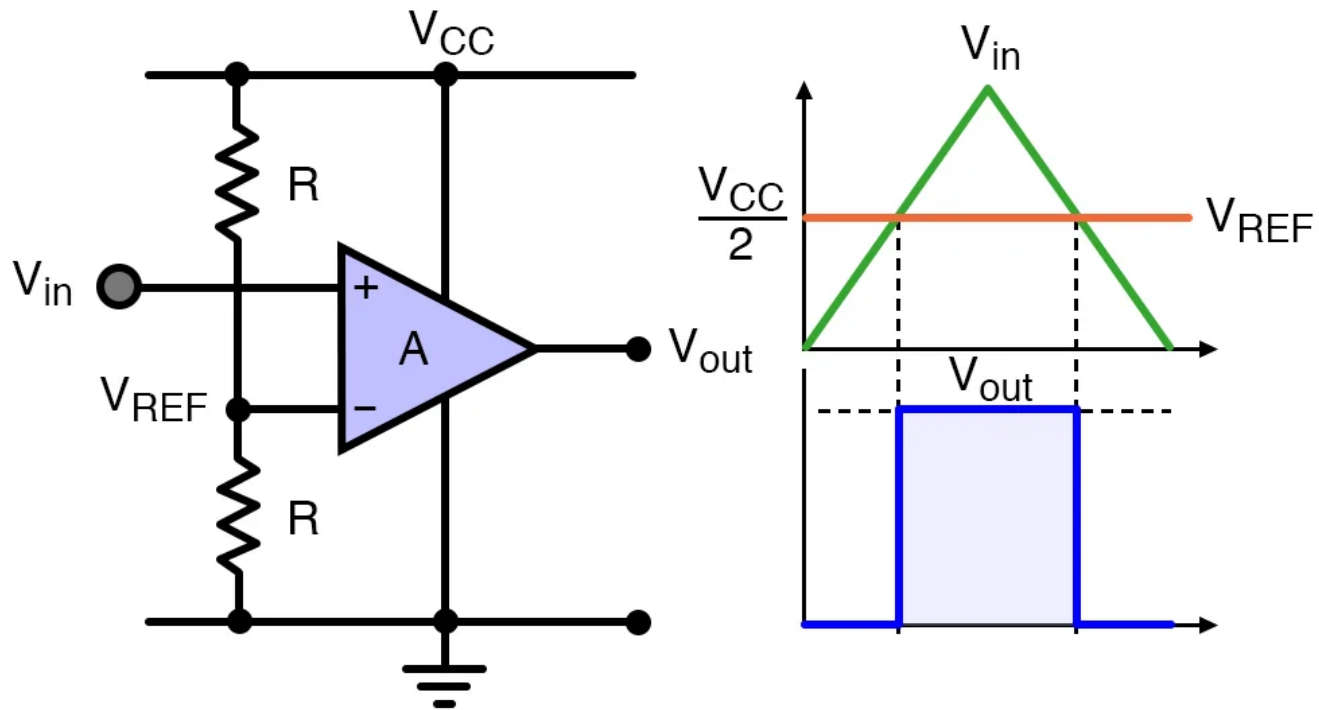


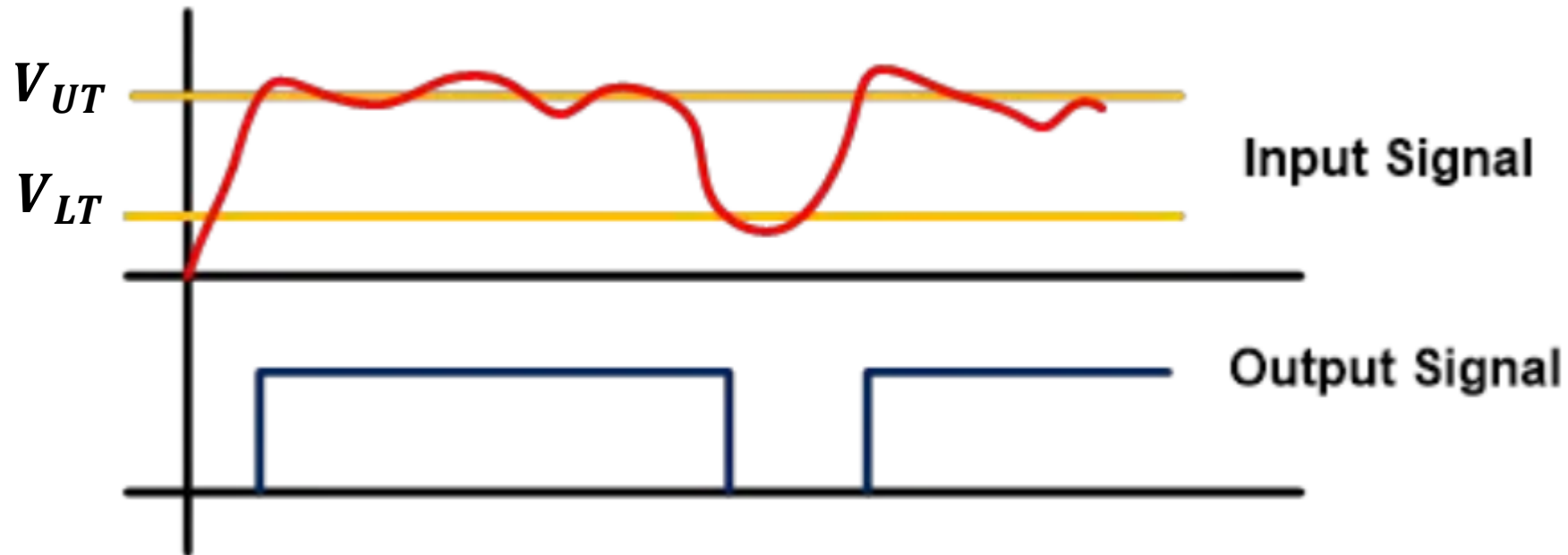Unlike typical comparator, Schmitt trigger uses 2 reference voltages; **Upper Threshold Voltage, V_{UT}** and **Lower Threshold Voltage, V_{LT}** , respectively.




1. The output will be **LOW** until the signal crosses the upper threshold voltage when the comparator is turned on.
2. If the noise affected input signal is greater than or equal the upper threshold voltage ($V_{in} \geq V_{UT}$), then the comparator output is **HIGH**.
3. If the noise affected input signal is less than the upper threshold voltage but greater than the lower threshold voltage ($V_{LT} < V_{in} < V_{UT}$), still the comparator output is **HIGH**.
4. If the noise-affected input signal is less than or equal the lower threshold voltage ($V_{in} \leq V_{LT}$), the comparator output is **LOW**.

Draw the output for the given output signals

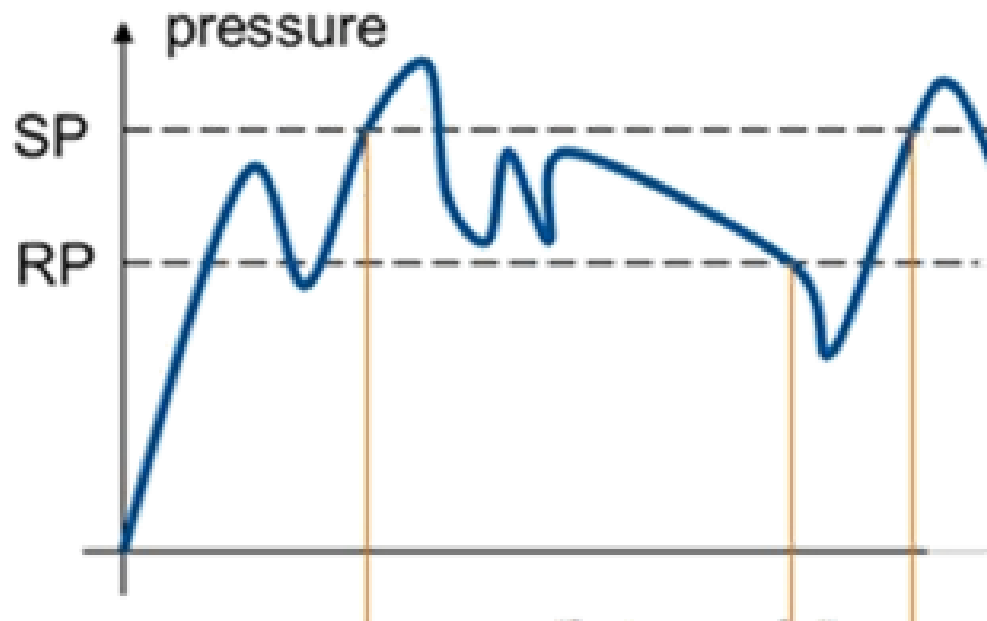


Signal 1

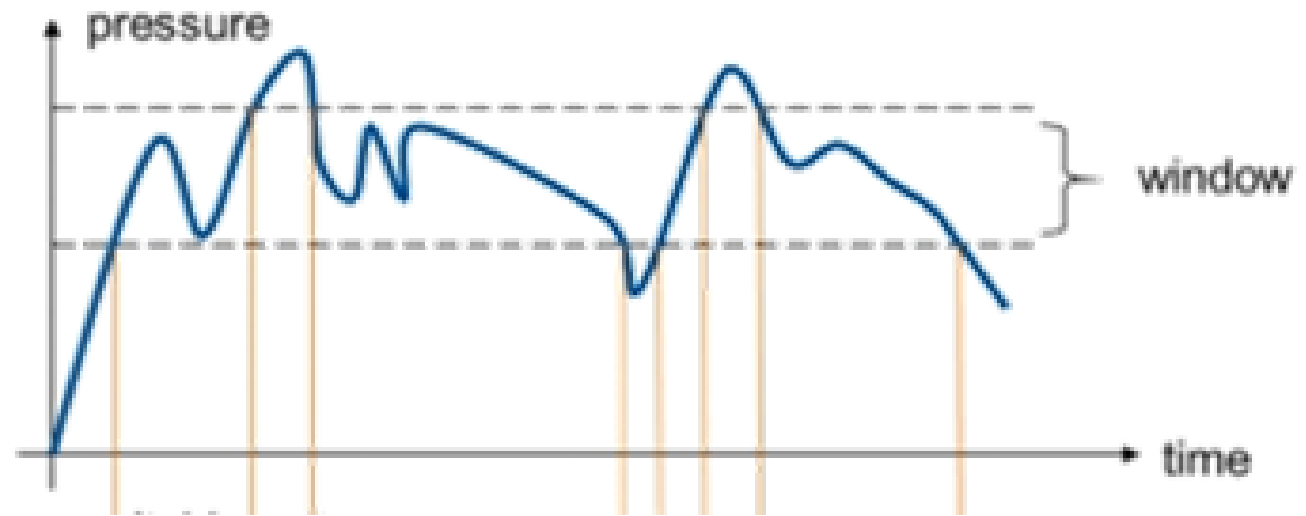


Signal 2

Hysteresis Characteristics

21

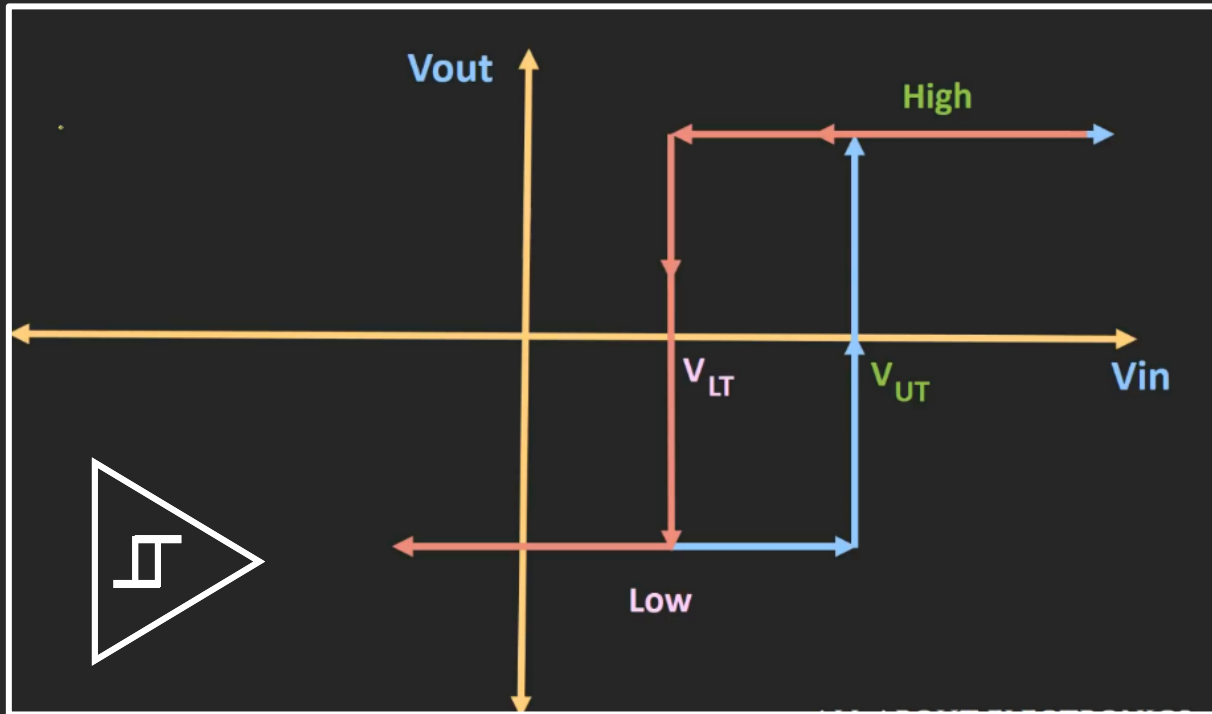


Non-inverting

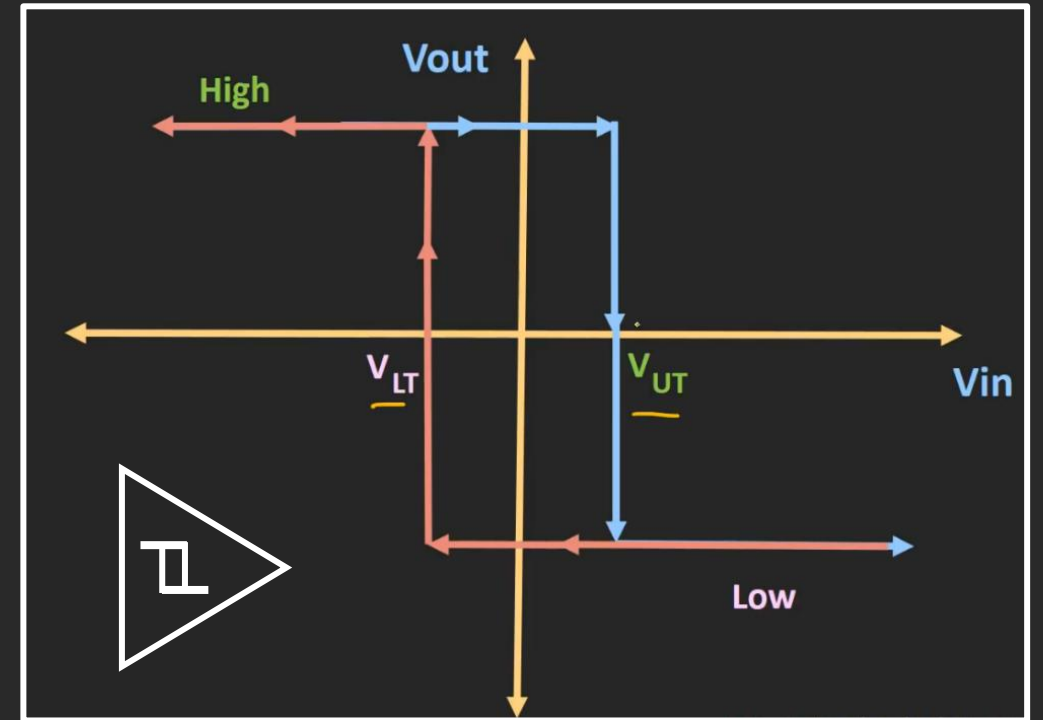

Inverting

Non-inverting Schmitt Trigger

22

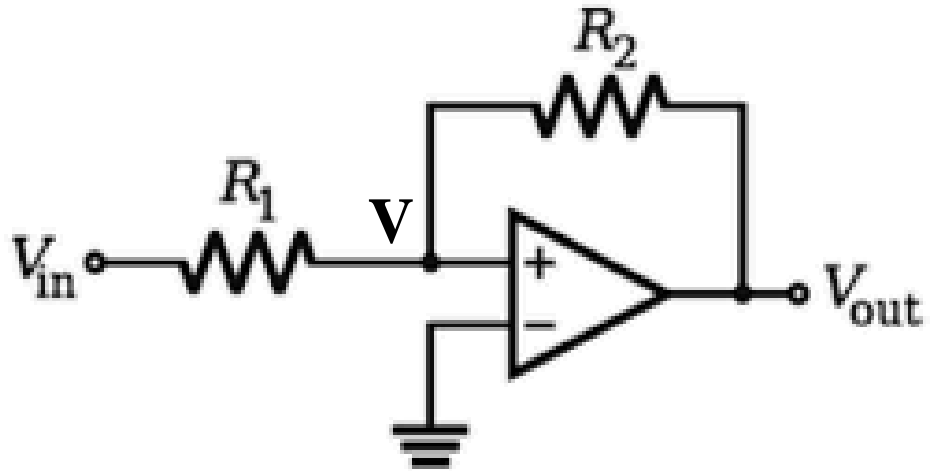

$$\begin{aligned} V &> 0; V_{out} = V_H \\ V &< 0; V_{out} = V_L \end{aligned}$$

Applying KCL at V, we get,

$$V = \frac{R_1}{R_1 + R_2} V_{out} + \frac{R_2}{R_1 + R_2} V_{in}$$

Assuming when $V = V_1$, $V_{out} = V_H$

$$\text{Therefore, } V_1 = \frac{R_1}{R_1 + R_2} V_L + \frac{R_2}{R_1 + R_2} V_{in}$$

Now, following the condition, $\frac{R_2}{R_1 + R_2} V_{in} > -\frac{R_1}{R_1 + R_2} V_L$


Finally, $V_{in} > -\frac{R_1}{R_2} V_L$ and so

$$V_{UT} = -\frac{R_1}{R_2} V_L$$

Similarly,


$$V_{LT} = -\frac{R_1}{R_2} V_H$$

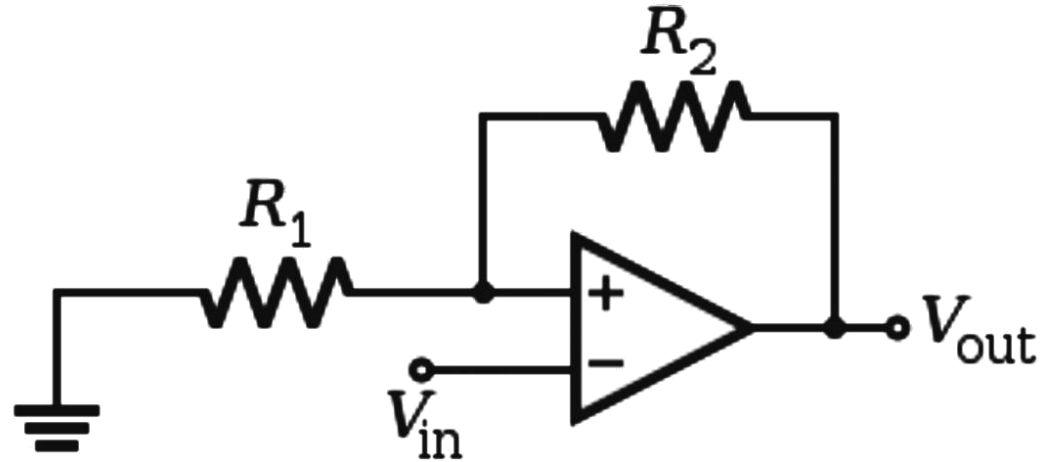Derive the formulations for inverting Schmitt trigger




Inverting Schmitt Trigger Circuit


References

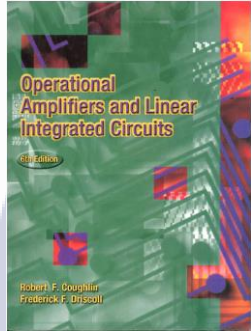

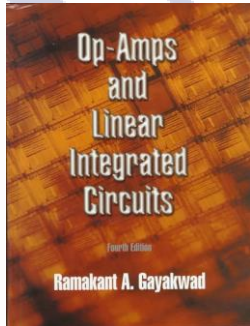1. Operational Amplifiers and Linear Integrated Circuits, 6th Ed., R.F. Coughlin, F.F. Driscoll
Chapter 06: Section 6.0 – 6.2; All examples, Relevant exercises



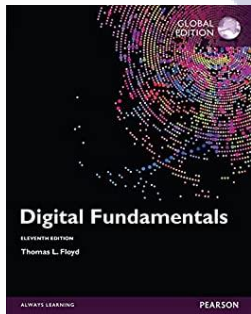2. Op-Amps and Linear Integrated Circuits, 4th Ed., R.A. Gayakwad



3. Digital Fundamentals 11th Ed., T.L. Floyd
Chapter 07

