

Course Instructor



Md. Saklain Morshed
Lecturer, EEE
Green University of Bangladesh

Introduction to MOSFET and Classification


Welcome to CMOS Gate Implementation

Observation – Pull Up & Pull Down Network


Example-1

Video Link of this Lecture:


https://youtu.be/zfPNEz_sNEE

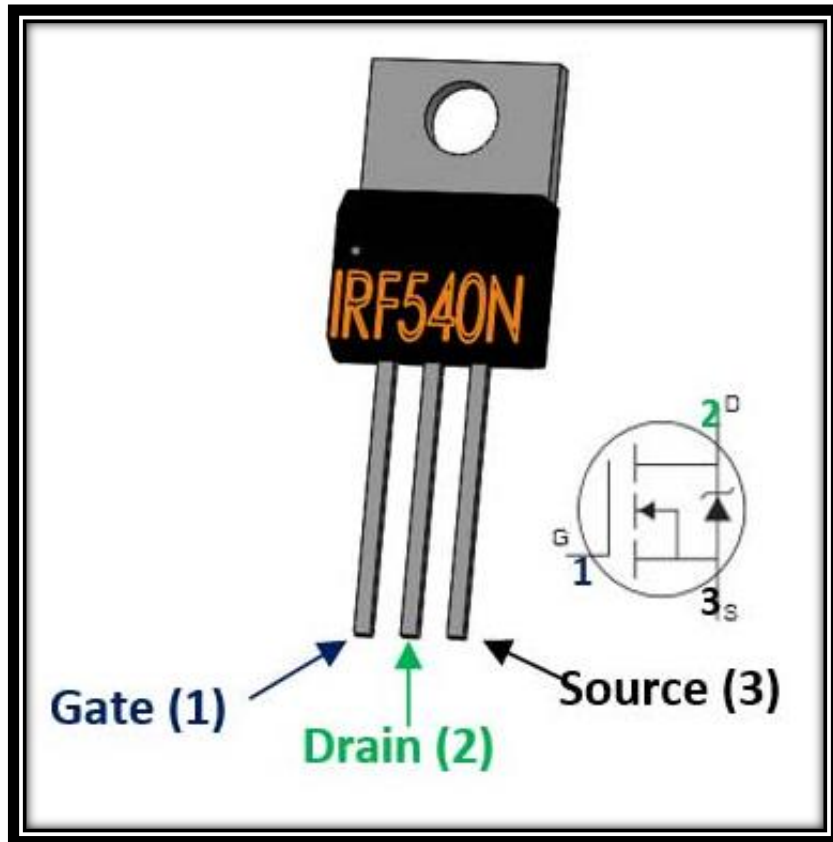


Physical Structure

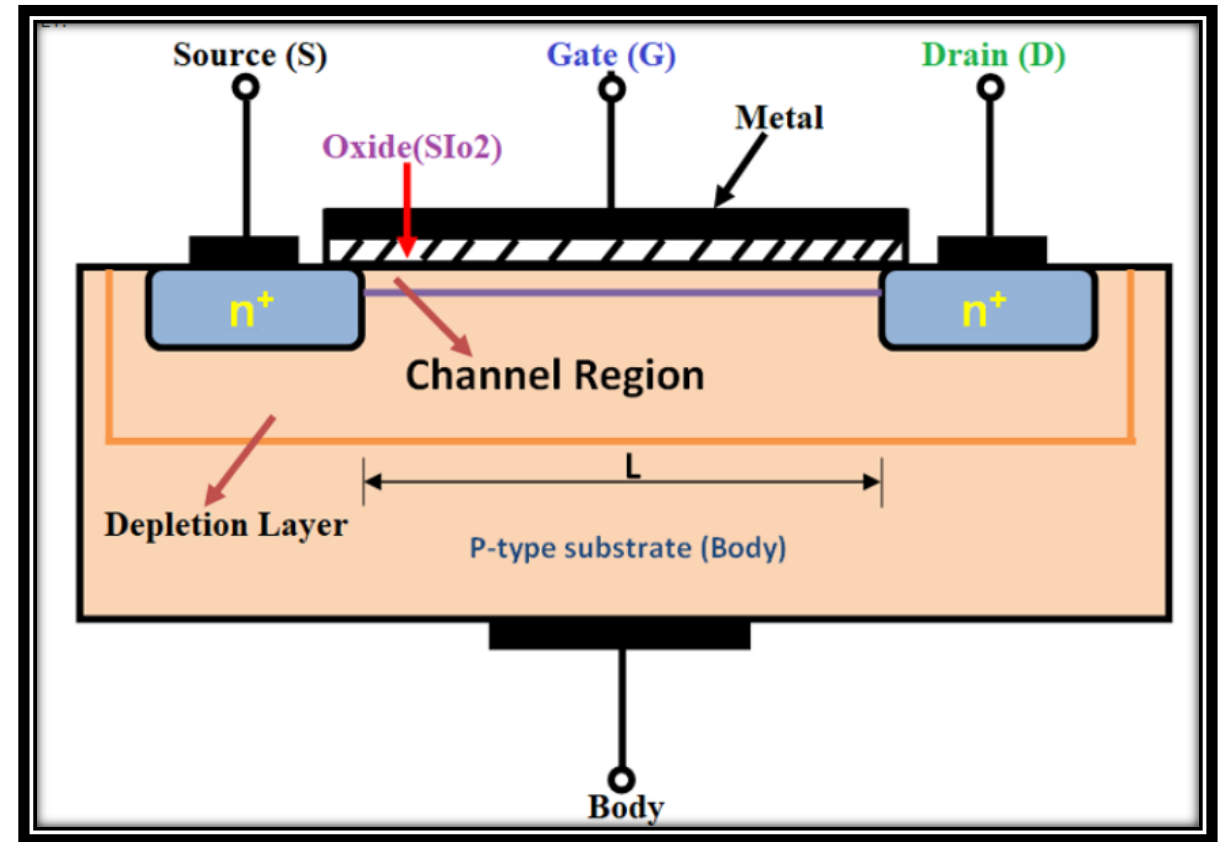


Schematic Structure

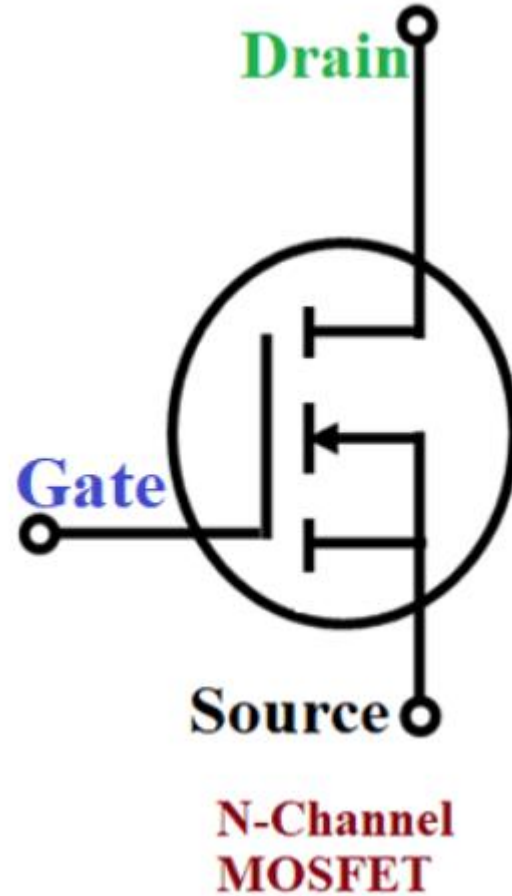

Channel Type

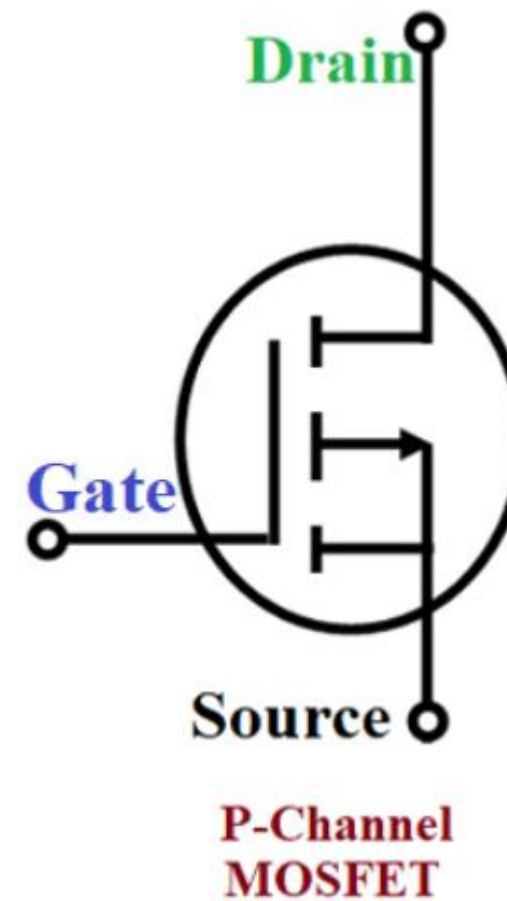


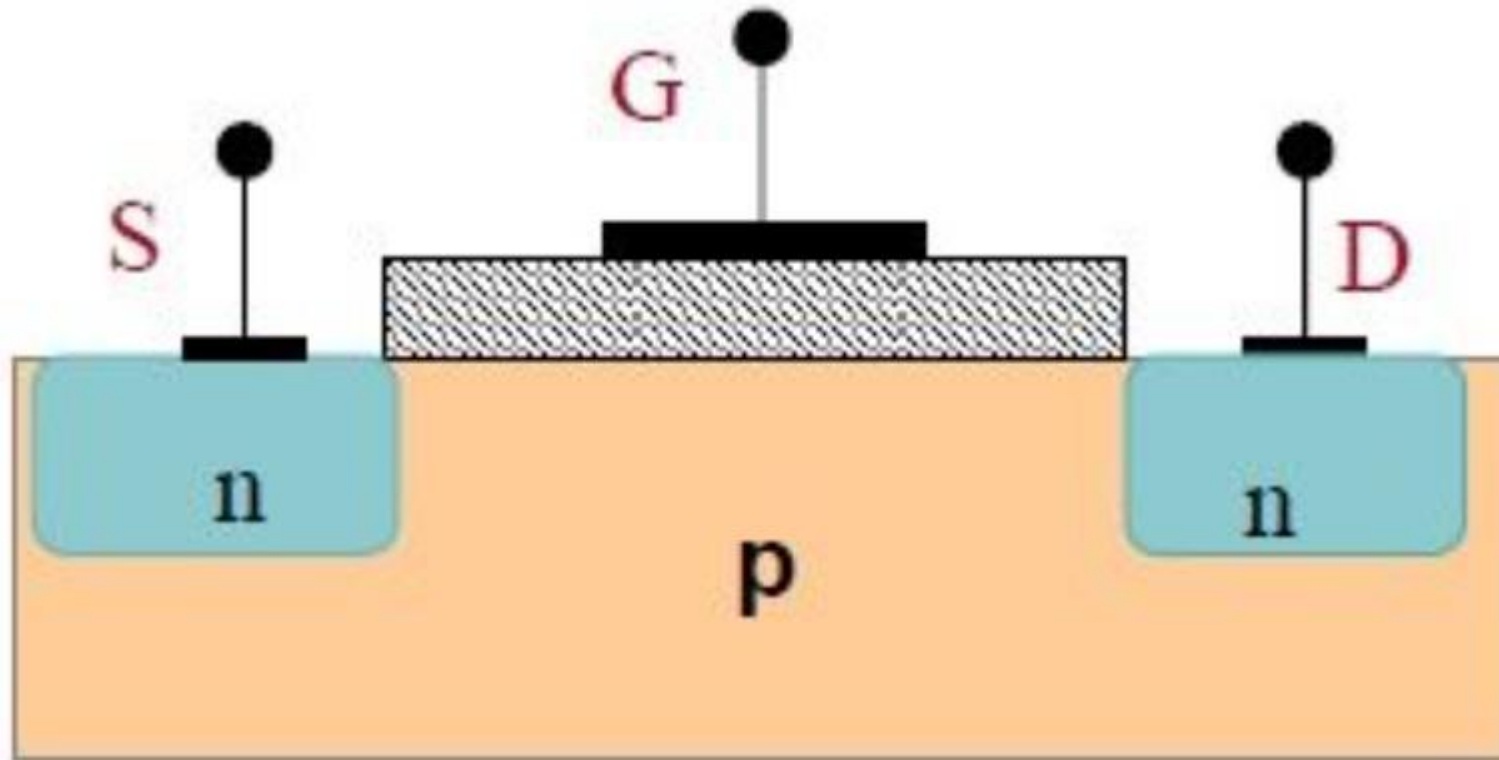


CMOS: complementary metal-oxide semiconductor




n-MOS

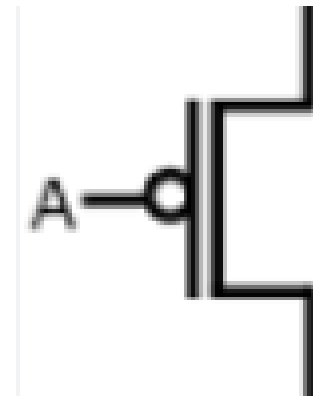


p-MOS

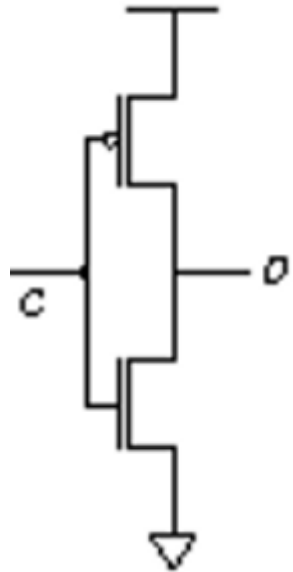

**NOT Gate
CMOS Design**

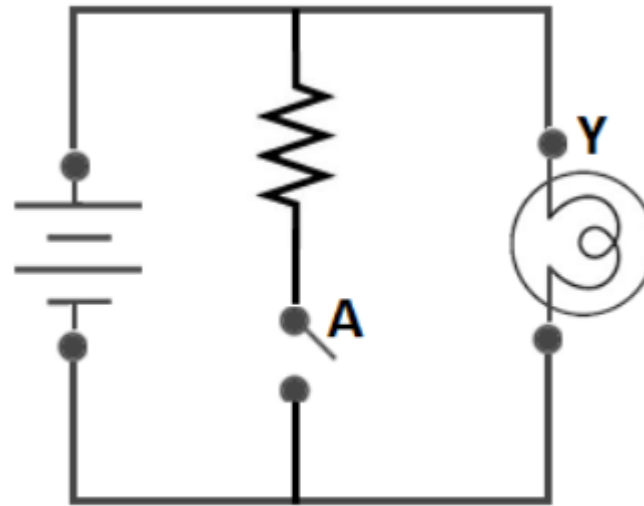


Electrical Circuit

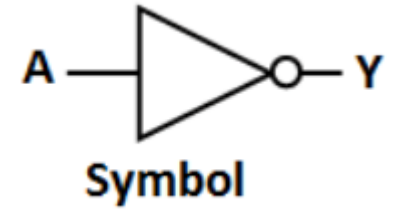


Symbol

A	$Y = \bar{A}$
0	1
1	0


Truth Table

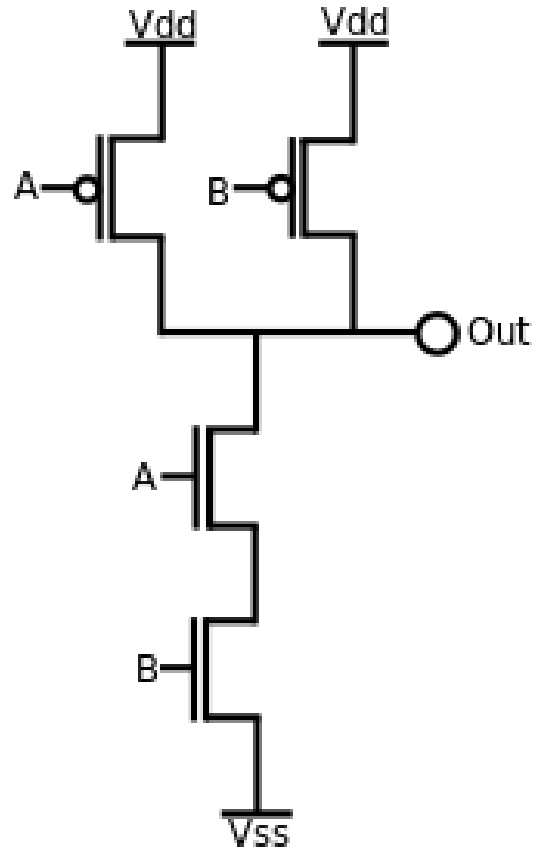

**NAND
CMOS Design**

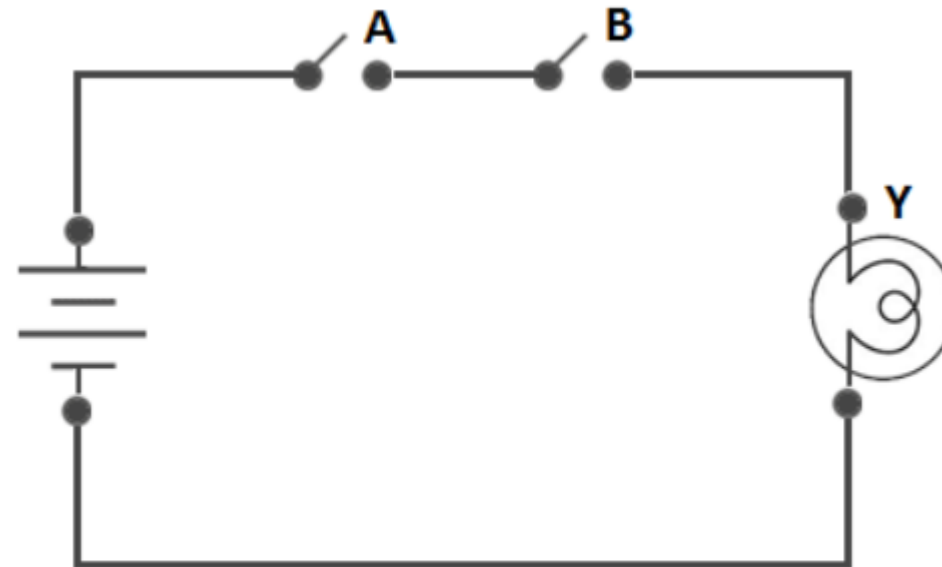


Electrical Circuit

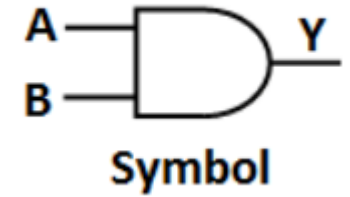


Symbol

A	B	$Y = A * B$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table

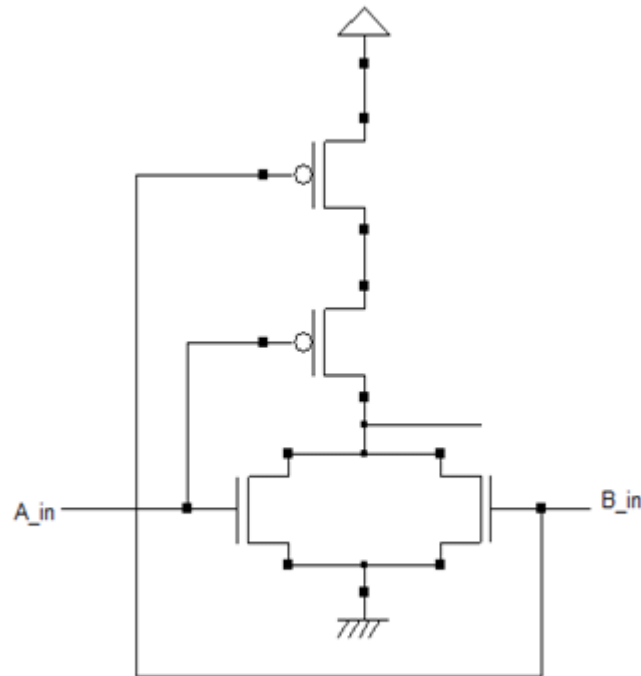

**NOR
CMOS Design**

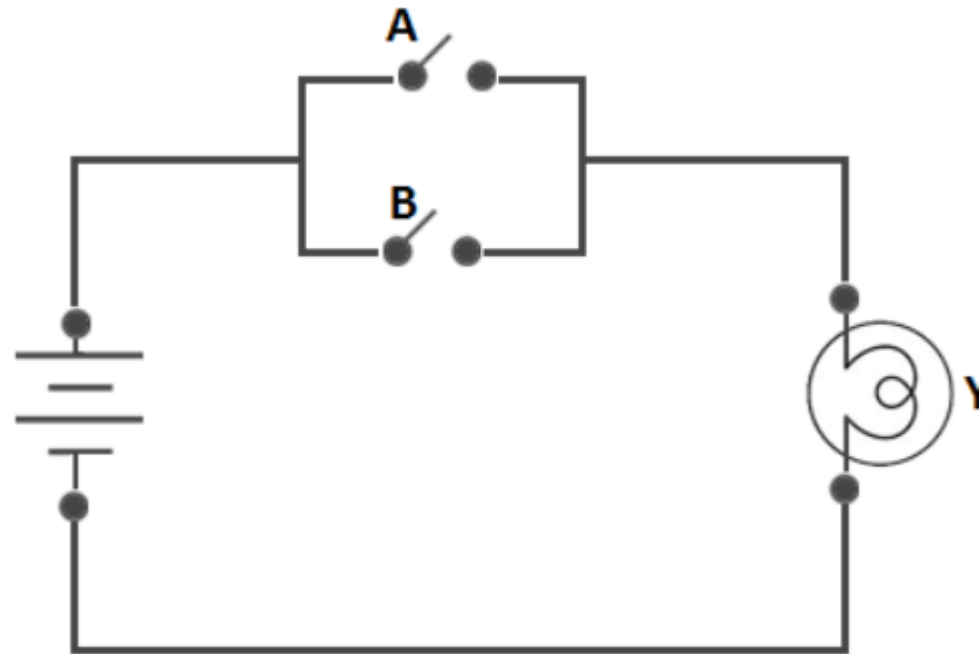




Electrical Circuit





Symbol


A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1


Truth Table

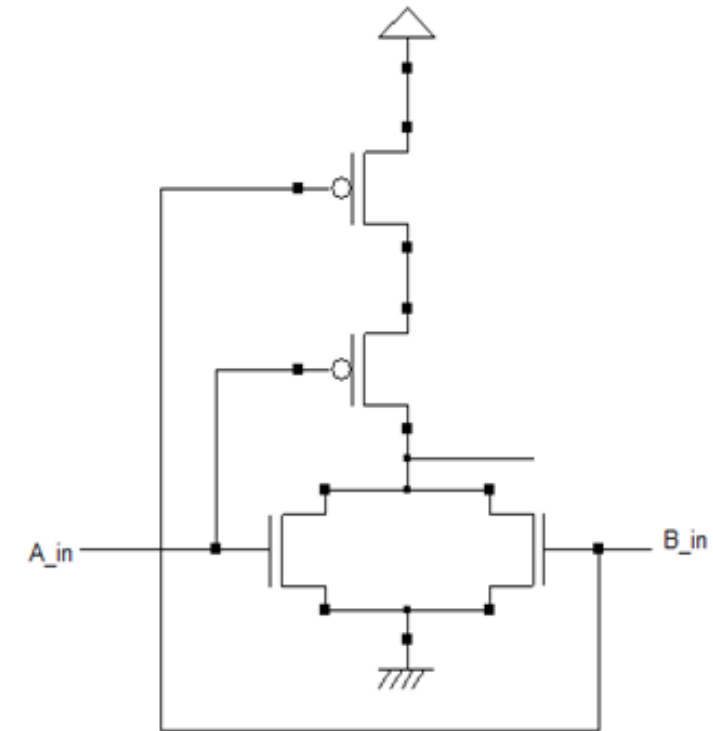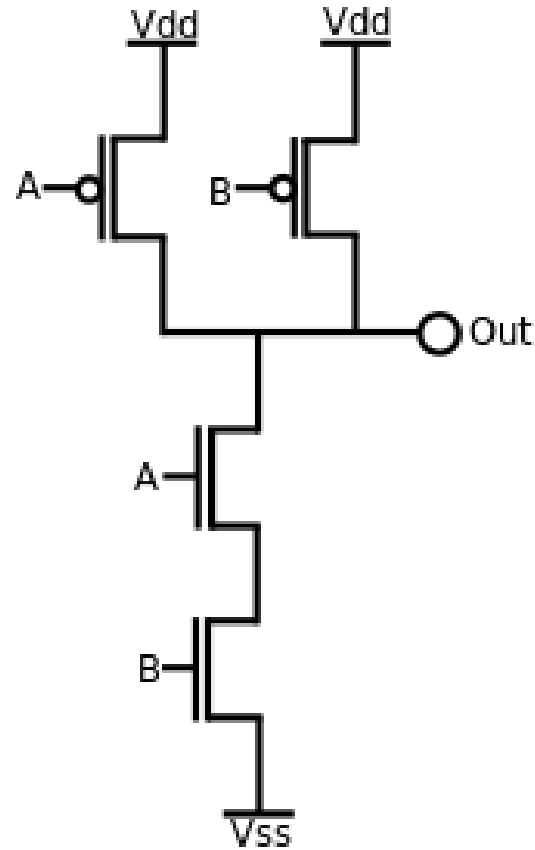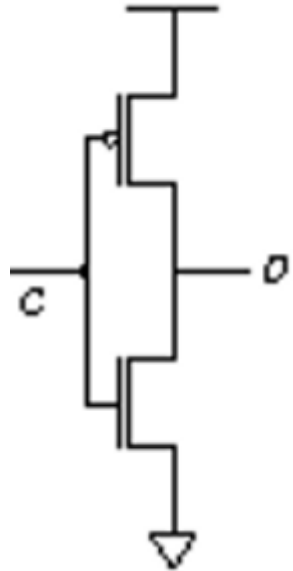

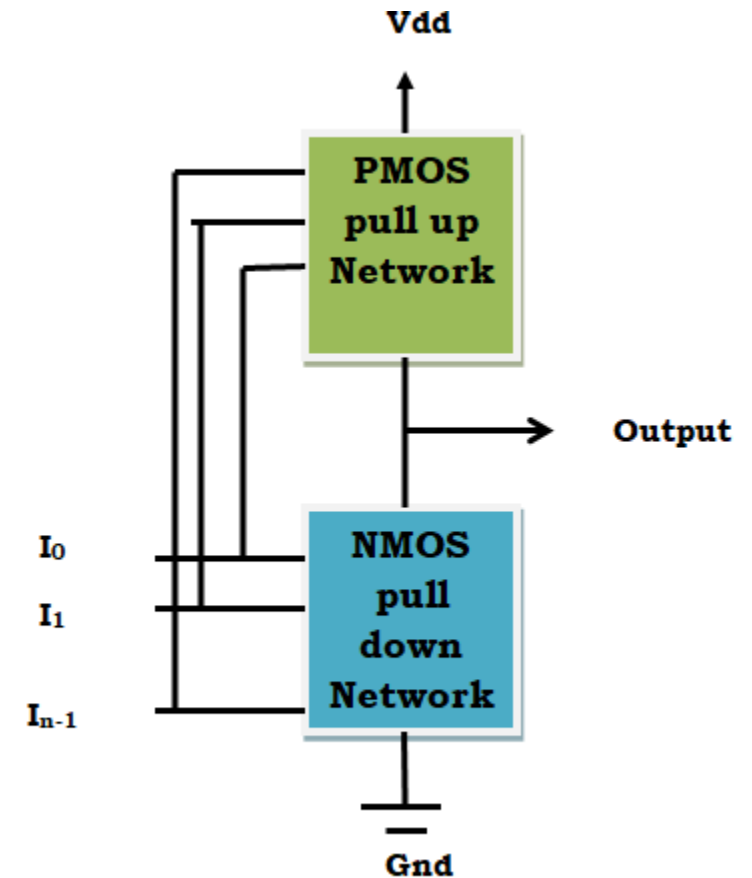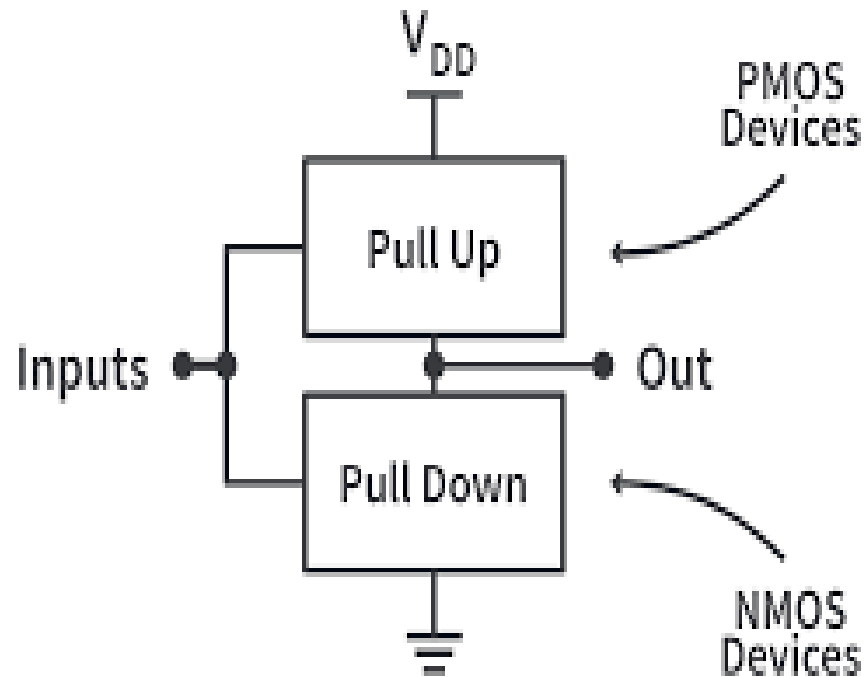

$$\text{OUT} = D + A \cdot (B + C)$$

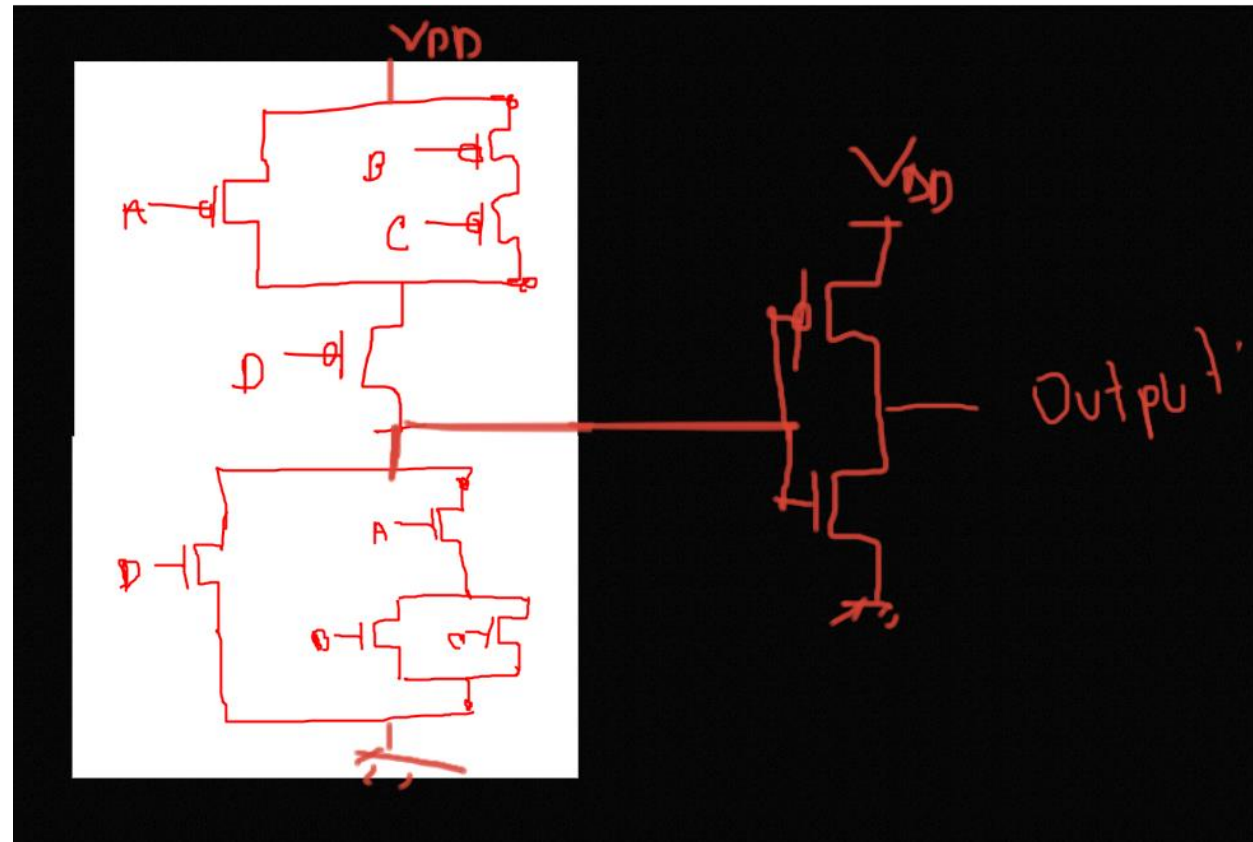

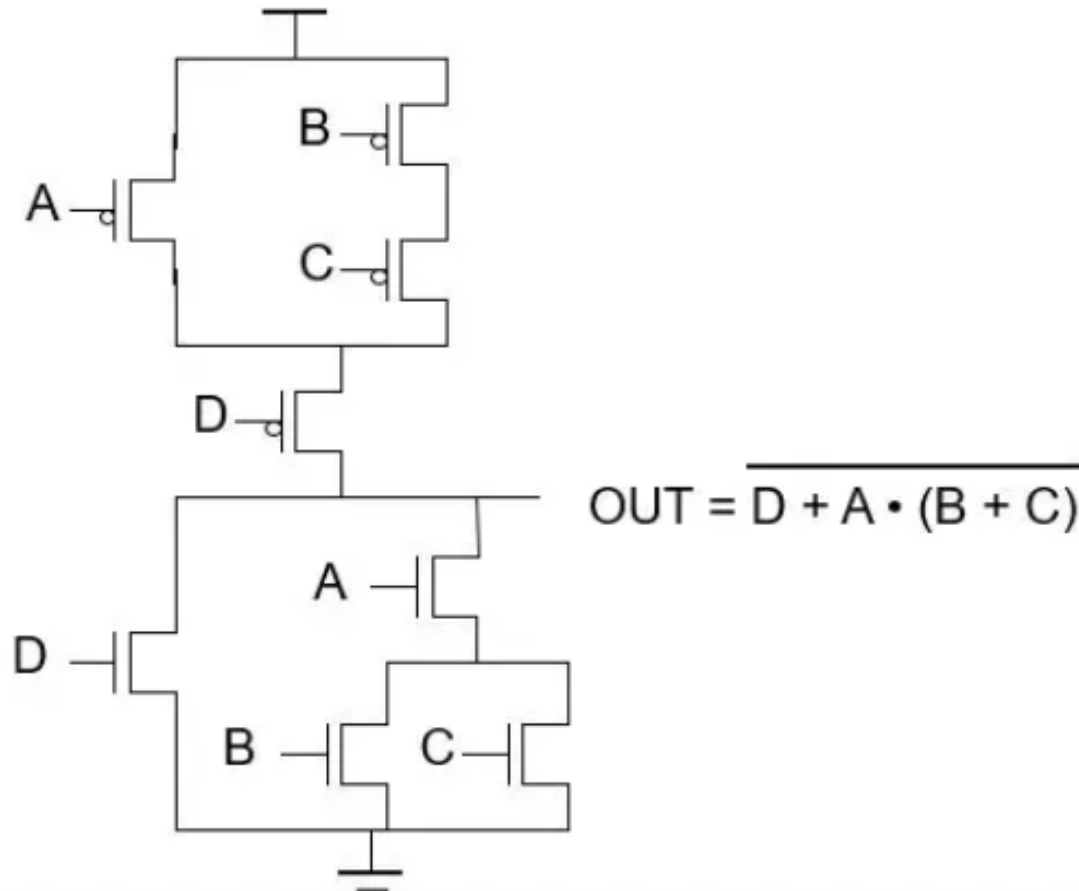

Thank You