

Course Instructor



Md. Saklain Morshed
Lecturer, EEE
Green University of Bangladesh

JK Flip Flop Review

Counter Design Steps

Design of MOD-4 Synchronous Up-Counter


Design of Synchronous Random Counter

Video Link of this Lecture:

Will be Updated After the Class

Q(t)	J	K	Q(t+1)
0	0	0	0 (Hold)
0	0	1	0 (reset)
0	1	0	1 (Set)
0	1	1	1 (Toggle)
1	0	0	1 (Hold)
1	0	1	0 (reset)
1	1	0	1 (Set)
1	1	1	0 (Toggle)

Characteristics Table

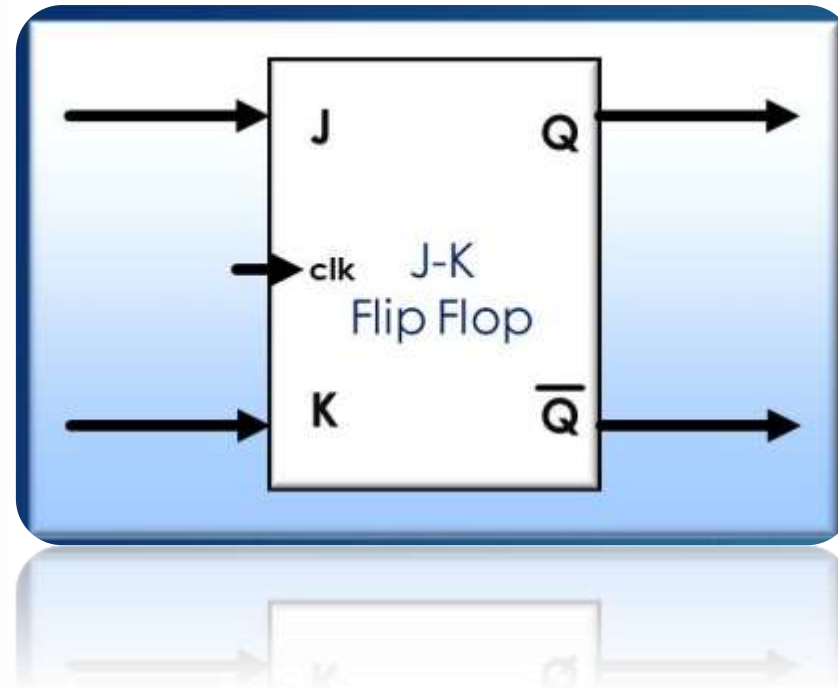


J	K	Q
0	0	Hold
0	1	0 (Reset)
1	0	1 (SET)
1	1	Toggle

Truth Table

Present Q_n	Next State Q_{n+1}	J	K
0	0		
0	1		
1	0		
1	1		

Excitation Table

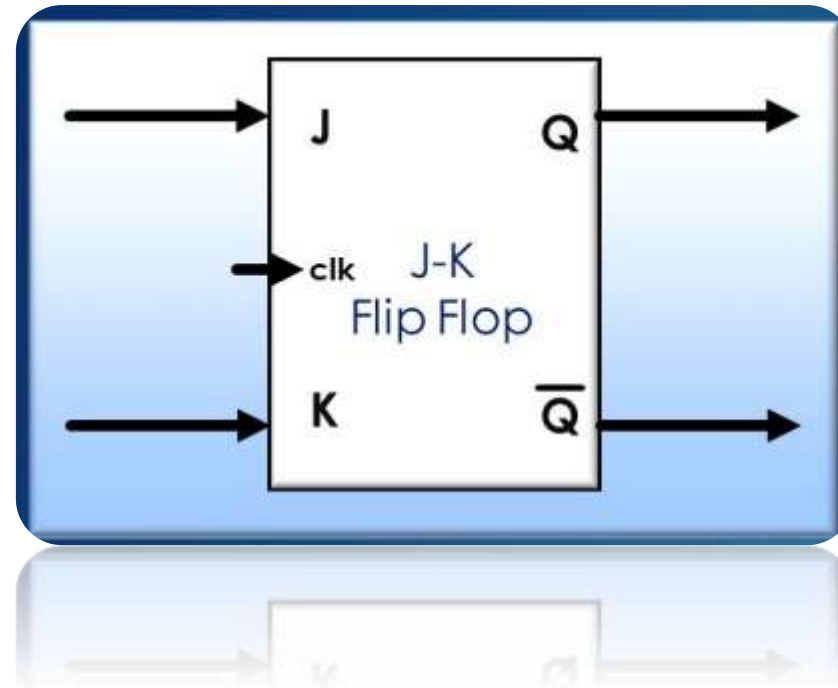


J	K	Q
0	0	Hold
0	1	0 (Reset)
1	0	1 (SET)
1	1	Toggle

Truth Table


MOD-4 synchronous down-counter



MOD-4 synchronous up-counter

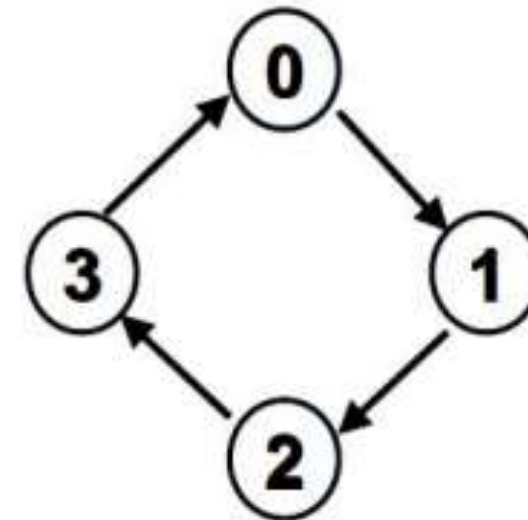

State Diagram

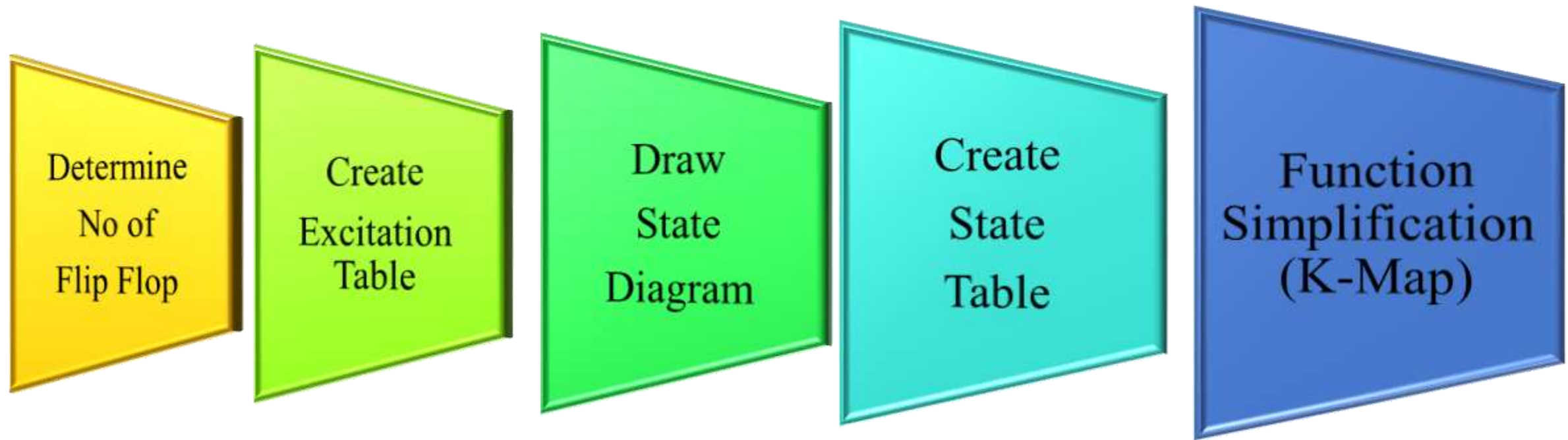

Determine
No of
Flip Flop

No of FF = 2

0, 1, 2, 3, 0, 1, 2, 3, 0, 1, 2, 3,

Maximum Digit

3

Covert Binary


11

Maximum 2 Bit is Needed

Create
Excitation Table


Present Q_n	Next State Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Excitation Table

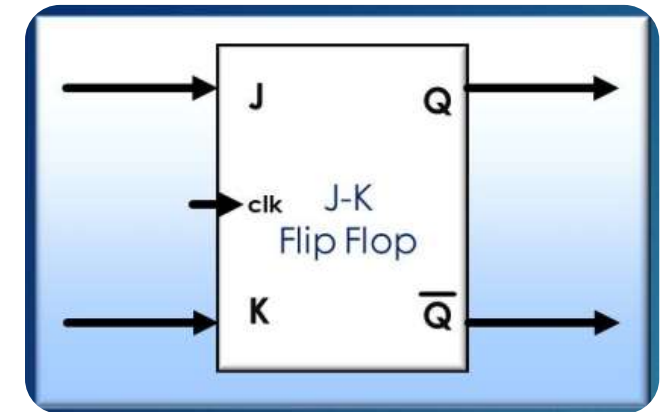


J	K	Q
0	0	Hold
0	1	0 (Reset)
1	0	1 (SET)
1	1	Toggle

Draw
State Diagram

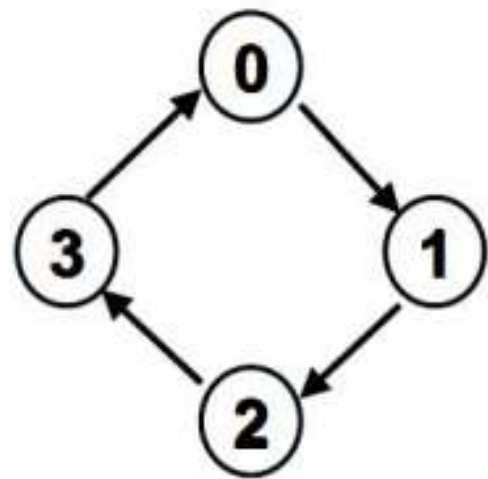

→
Binary

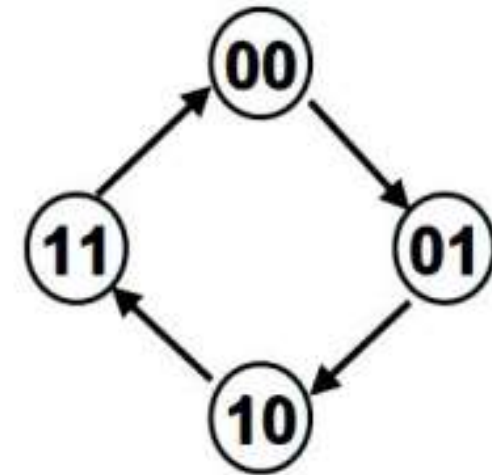

Create
State Table

Present State	
B	A
0	0
0	1
1	0
1	1

Next State	
B	A
0	1
1	0
1	1
0	0


Input, J K			
J _B K _B		J _A K _A	
0	X	1	X
1	X	X	1
X	0	1	X
X	1	X	1

Present Q _n	Next State Q _{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Excitation Table

Function Simplification (K-Map)

Input, J K			
J_B	K_B	J_A	K_A
0	X	1	X
1	X	X	1
X	0	1	X
X	1	X	1

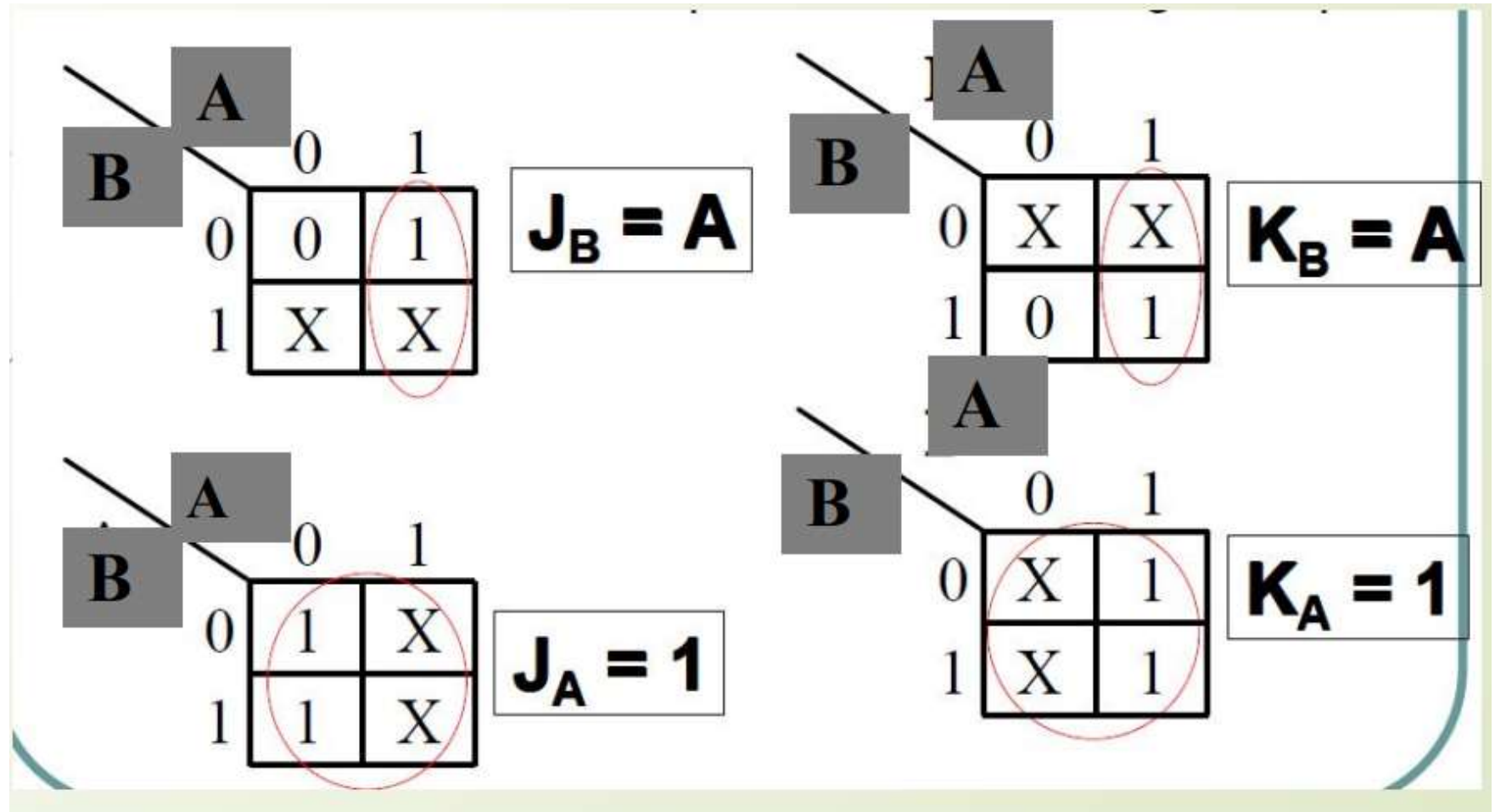

Circuit Connection

B \ A	A		
	0	1	
B	0	0	1
	1	X	X

$J_B = A$

B \ A	A		
	0	1	
B	0	X	X
	1	0	1


$K_B = A$

B \ A	A		
	0	1	
B	0	1	X
	1	1	X

$J_A = 1$

B \ A	A		
	0	1	
B	0	X	1
	1	X	1

$K_A = 1$

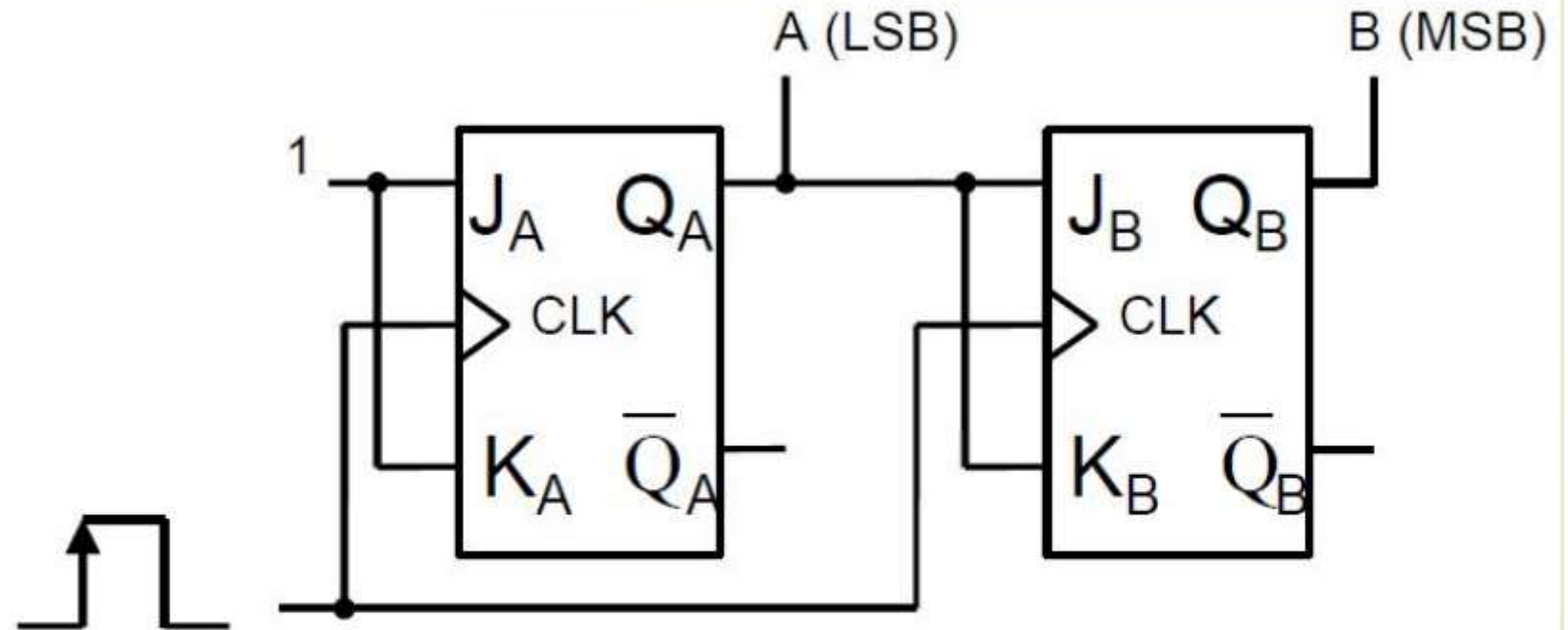


(MOD-4 synchronous up-counter)

Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JKFlip Flop negative triggered by showing:

n = 3 bit = 3 Flip Flop

Present Q _n	Next State Q _{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

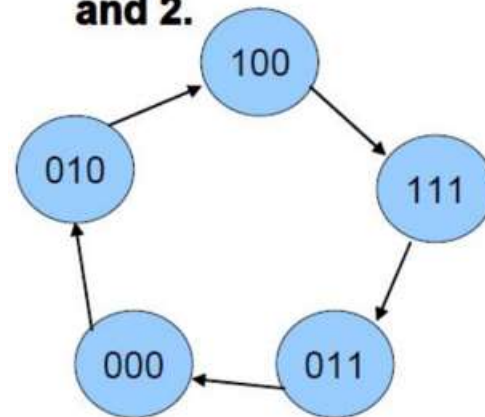**State Transation
Diagram, to count 4, 7, 3, 0
and 2.**



Deci mal	Present State			Next State			JC	KC	JB	KB	JA	KA
	QC	QB	QA	QC	QB	QA						
4	1	0	0	1	1	1	x	0	1	x	1	x
7	1	1	1	0	1	1	x	1	x	0	x	0
3	0	1	1	0	0	0	0	x	x	1	x	1
0	0	0	0	0	1	0	0	x	1	x	0	x
2	0	1	0	1	0	0	1	x	x	1	0	x

Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JKFlip Flop negative triggered by showing:

Decimal	Present State			Next State			JC	KC	JB	KB	JA	KA
	QC	QB	QA	QC	QB	QA						
4	1	0	0	1	1	1	x	0	1	x	1	x
7	1	1	1	0	1	1	x	1	x	0	x	0
3	0	1	1	0	0	0	0	x	x	1	x	1
0	0	0	0	0	1	0	0	x	1	x	0	x
2	0	1	0	1	0	0	1	x	x	1	0	x

K Map for JA

C B A

4=100

5=101

7=111

6=110

$J_A = C = Q_C$

C	BA			
	0	1	3	2
0	0	X	X	0
1	1	X	X	X

Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JKFlip Flop negative triggered by showing:

Decimal	Present State			Next State			JC	KC	JB	KB	JA	KA
	QC	QB	QA	QC	QB	QA						
4	1	0	0	1	1	1	x	0	1	x	1	x
7	1	1	1	0	1	1	x	1	x	0	x	0
3	0	1	1	0	0	0	0	x	x	1	x	1
0	0	0	0	0	1	0	0	x	1	x	0	x
2	0	1	0	1	0	0	1	x	x	1	0	x

K Map for K_A

C B A

0=000

1=001

3=011

2=010

$$K_A = \overline{C} = \overline{Q_C}$$

C	BA			
	0	1	3	2
0	X	X	1	X
4	X	X	0	X

Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JKFlip Flop negative triggered by showing:

Decimal	Present State			Next State			JC	KC	JB	KB	JA	KA
	QC	QB	QA	QC	QB	QA						
4	1	0	0	1	1	1	x	0	1	x	1	x
7	1	1	1	0	1	1	x	1	x	0	x	0
3	0	1	1	0	0	0	0	x	x	1	x	1
0	0	0	0	0	1	0	0	x	1	x	0	x
2	0	1	0	1	0	0	1	x	x	1	0	x

K Map for JB

JB=1

		BA			
C		1	X	X	X
	0				
		1	X	X	X
	4				
		5	X	X	X
		7			
			6		

Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JKFlip Flop negative triggered by showing:

Decimal	Present State			Next State			JC	KC	JB	KB	JA	KA
	QC	QB	QA	QC	QB	QA						
4	1	0	0	1	1	1	x	0	1	x	1	x
7	1	1	1	0	1	1	x	1	x	0	x	0
3	0	1	1	0	0	0	0	x	x	1	x	1
0	0	0	0	0	1	0	0	x	1	x	0	x
2	0	1	0	1	0	0	1	x	x	1	0	x

K Map for K_B

C B A

0=000

1=001

3=011

2=010

$$K_B = \overline{C} = \overline{Q_C}$$

C	BA			
	0	1	3	2
0	X	X	1	1
1	X	X	0	X

Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JKFlip Flop negative triggered by showing:

K Map for K_c

C B A

2=010

3=011

7=111

6=110

$$K_c = B = Q_B$$

C	BA			
	0	1	3	2
0	X	X	X	X
1	0	X	1	X

K Map for J_c

C B A


2=010

6=110

$$J_c = \overline{B}\overline{A} = Q_B\overline{Q_A}$$

C	BA			
	0	1	3	2
0	0	X	0	1
1	X	X	X	X

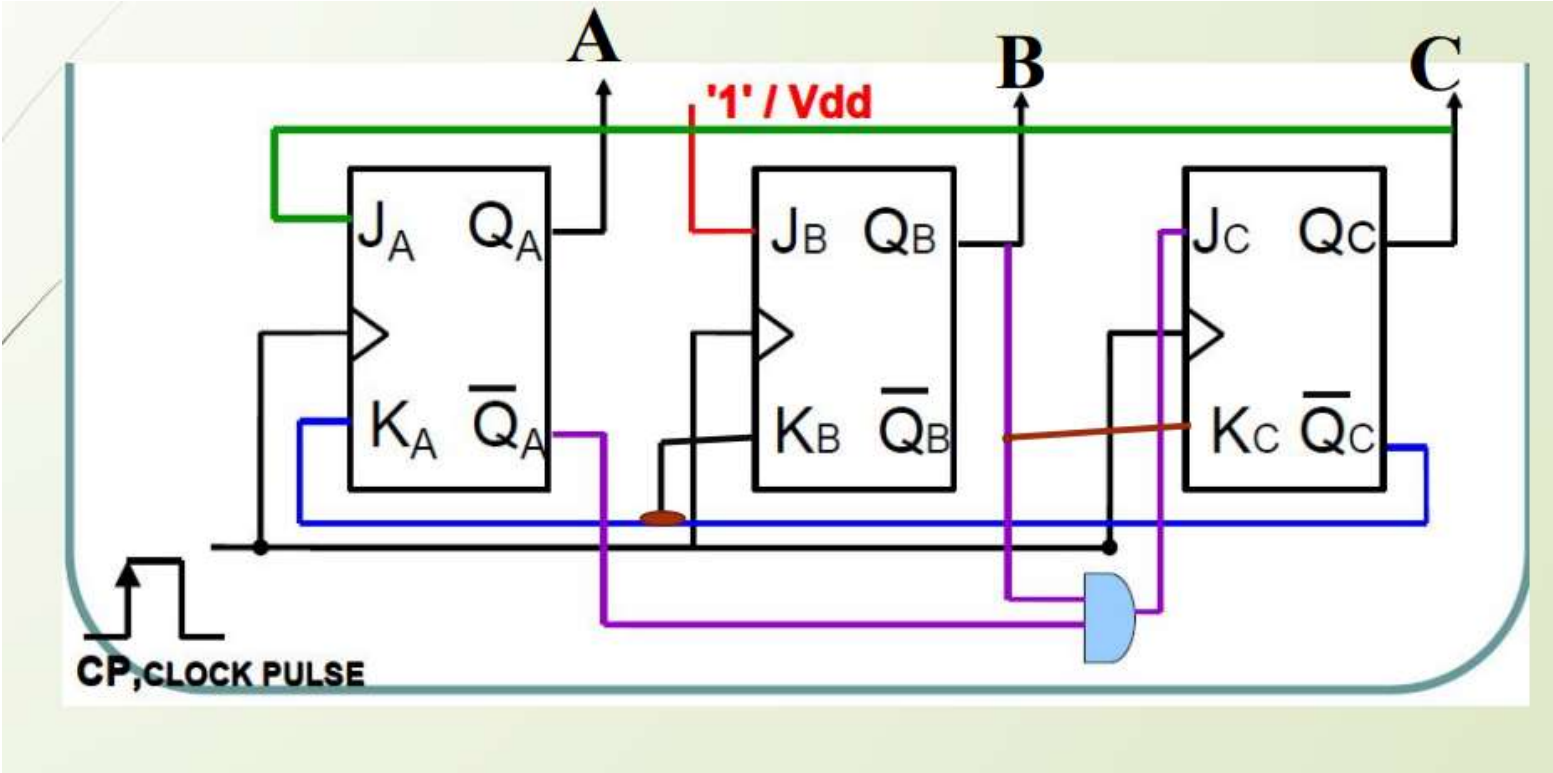Design a Synchronous Counter to Count 4,7,3,0 and 2 respectively using JKFlip Flop negative triggered by showing:



Thank You