

Course Instructor



Md. Saklain Morshed
Lecturer, EEE
Green University of Bangladesh

MOSFET Current Voltage Characteristics

Modes of Operation



MOSFET Related Important Equations

MOSFET Related Ckt Problem


Video Link of this Lecture:

- Lecture-1: <https://youtu.be/7CrDQtUQbwA>
- Lecture-2: <https://youtu.be/DSuMV-5ANr8>
- Lecture-3: <https://youtu.be/JE-UHIML3jw>

OHM'S LAW

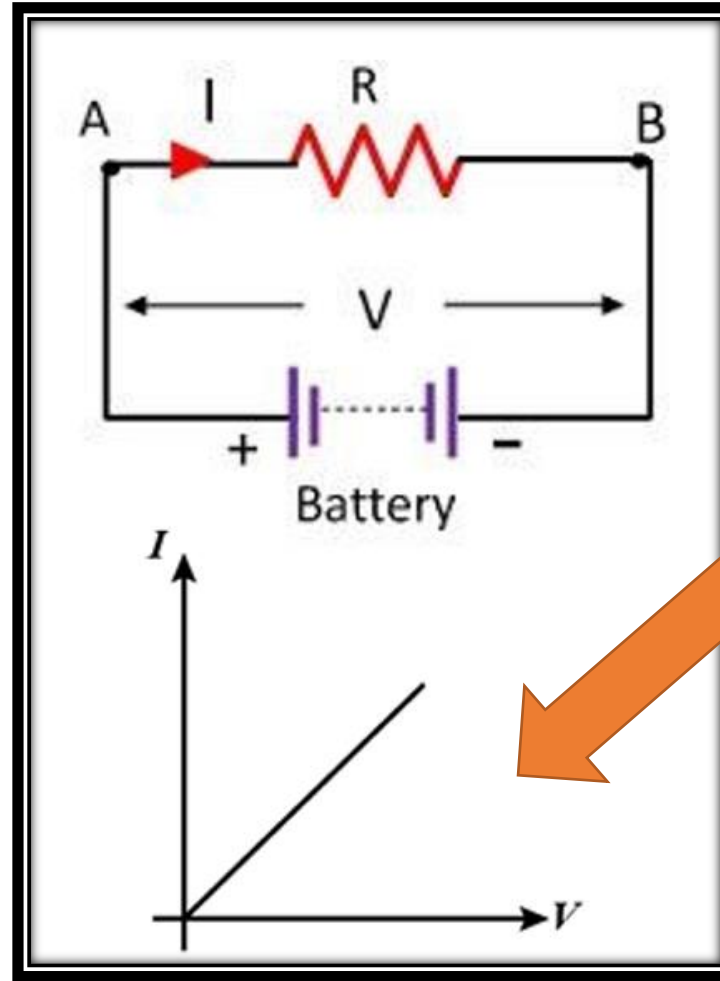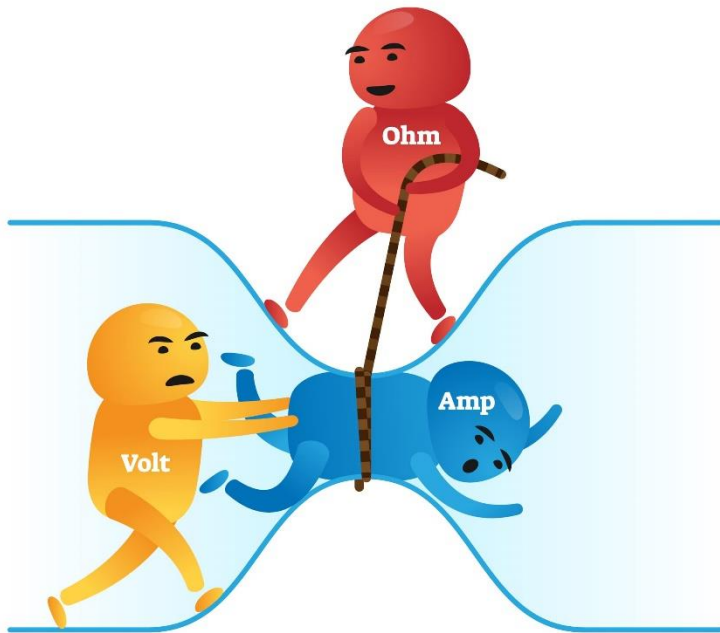


$$V = I * R$$

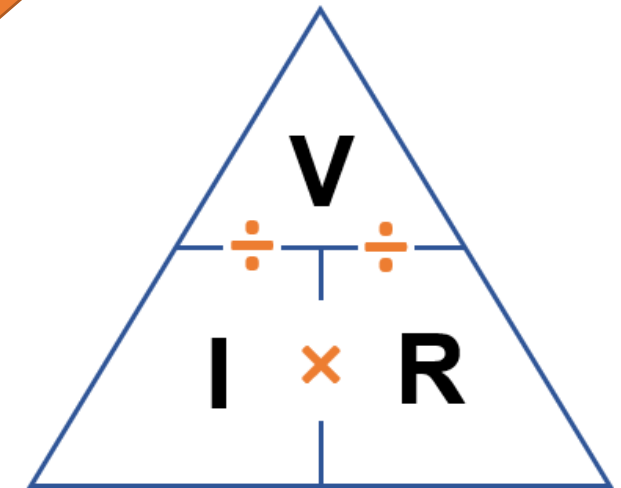

$$I_D = \frac{W}{L} \cdot \mu_n C_{ox} \left[V_{GS} - \frac{V_{DS}}{2} - V_T \right] \cdot V_{DS}$$

 L μ_n V_{GS} W V_{DS} V_T I_D C_{ox}
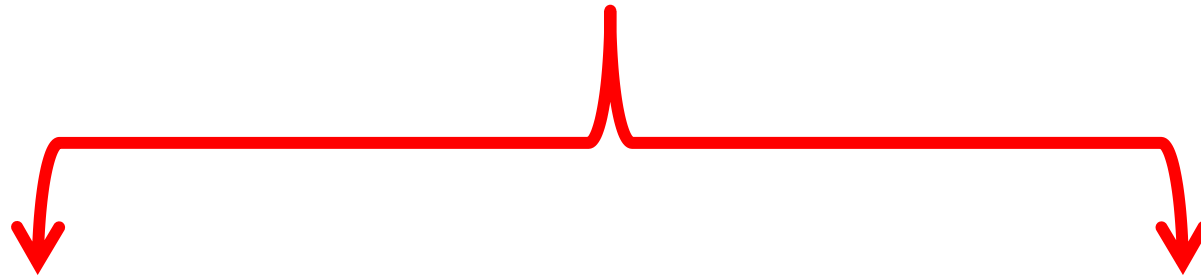
$$I_D = \frac{W}{L} \cdot \mu_n C_{ox} \left[V_{GS} - \frac{V_{DS}}{2} - V_T \right] \cdot V_{DS}$$



$$V_{DS} < V_{GS} - V_T$$

linear or triode


$$V_{DS} \geq V_{GS} - V_T$$

Saturation

v_{DS} is kept small

$$V_{DS} \ll V_{GS} - V_T$$
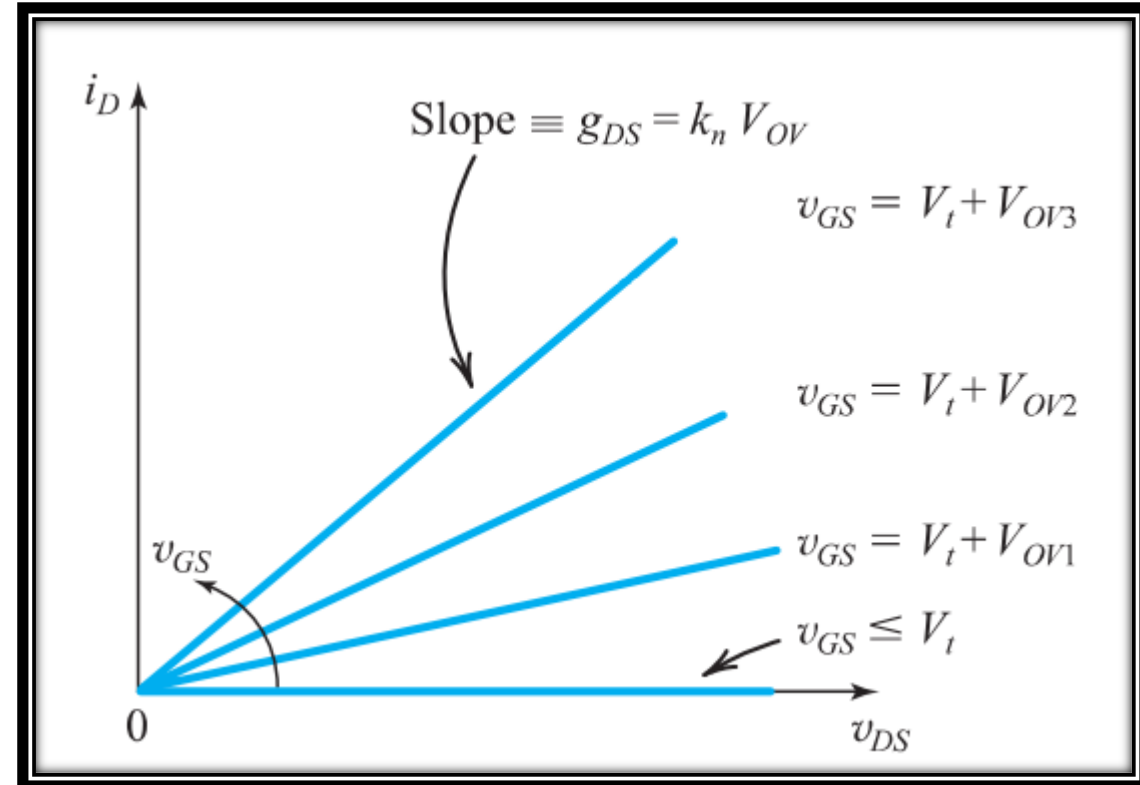
$$I_D = \frac{W}{L} \cdot \mu_n C_{ox} \left[V_{GS} - \frac{V_{DS}}{2} - V_T \right] \cdot V_{DS}$$




$$V_{DS} \geq V_{GS} - V_T$$

$$I_D = \frac{W}{L} \cdot \mu_n C_{ox} \left[V_{GS} - \frac{V_{DS}}{2} - V_T \right] \cdot V_{DS}$$



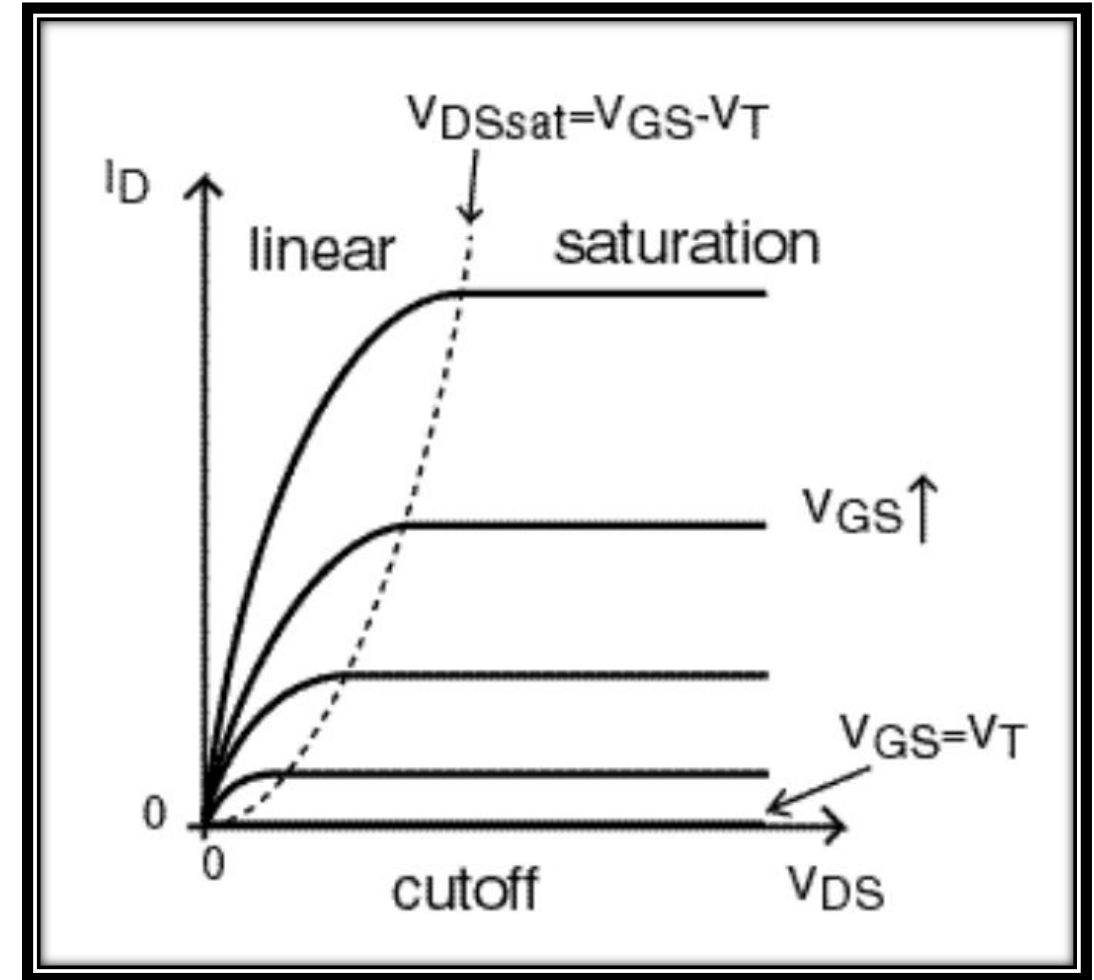
$$I_{Dsat} = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2$$




Operating mode	Voltages	
Cut-off	$V_{GS} < V_{th}$	
Linear	$V_{GS} > V_{th}$	$V_{DS} < V_{GS} - V_{th}$
Saturation	$V_{GS} > V_{th}$	$V_{DS} \geq V_{GS} - V_{th}$

Operating mode	Voltages		Drain current
Cut-off	$V_{GS} < V_{th}$		$I_{DS} = 0$
Linear	$V_{GS} > V_{th}$	$V_{DS} < V_{GS} - V_{th}$	$I_D = \frac{W}{L} \cdot \mu_n C_{ox} \left[V_{GS} - \frac{V_{DS}}{2} - V_T \right] \cdot V_{DS}$
Saturation	$V_{GS} > V_{th}$	$V_{DS} \geq V_{GS} - V_{th}$	$I_{Dsat} = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2$

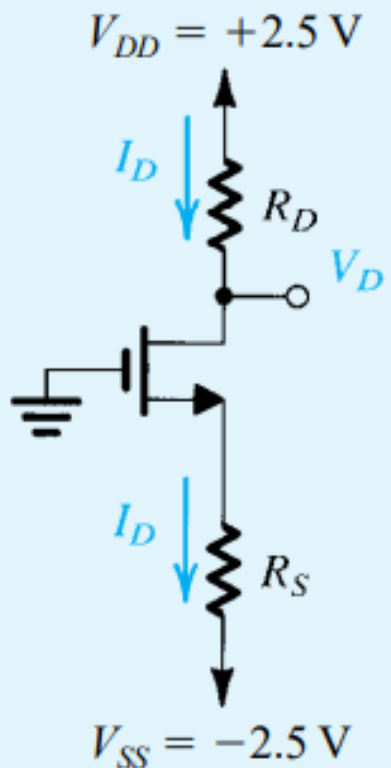Design the circuit of Fig. 5.21, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4$ mA and $V_n = +0.5$ V. The NMOS transistor has $V_t = 0.7$ V, $\mu_n C_{ox} = 100$ $\mu\text{A}/\text{V}^2$, $L = 1$ μm , and $W = 32$ μm .



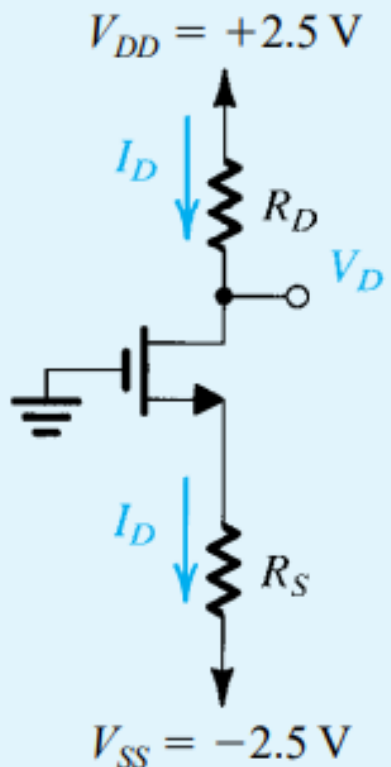Design the circuit of Fig. 5.21, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D = 0.4 \text{ mA}$ and $V_D = +0.5 \text{ V}$. The NMOS transistor has $V_t = 0.7 \text{ V}$, $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $L = 1 \mu\text{m}$, and $W = 32 \mu\text{m}$.



$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.5}{0.4} = 5 \text{ k}\Omega$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{OV}^2$$


$$400 = \frac{1}{2} \times 100 \times \frac{32}{1} V_{OV}^2$$

$$V_{OV} = 0.5 \text{ V}$$

$$V_{GS} = V_t + V_{OV} = 0.7 + 0.5 = 1.2 \text{ V}$$

$$R_S = \frac{V_S - V_{SS}}{I_D} = \frac{-1.2 - (-2.5)}{0.4} = 3.25 \text{ k}\Omega$$

Design the circuit in Fig. 5.23 to establish a drain voltage of 0.1 V. What is the effective resistance between drain and source at this operating point? Let $V_{tn} = 1$ V and $k'_n(W/L) = 1$ mA/V².

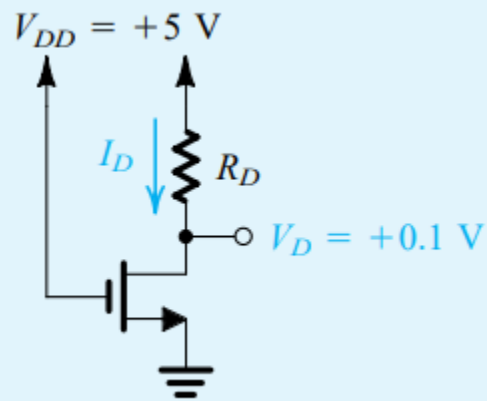**Solution**

Since the drain voltage is lower than the gate voltage by 4.9 V and $V_{tn} = 1$ V, the MOSFET is operating in the triode region. Thus the current I_D is given by

$$I_D = k'_n \frac{W}{L} \left[(V_{GS} - V_{tn}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$I_D = 1 \times \left[(5 - 1) \times 0.1 - \frac{1}{2} \times 0.01 \right]$$


$$= 0.395 \text{ mA}$$

The required value for R_D can be found as follows:

$$R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{5 - 0.1}{0.395} = 12.4 \text{ k}\Omega$$

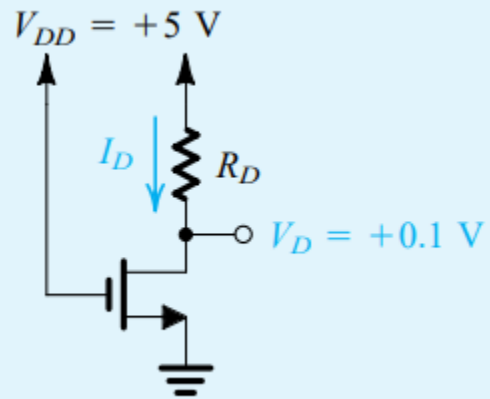Design the circuit in Fig. 5.23 to establish a drain voltage of 0.1 V. What is the effective resistance between drain and source at this operating point? Let $V_{tn} = 1$ V and $k'_n(W/L) = 1$ mA/V².



D5.9 For the circuit in Fig. E5.9, find the value of R that results in $V_D = 0.8$ V. The MOSFET has $V_{tn} = 0.5$ V, $\mu_n C_{ox} = 0.4$ mA/V², $W/L = \frac{0.72 \mu\text{m}}{0.18 \mu\text{m}}$, and $\lambda = 0$.

Ans. 13.9 k Ω

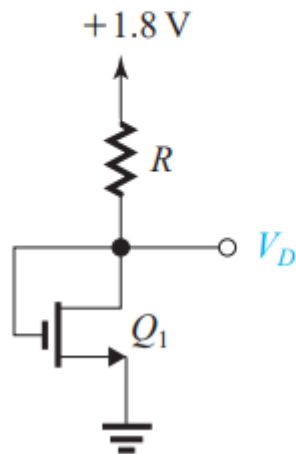


Figure E5.9

Thank You