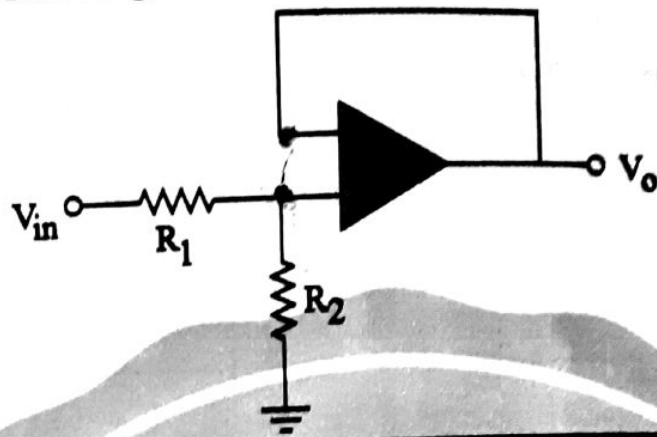



Find the output of the following circuits:



on:

$$V_o = \frac{R_2}{R_1 + R_2} \times V_{in}$$

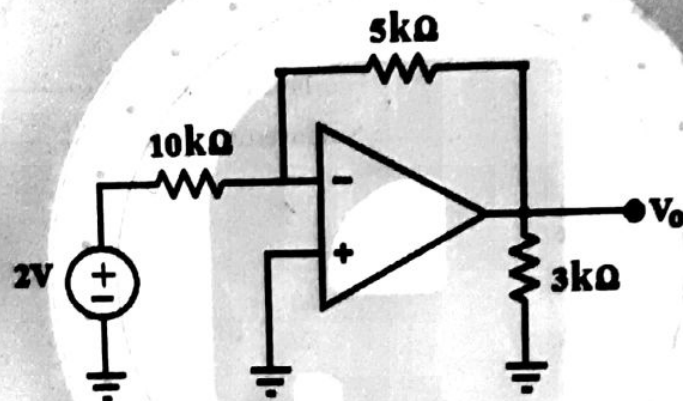
Find the gain in the following op-amp circuit.



ution:

$$\text{gain} = \frac{V_o}{V_i} = -\frac{R_f}{R_i} = -\frac{5}{10} = -\frac{1}{2}$$


Find V_o in the following:

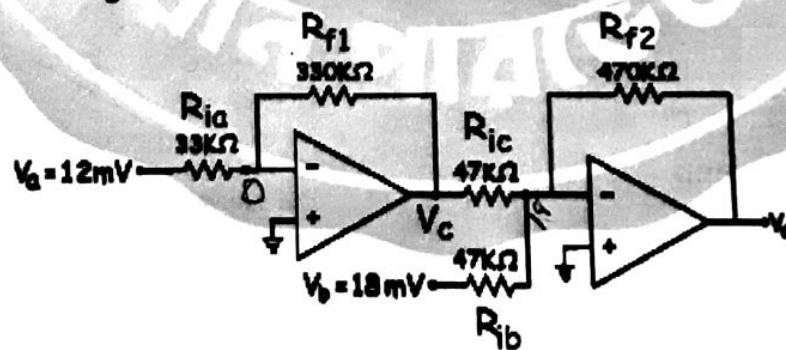

$$V_c = -\frac{R_{f1}}{R_{ia}} \times V_a = -\frac{330}{33} \times 12 = -120 \text{ mV}$$

$$V_o = -\frac{R_{f2}}{R_{ic}} \times V_c - \frac{R_{f2}}{R_{ib}} \times V_b = -\frac{470}{47} \times (-120) - \frac{470}{47} \times 18 = 1020 \text{ mV}$$

নিম্নের সার্কিট হতে V_1 ও V_2 বের কর।

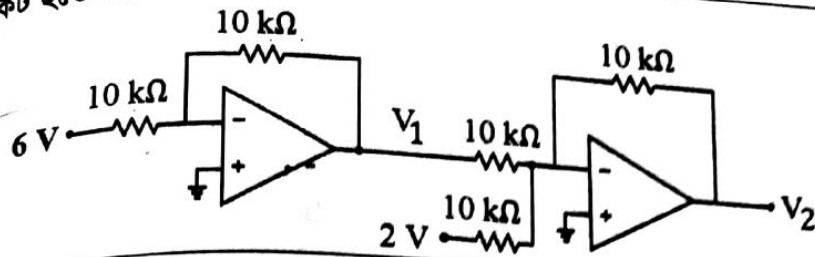


PG
(S)

Solution:

$$V_1 = -\frac{10}{10} \times 6 = -6V$$


$$V_2 = -\frac{10}{10} \times V_1 - \frac{10}{10} \times 2 = -V_1 - 2 = -(-6) - 2 = 4V \text{ Ans.}$$

Find V_o

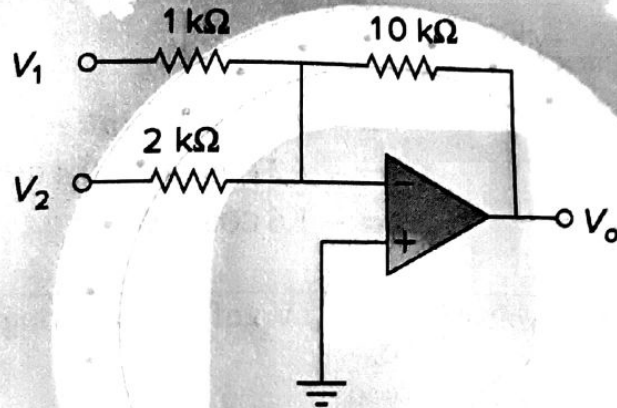

$$-\frac{R_f}{R_1} \times V_1 - \frac{R_f}{R_2} \times V_2 = -\frac{10}{1} \times V_1 - \frac{10}{2} \times V_2 = -10V_1 - 5V_2 \text{ Ans.}$$

Find i_o in the following ideal op-amp.

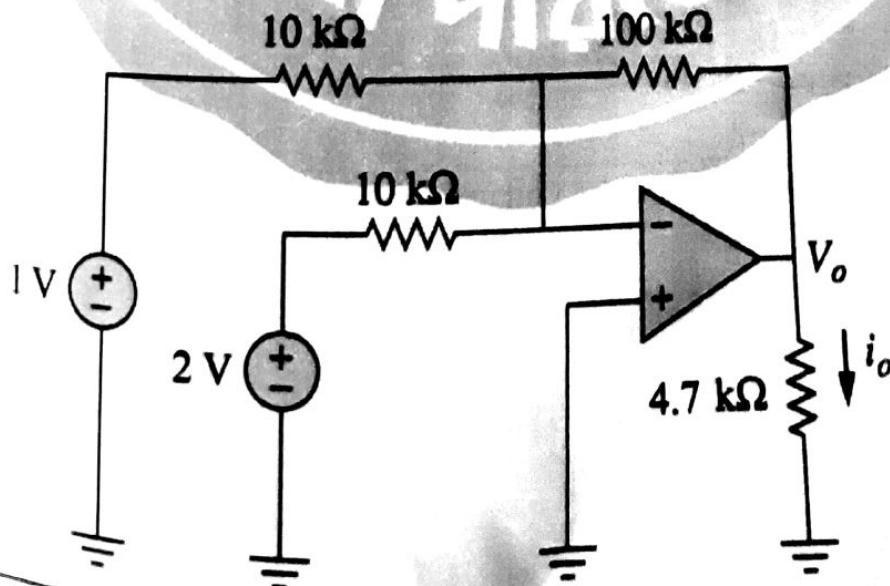


Solution:

$$V_0 = -\frac{R_f}{R_1} \times V_1 - \frac{R_f}{R_2} \times V_2 = -\frac{100}{10} \times 1 - \frac{100}{10} \times 2 = -10 - 20 = -30$$

$$I_0 = \frac{V_0}{4.7} = -\frac{30}{4.7} = -6.383 \text{ mA} \quad \text{Ans.}$$

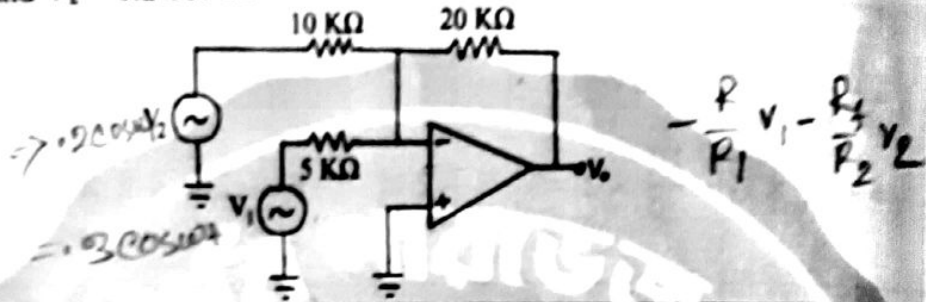
Calculate the output voltage of the following amplifier. Input signals are $V_1 = 0.3 \cos \omega t$ and $V_2 = 0.2 \cos \omega t$



Solution:

$$\begin{aligned} V_0 &= -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = -20 \times \left(\frac{V_1}{5} + \frac{V_2}{10} \right) = -4V_1 - 2V_2 \\ &= -4 \times 0.3 \cos \omega t - 2 \times 0.2 \cos \omega t \\ &= -1.2 \cos \omega t - 0.4 \cos \omega t \\ &= -1.6 \cos \omega t \end{aligned}$$

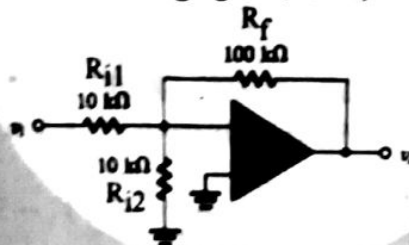Assuming ideal op amp find the voltage gain (V_0/V_i) of the following circuit:




Solution:

$$V_0 = -\frac{R_f}{R_{i1}} \times V_i - \frac{R_f}{R_{i2}} \times 0 = -\frac{100}{10} \times V_i - 0 = -10V_i$$

$$\therefore \frac{V_0}{V_i} = -10 \quad \text{Ans.}$$

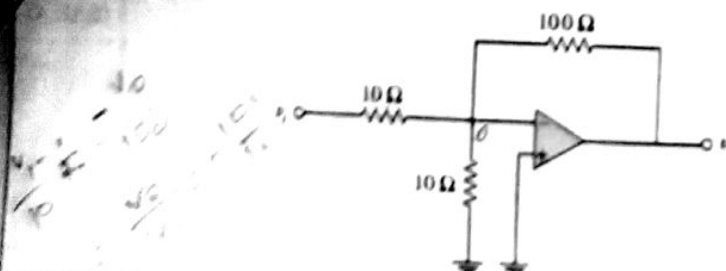For the following op amp circuit, find the voltage gain v_0/v_i . [Similar to Exercise 6.23, Sedilcu]




olution:

$$V_0 = -\frac{R_f}{R_1} \times V_1 - \frac{R_f}{R_2} \times V_2 = -\frac{100}{10} \times 1 - \frac{100}{10} \times 2 = -10 -$$

$$i_0 = \frac{V_0}{4.7} = -\frac{30}{4.7} = -6.383 \text{ mA} \quad \text{Ans.}$$

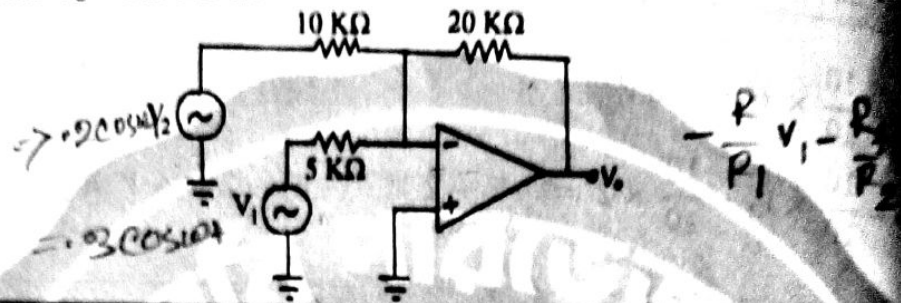
Calculate the output voltage of the following amplifier. Input signals are $V_1 = 0.3 \cos \omega t$ and $V_2 = 0.2 \cos \omega t$



olution:

$$\begin{aligned} V_0 &= -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = -20 \times \left(\frac{V_1}{5} + \frac{V_2}{10} \right) = -4V_1 - 2V_2 \\ &= -4 \times 0.3 \cos \omega t - 2 \times 0.2 \cos \omega t \\ &= -1.2 \cos \omega t - 0.4 \cos \omega t \\ &= -1.6 \cos \omega t \end{aligned}$$

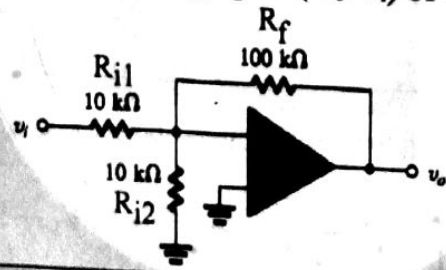Assuming ideal op amp find the voltage gain (V_0/V_i) of the following circuit




olution:

$$\begin{aligned} V_0 &= -\frac{R_{f2}}{R_{i1}} \times V_i - \frac{R_f}{R_{i2}} \times 0 = -\frac{100}{10} \times V_i - 0 = -10V_i \\ \therefore \frac{V_0}{V_i} &= -10 \quad \text{Ans.} \end{aligned}$$

For the following op amp circuit, find the voltage gain v_o/v_i . [Similar to Exercise 5.23, Sadiku]

9

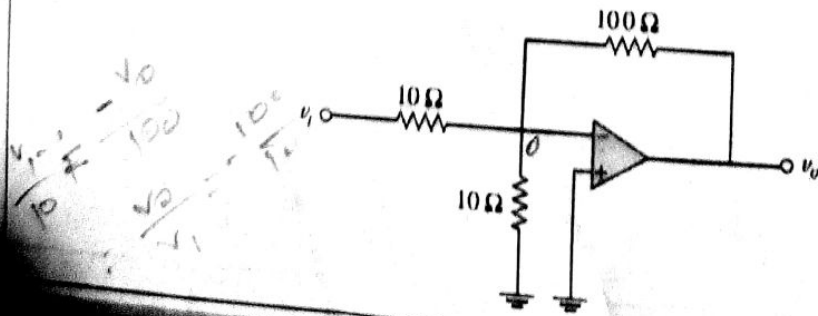


tion:

lying nodal analysis at non-inverting terminal,

$$\frac{v_i - 0}{10} = \frac{0 - 0}{10} + \frac{0 - v_0}{100}$$


$$\frac{v_i}{10} = \frac{-v_0}{100}$$
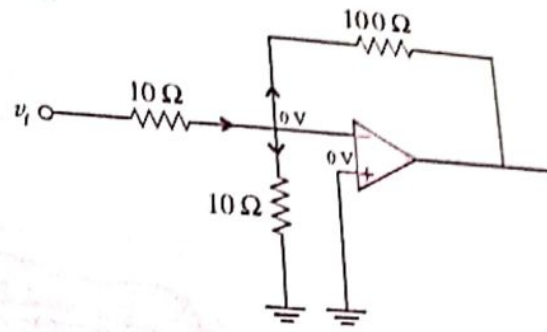
$$\frac{v_0}{v_i} = \frac{-100}{10} = -10 \text{ Ans.}$$




Draw a 3 input summing amplifier using Op-Amp.

BT

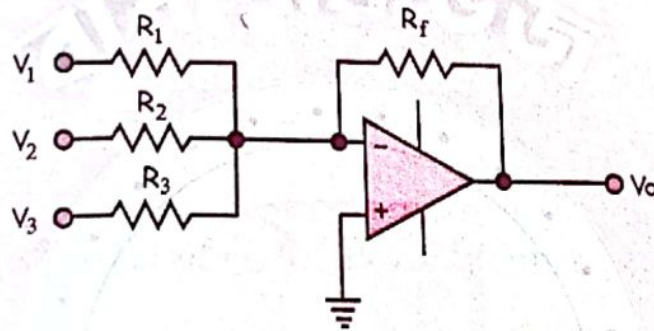

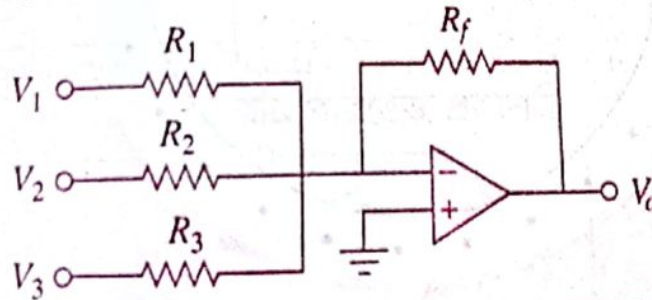
চের সার্কিটে, $V_1 = 1 \text{ V}$, $V_2 = 2 \text{ V}$, $V_3 = 3 \text{ V}$, $R_1 = 500 \text{ k}\Omega$, $R_2 = R_3 = R_f = 1 \text{ M}\Omega$ ল V_0 এর মান কত?



$$V_0 = -\frac{R_f}{R_1} \times V_1 - \frac{R_f}{R_2} \times V_2 - \frac{R_f}{R_3} \times V_3$$

$$= -\frac{1}{0.5} \times 1 - \frac{1}{1} \times 2 - \frac{1}{1} \times 3 = -2 - 2 - 3 = -7 \text{ V Ans.}$$

nd V_0 of the following circuit.

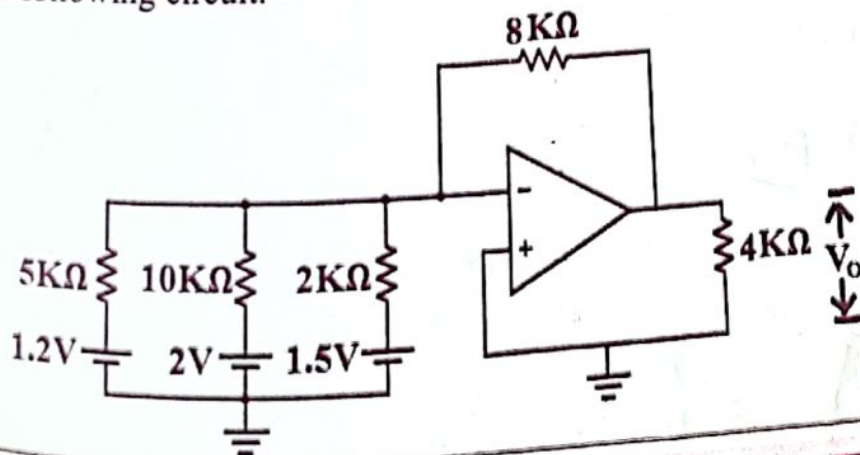


একমাত্র প্রতিস্থান

Solution:

$$V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) = -8 \times \left(\frac{1.2}{5} + \frac{2}{10} + \frac{1.5}{2} \right) = -9.52 \text{ V}$$

13

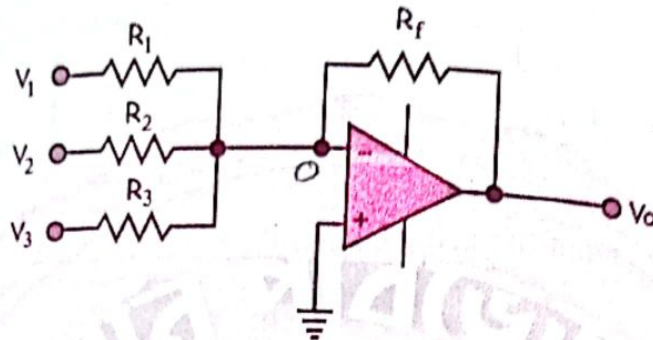In the following op-amp, $V_1 = 50 \sin(1000t) \text{ mV}$, $V_2 = 10 \sin(3000t) \text{ mV}$, $V_3 = 0$ and $R_1 = 33 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_3 = 10 \text{ k}\Omega$ and $R_f = 330 \text{ k}\Omega$. Find V_0 .




Solution:

$$\begin{aligned} V_0 &= -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3 \\ &= -\frac{330}{33} \times (50 \sin 1000t) - \frac{330}{10} \times (10 \sin 3000t) - \frac{330}{10} \times 0 \\ &= -500 \sin 1000t - 330 \sin 3000t \quad \text{Ans.} \end{aligned}$$

14

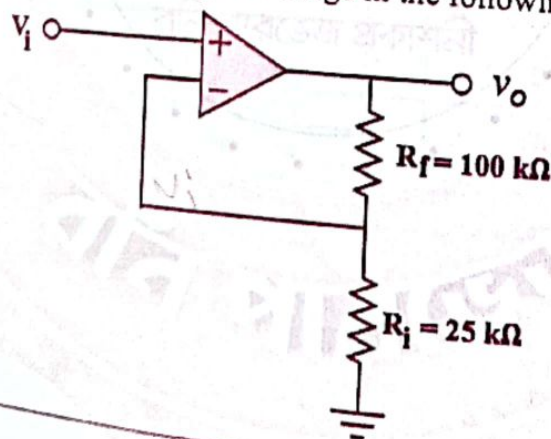Find the ratio of Input voltage and Output Voltage in the following operational amplifier




Solution:

$$\begin{aligned} V_0 &= \left(1 + \frac{R_f}{R_i} \right) \times V_i \\ \Rightarrow \frac{V_0}{V_i} &= \left(1 + \frac{R_f}{R_i} \right) = \left(1 + \frac{100}{25} \right) = 5 \\ \Rightarrow \frac{V_i}{V_0} &= \frac{1}{5} \end{aligned}$$

Ans.

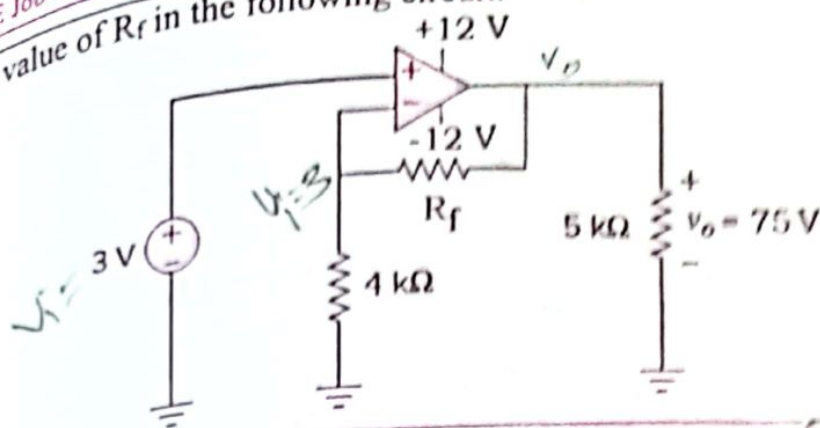Find the value of R_f in the following circuit.




olution:

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_i$$

$$R_f = \left(\frac{V_o}{V_i} - 1\right) R_i = \left(\frac{75}{3} - 1\right) \times 4000 = 96000 \Omega = 96 \text{ k}\Omega \quad \text{Ans}$$

Find V_o using superposition theorem

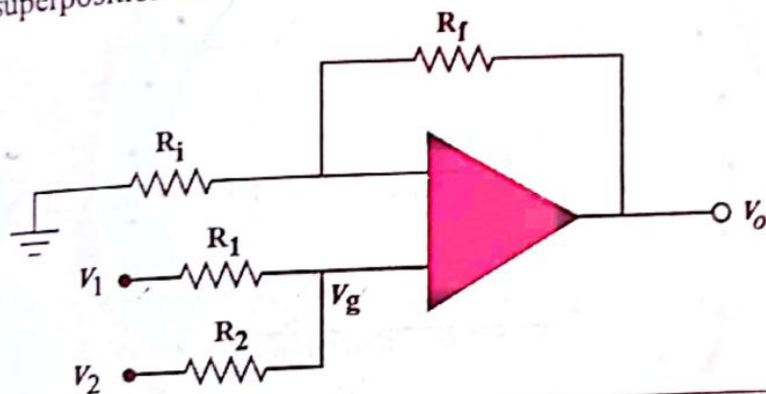

ution:

When only V_1 is active and $V_2 = 0$, then applying voltage divider rule:

$$V_g = V_{g1} = \frac{R_2}{R_1 + R_2} \times V_1$$

$$\therefore V_o = V_{o1} = \left(1 + \frac{R_f}{R_i}\right) \times V_{g1} = \left(1 + \frac{R_f}{R_i}\right) \times \frac{R_2}{R_1 + R_2} \times V_1$$

When only V_2 is active and $V_1 = 0$, then applying voltage divider rule:


$$V_g = V_{g2} = \frac{R_1}{R_1 + R_2} \times V_2$$

$$\therefore V_o = V_{o2} = \left(1 + \frac{R_f}{R_i}\right) \times V_{g2} = \left(1 + \frac{R_f}{R_i}\right) \times \frac{R_1}{R_1 + R_2} \times V_2$$

Applying superposition theorem (both V_1 and V_2 is active)

$$V_o = V_{o1} + V_{o2} = \left(1 + \frac{R_f}{R_i}\right) \times \frac{R_2}{R_1 + R_2} \times V_1 + \left(1 + \frac{R_f}{R_i}\right) \times \frac{R_1}{R_1 + R_2} \times V_2 \quad \text{Ans.}$$

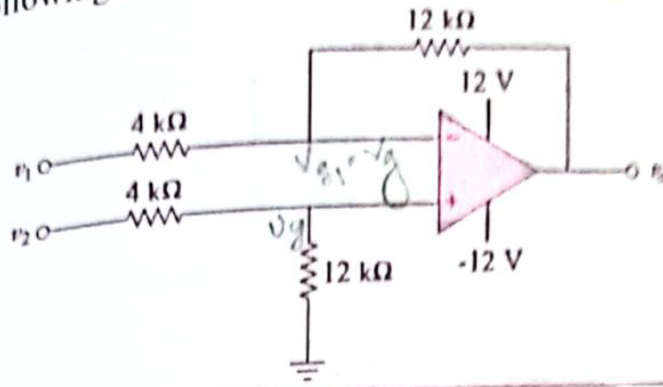Find V_0 in the following circuit when $V_1 = V_2 = 0.5$ V.




Solution:

$$V_g = \frac{12}{4 + 12} \times 0.5 = 0.375 \text{ V}$$

At V_g node,

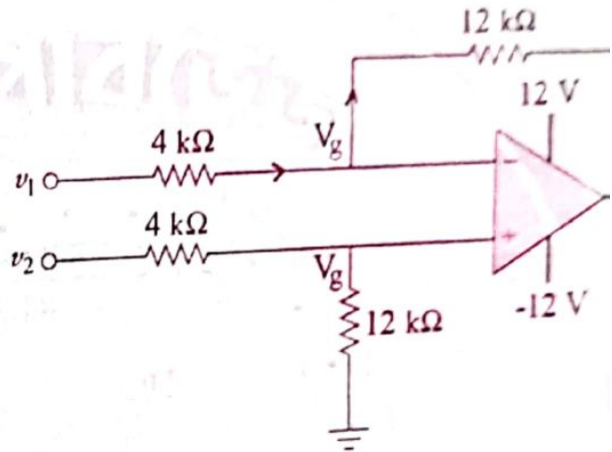
$$\begin{aligned} \frac{V_1 - V_g}{4} &= \frac{V_g - V_0}{12} \\ \Rightarrow 3(V_1 - V_g) &= V_g - V_0 \\ \Rightarrow V_0 &= V_g - 3V_1 + 3V_g \\ &= 4V_g - 3V_1 \\ &= 4 \times 0.375 - 3 \times 0.5 \\ &= 4 \times 0.375 - 3 \times 0.5 \\ &= 0 \text{ V Ans.} \end{aligned}$$



Alternate Solution:

$$V_0 = \left(1 + \frac{R_f}{R_i}\right) V_g - \frac{R_f}{R_i} V_1 = \left(1 + \frac{12}{4}\right) \times 0.375 - \frac{12}{4} \times 0.5 = 1.5 - 1.5 = 0 \text{ V}$$

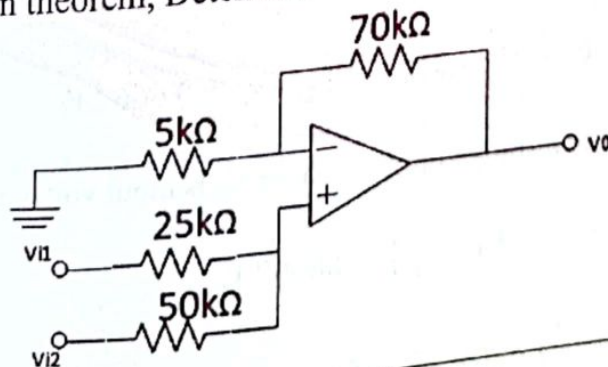
Using superposition theorem, Determine the V_0 of the Op-Amp:



Solution:

$$V_0 = \left\{ \left(1 + \frac{70}{5}\right) \times \frac{50}{25 + 50} \times V_{11} \right\} + \left\{ \left(1 + \frac{70}{5}\right) \times \frac{25}{25 + 50} \times V_{12} \right\} = 10 V_{11} + 5 V_{12}$$

20

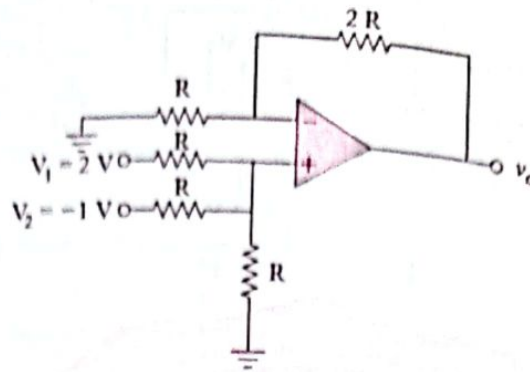Find V_o in the following circuit:


Solution:

$$V_{o1} = \left(1 + \frac{2R}{R}\right) \times V_1' = \left(1 + \frac{2R}{R}\right) \times \frac{R \parallel R}{R + R \parallel R} \times V_1 = (1 + 2) \times \frac{R}{3R} \times 2$$

$$V_{o2} = \left(1 + \frac{2R}{R}\right) \times V_2' = \left(1 + \frac{2R}{R}\right) \times \frac{R \parallel R}{R + R \parallel R} \times V_2 = (1 + 2) \times \frac{R}{3R} \times (-1)$$

$$V_o = V_{o1} + V_{o2} = 2 + (-1) = 1 \text{ V} \quad \text{Ans.}$$

21

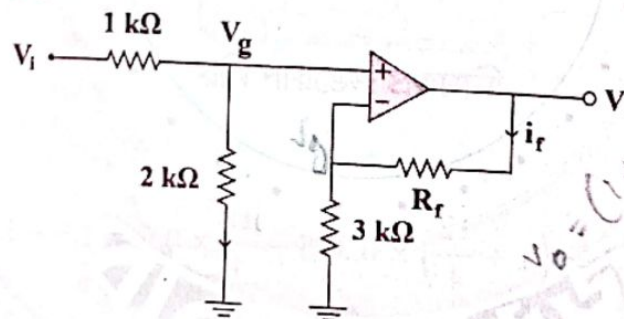Find R_f for having gain 5.

Solution:

Using voltage divider rule, $V_g = \frac{2}{2+1} \times V_i = 0.6667 V_i$

The circuit is like non-inverting amplifier where V_g is input voltage.

$$\therefore V_o = \left(1 + \frac{R_f}{R_1}\right) \times V_g = \left(1 + \frac{R_f}{3}\right) \times 0.6667 V_i$$


$$\Rightarrow \frac{V_o}{V_i} = \left(1 + \frac{R_f}{3}\right) \times 0.6667 = 5$$

[Given, gain $\frac{V_o}{V_i}$]

$$\Rightarrow R_f = \left(\frac{5}{0.6667} - 1\right) \times 3 = 19.5 \text{ k}\Omega$$

Ans.


নীচের সার্কিটে V_0 এর মান কত?

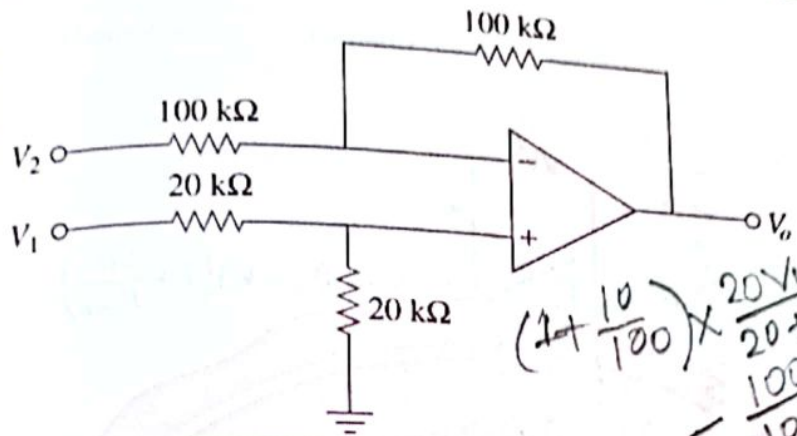

TGTDCL-13
(SAE)

$$\left(1 + \frac{100}{100}\right) \times \frac{20V_1}{20+20} - \frac{100}{100} \times V_2$$

Solution:

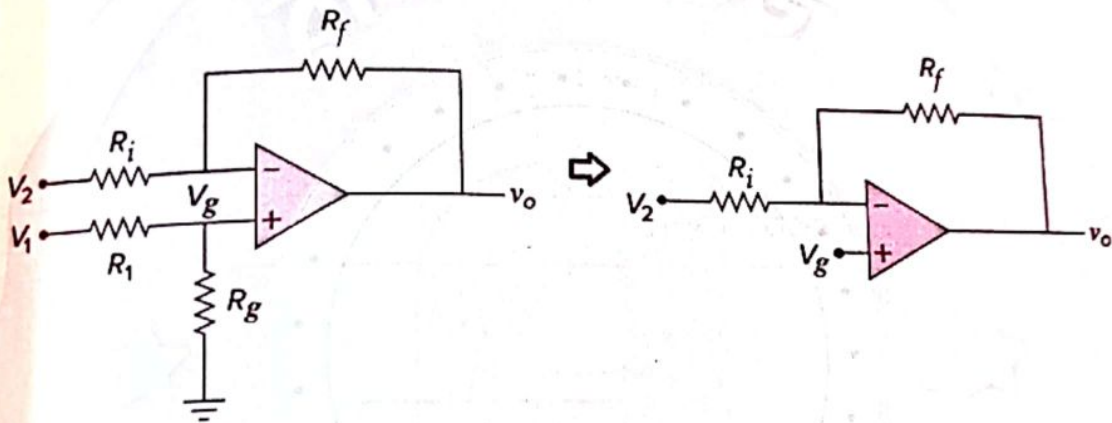


Applying voltage divider rule: $V_g = \frac{R_g}{R_1 + R_g} \times V_1 = \frac{20}{20 + 20} \times V_1 = 0.5 V_1$

$$V_0 = \left(1 + \frac{R_f}{R_i}\right) \times V_g - \frac{R_f}{R_i} \times V_2 = \left(1 + \frac{100}{100}\right) \times 0.5 V_1 - \frac{100}{100} \times V_2 = V_1 - V_2 \quad \text{Ans.}$$

6 Calculate the Output V_0 of the following circuit:


DPDC-14

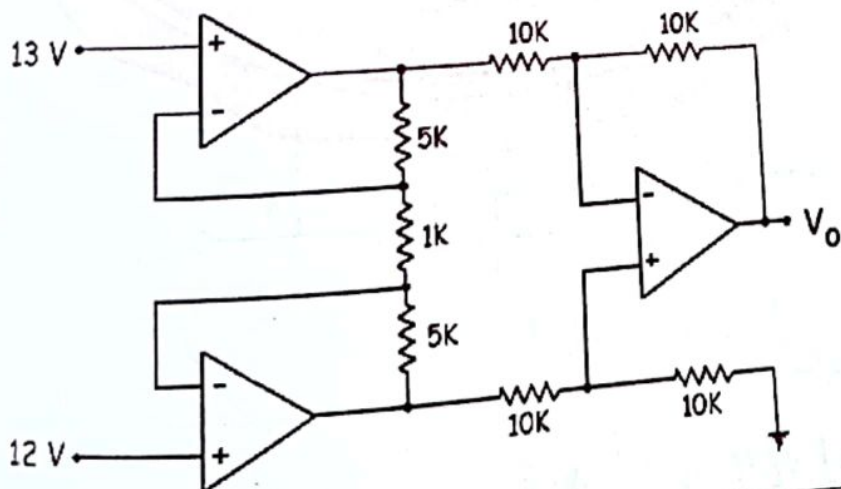

Solution:

The given circuit is a circuit diagram of instrument amplifier. Comparing with the amplifier,


Instrument amplifier

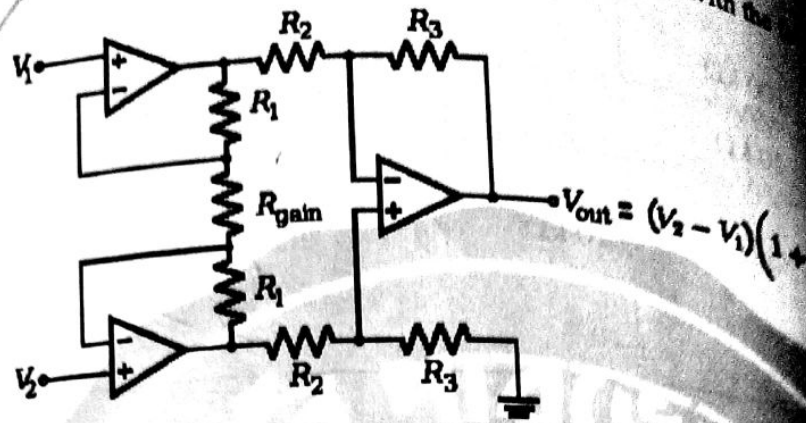


$$\therefore V_0 = (V_2 - V_1) \left(1 + \frac{2R_1}{R_{gain}} \right) \frac{R_3}{R_2} = (12 - 13) \left(1 + 2 \times \frac{5}{1} \right) \times \frac{10}{10} = -11V$$

27 একটি Op-Amp Integrator এর চিত্র আঁকুন।

Solution:

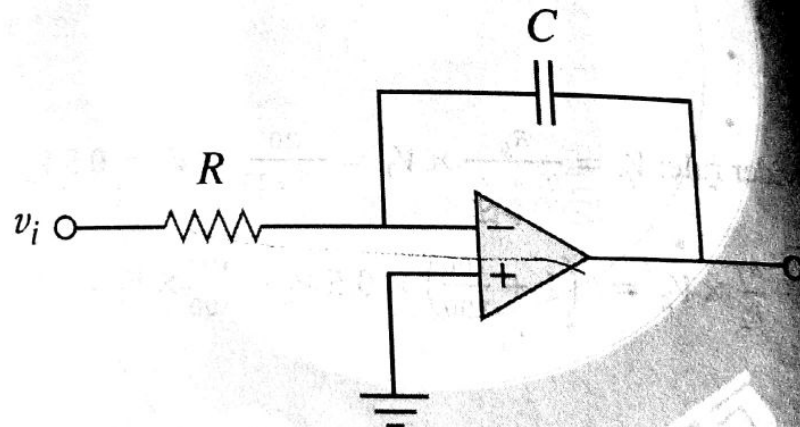

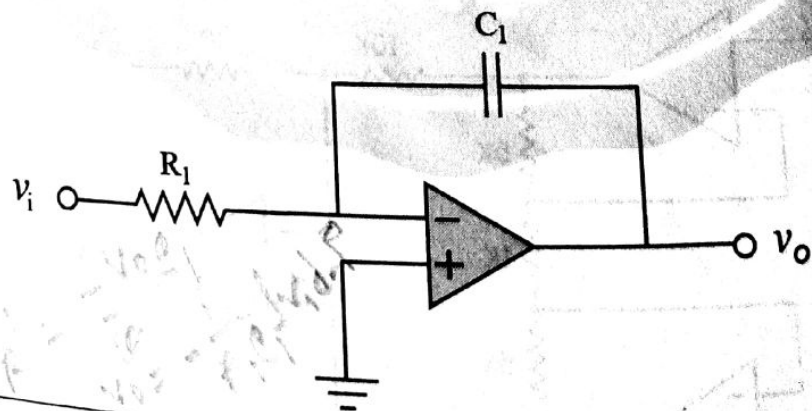28 Find the output of the following circuits:




Solution:

$$V_0 = -\frac{1}{R_1 C_1} \int v_i dt$$

Ans.

Solution (V-1) 2nd Edition
 The output of the following circuit when $V_{IN} = 10 \cos 2\pi \times 10^3 t$.

EGCB-14

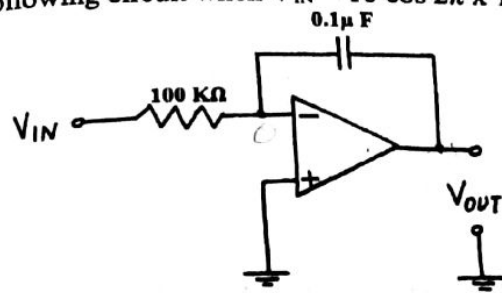

$$V_{in} = -V_{out}$$


$$V_0 = -\frac{1}{RC} \int v_{in} dt$$

$$= -\frac{1}{100 \times 10^3 \times 0.1 \times 10^{-6}} \int_0^t 10 \cos (2\pi \times 10^3) t dt$$

$$= -\frac{1}{100 \times 10^3 \times 0.1 \times 10^{-6}} \times \frac{1}{2\pi \times 10^3} [10 \sin (2\pi \times 10^3) t]_0^t$$

$$= -\frac{1}{2\pi} \sin (2\pi \times 10^3) t \quad \text{Ans.}$$

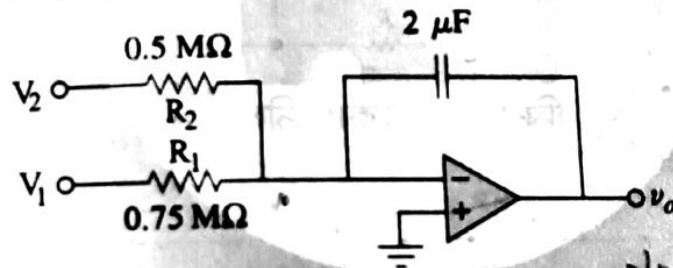দুই সার্কিটের জন্য $V_1 = 10 \sin (200t)$ এবং $V_2 = 15 \sin (200t)$ হলে V_0 এর মান
 এখানে অপ-এম্পটি অসীম গেইনসহ আদর্শ বৈশিষ্ট্যসম্পন্ন।



DPDC-20
(SAE)

$$\frac{1}{R_1} \int v_1 dt - \frac{1}{R_2 C} \int v_2 dt$$

$$\frac{1}{0.75 \times 10^6} \times (2 \times 10^{-6}) \times \int 10 \sin(200t) dt - \frac{1}{(0.5 \times 10^3) \times (2 \times 10^{-6})} \times \int 15 \sin(200t) dt$$

$$= \frac{1}{5} \times \left\{ 10 \times \frac{1}{200} \times \cos(200t) \right\} - 1 \times \left\{ 15 \times \frac{1}{200} \times \cos(200t) \right\}$$

$$= 0.33 \cos(200t) - 0.075 \cos(200t)$$

$$= 0.255 \cos(200t) \quad \text{Ans.}$$