Status Register:


A **status register**, flag **register**, or **condition** code **register** (CCR) is a collection of **status** flag **bits** for a processor. For example, a Z **bit** may be set if the result of the operation is zero and cleared if it is nonzero. Other classes of instructions may also modify the flags to indicate **status**.


The **status register** lets an instruction take action contingent on the outcome of a previous instruction. Typically, flags in the **status register** are modified as effects of arithmetic and bit manipulation operations.

Status register

- Relative magnitude of two numbers may be determined by subtracting one from the other.
- Also called as flag bits or condition code bits
- Status Bits
 - □ C Carry
 - S Sign bit
 - Z zero bit
 - V Overflow bit

Status register

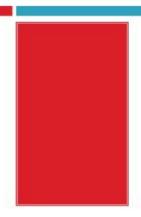

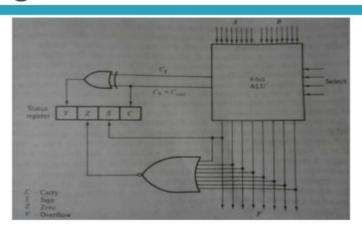


Status register

- C Carry bit
 - Set if the output carry of ALU is 1
- □ S Sign bit
 - Set if the highest order bit is 1
- Z Zero bit
 - Set if the ALU's output contains all zeros
- V Overflow bit
 - Set if there is any overflow. For a 8bit ALU, V is set if the result is greater than 127 and less than -128

(A-B) of unsigned numbers

Aa	nd	В	are
uns	igr	nec	d
nun	nbe	ers	5

Relation	Condition of status bits	Boolean function
A>B	C=1 and Z=0	CZ'
A>=B	C=1	С
A <b< td=""><td>C=0</td><td>C'</td></b<>	C=0	C'
A<=B	C=0 or Z=1	C'+Z
A=B	Z=1	Z
A≠B	Z=0	Z'

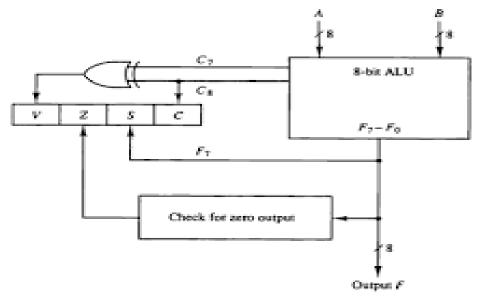

Status register bits.

5.5. ALU status register

The ALU results are characterized by four status bits (C, S, Z, and V), which are defined as follows:

- Bit Cy (carry) is set to 1 only when the operation is an arithmetic operation and its carry output is 1. It is cleared to 0 if the carry is 0.
- Bit S (sign) is set to 1 if the most significant bit of the result C3 is one..
- Bit Z (zero) is set to 1 only if the output of the ALU contains all 0's. It is set to 0
 otherwise.
- Bit V (overflow) is set to 1 only when an overflow occurs when performing operations on signed numbers in 2's complement representation (exclusive-OR of the 2 most significant carries).

Derive the logic equations of the status bits and implement them with conventional gates.